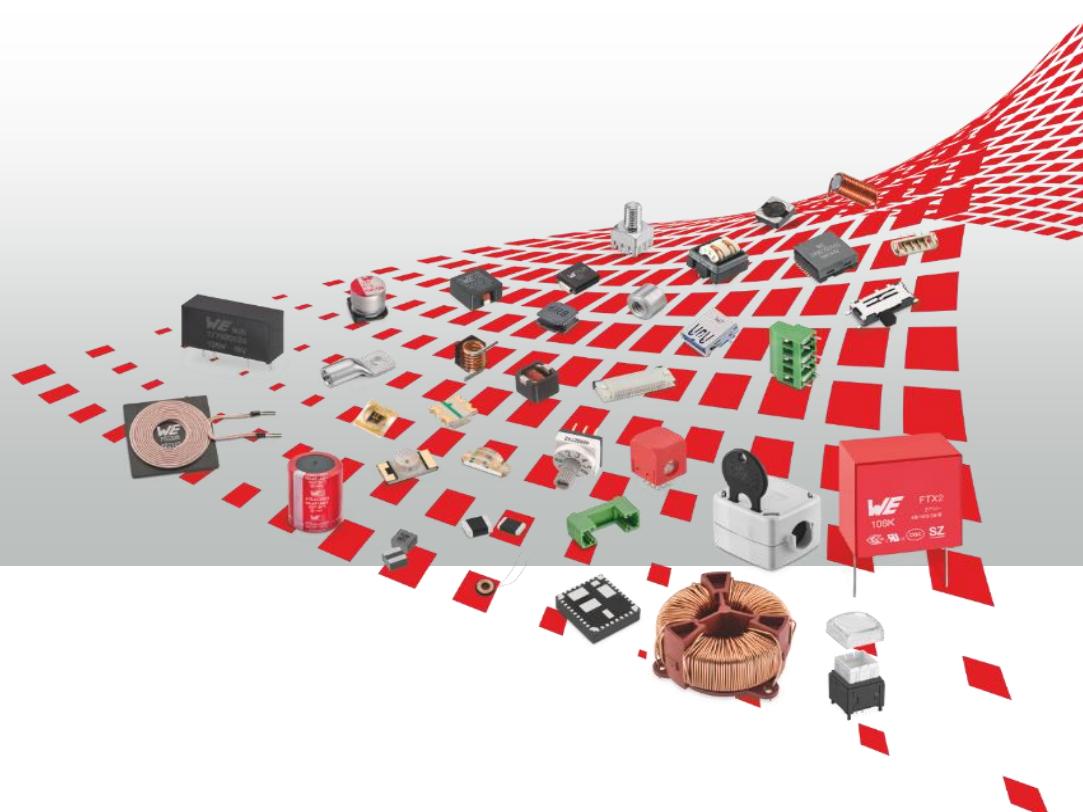




# Anticipate EMC with LTSPICE

**more  
than you  
expect**



**Sylvain Le Bras**  
Field Application Engineer

[Sylvain.LeBras@w-e-online.com](mailto:Sylvain.LeBras@w-e-online.com)

# Anticipate EMC with LTSpice

Using LTSPICE and Redexpert to check power supply designs




- Intro : From functional simulation...

- Output ripple of a Buck
- Extracting EMC accurate data from REDEXPERT
- Example of (non) EMC accurate impact on simulation

- ...To EMC simulation

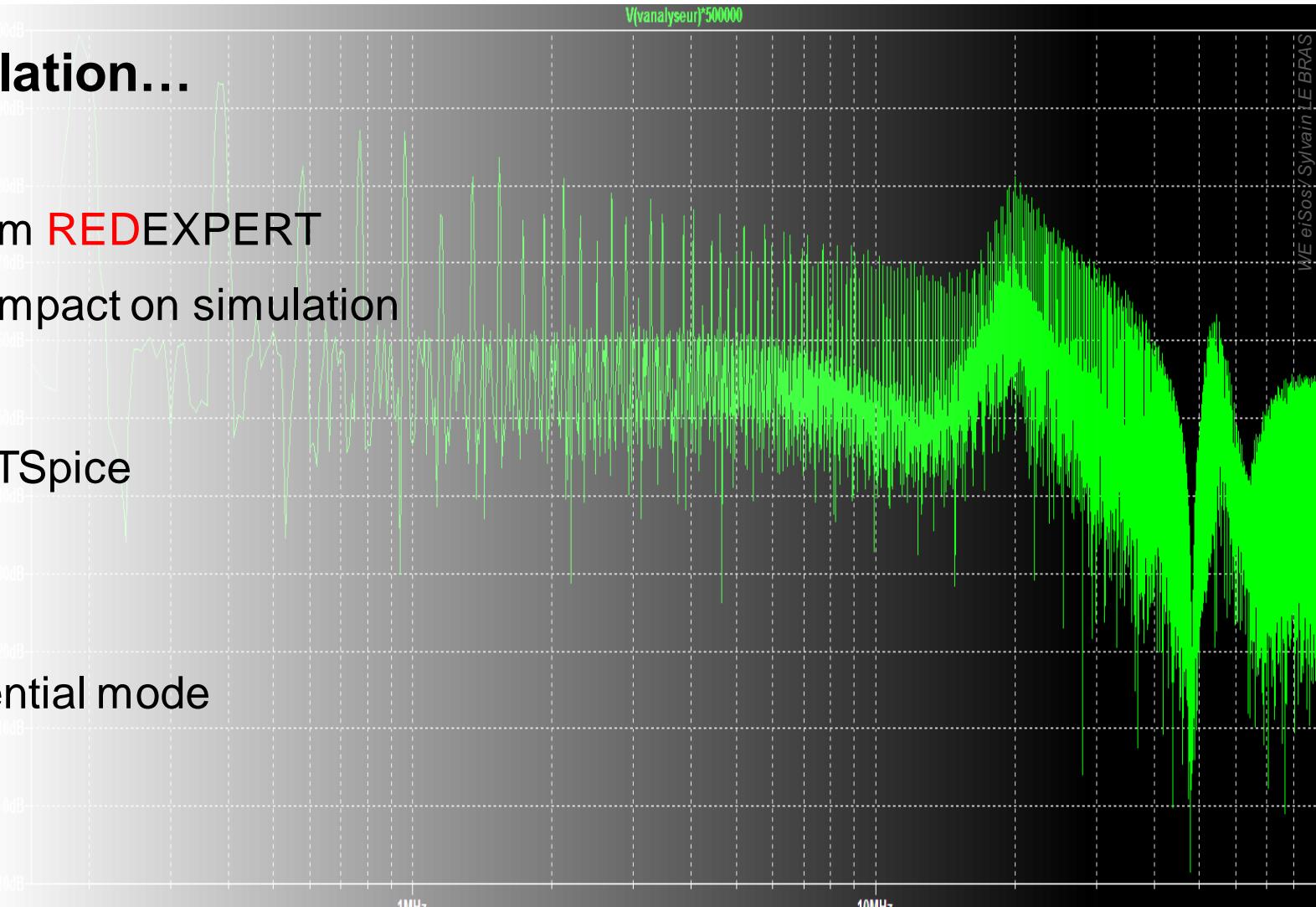- Enabling EMC measurement in LTSpice
- Getting Seriously Accurate ?
- Going further with simulation
  - Splitting Common and Differential mode
  - Making simulation look real
- Examples




# Anticipate EMC with LTSpice

## Using LTSPICE and Redexpert to check power supply designs



### ■ Available examples

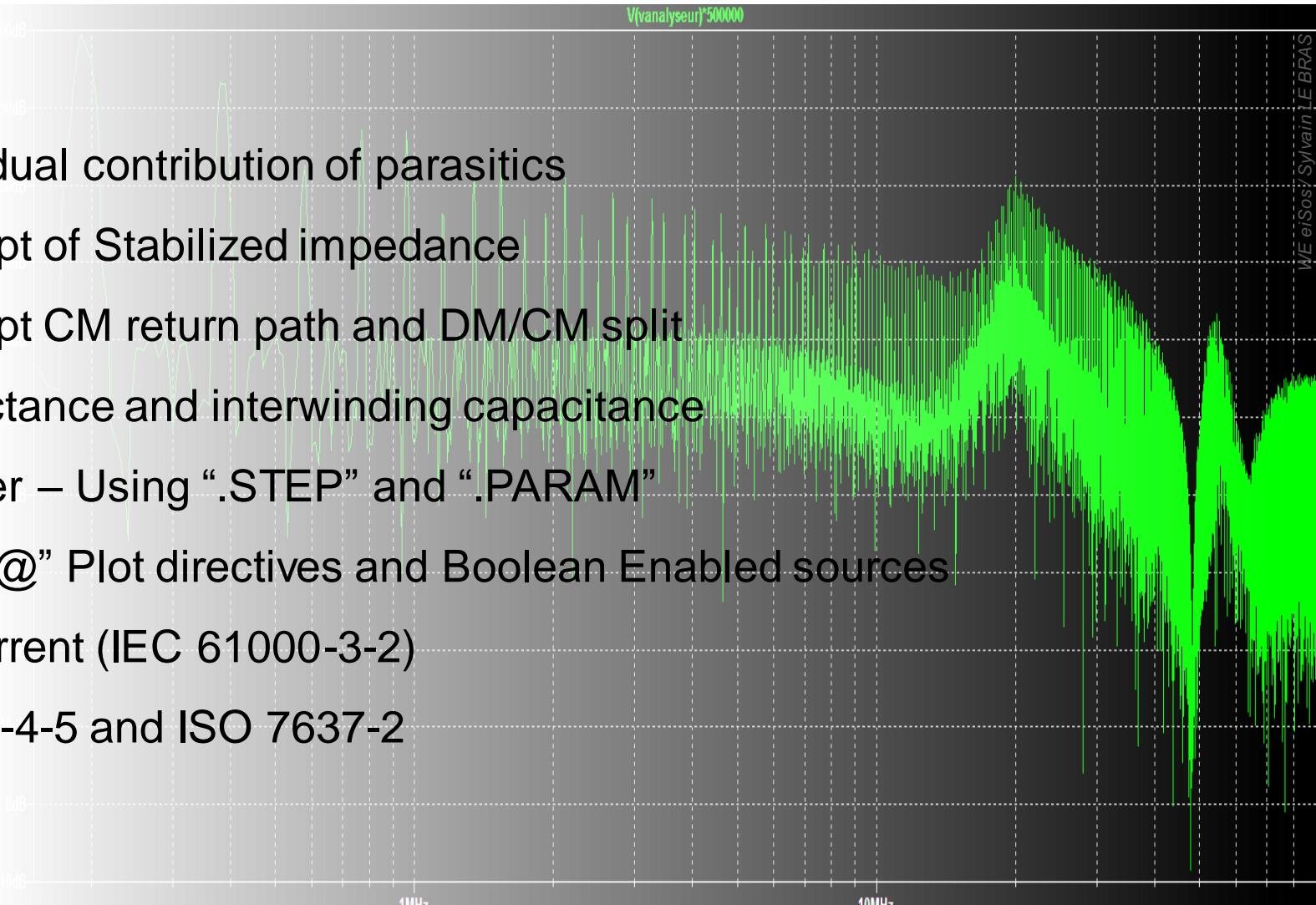1. Output ripple of a Buck – Individual contribution of parasitics
2. Noise at Input of Buck – Concept of Stabilized impedance
3. Noise at Input of Buck – Concept CM return path and DM/CM split
4. Flyback converter – Stray inductance and interwinding capacitance
5. Brushless DC motor and inverter – Using “.STEP” and “.PARAM”
6. Evaluation of filter response – “@” Plot directives and Boolean Enabled sources
7. Power Factor and Harmonic current (IEC 61000-3-2)
8. Surges according to IEC 61000-4-5 and ISO 7637-2



# Setup

## Getting the tools ready



NOW PART OF




<https://www.analog.com/en/design-center/design-tools-and-calculators/ltspice-simulator.html>

# RED EXPERT

<https://www.we-online.com/redexpert>

# Intro : From functional simulation...

## Output ripple of a Buck

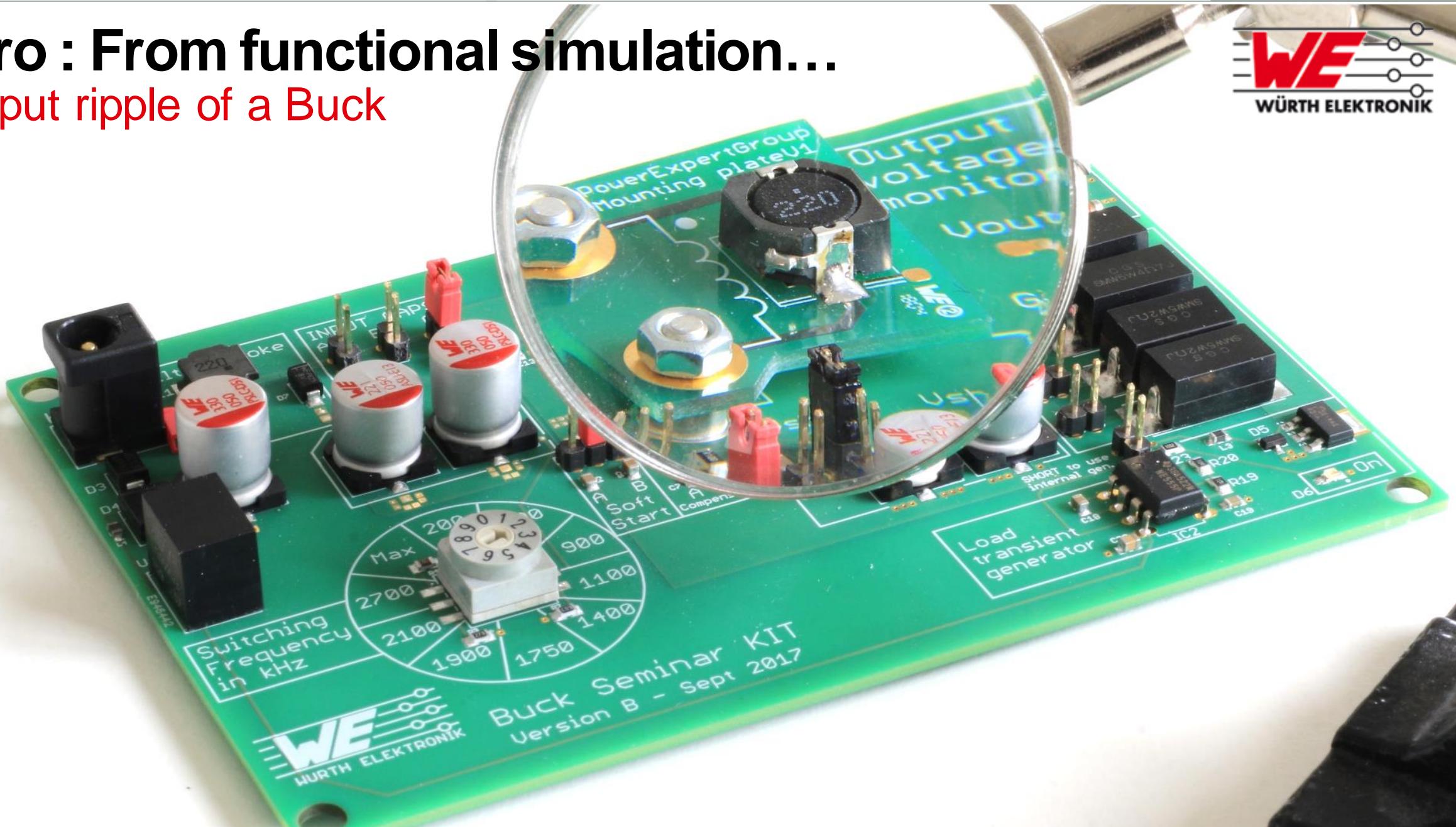

# Intro : From functional simulation...


## Output ripple of a Buck



The image shows the LTspice XVII software interface. A yellow component symbol for the LT3975 is centered on the workspace. The symbol has seven pins labeled: EN, Vin, PG, OUT, SS, Boost, Rt, SW, GND, and FB. The LT logo is visible inside the symbol. To the right of the symbol, a modal dialog box displays the following text:  
LTspice XVII  
42V, 2.5A, 2MHz Step-Down Switching Regulator with  
2.7 $\mu$ A Quiescent Current  
Note: Sync pin is not  
modeled; Burst Mode is selected.  
Buttons in the dialog box include: Open this macromodel's test fixture, Go to Linear's website for datasheet, and Cancel.
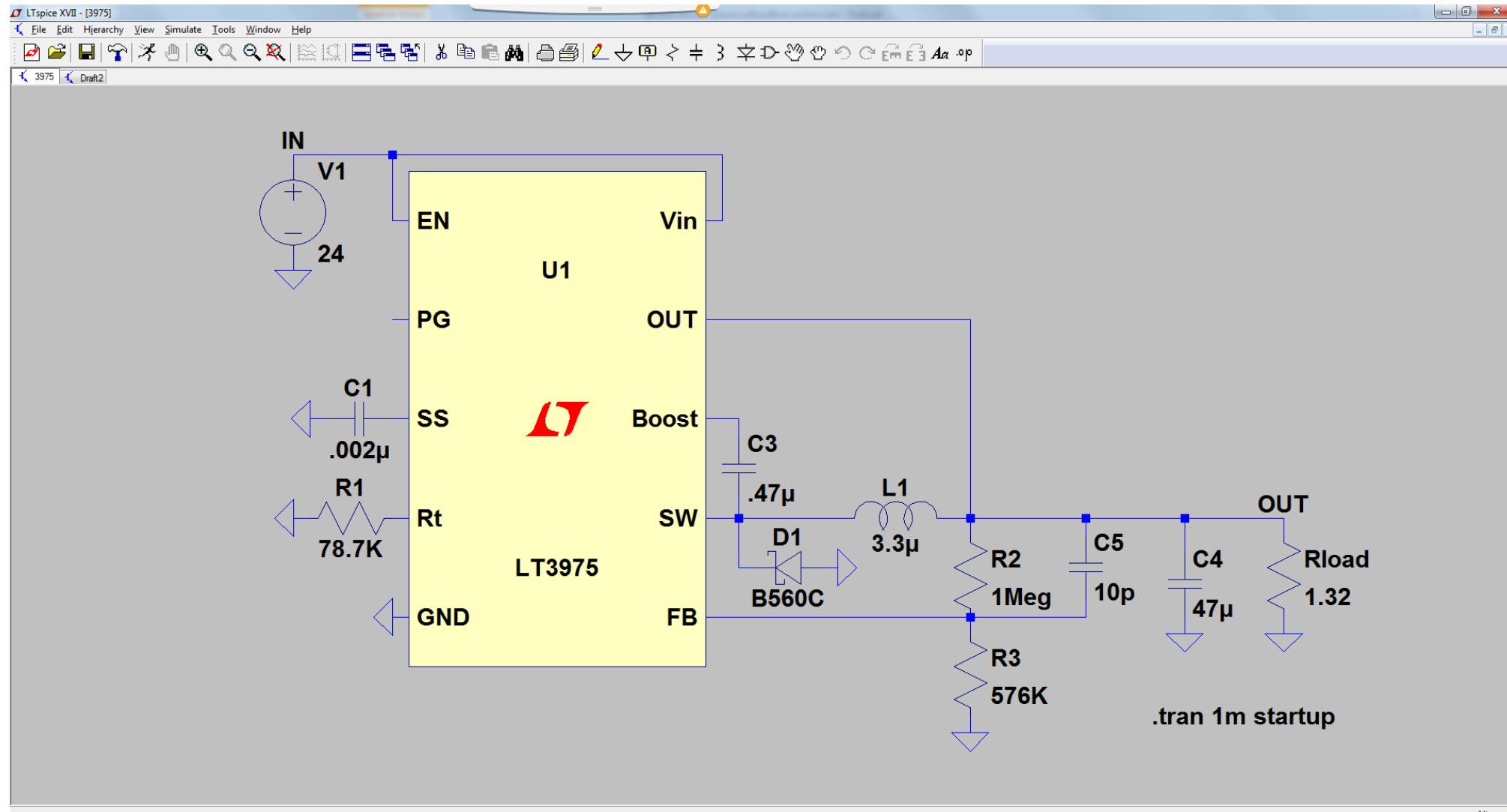
# Intro : From functional simulation...

Output ripple of a Buck (without the “hardcore mathematics”)




# Output ripple of a Buck

## Hardcore maths ?



$$V = R \cdot I$$

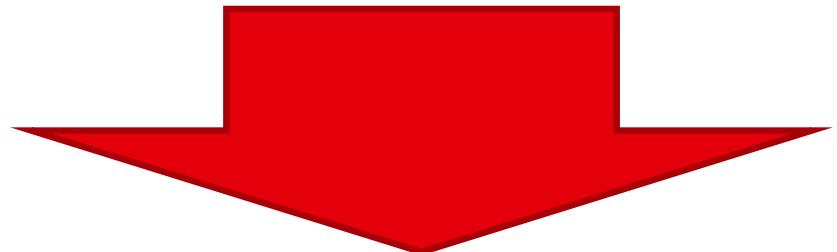


$$\Delta V = Z_C \cdot \Delta I_L$$

# Output ripple of a Buck

## Redexpert : an ode to laziness


REDEXPERT® ALUMINIUM ELECTROLYTIC CAPACITORS

APPLICATIONS

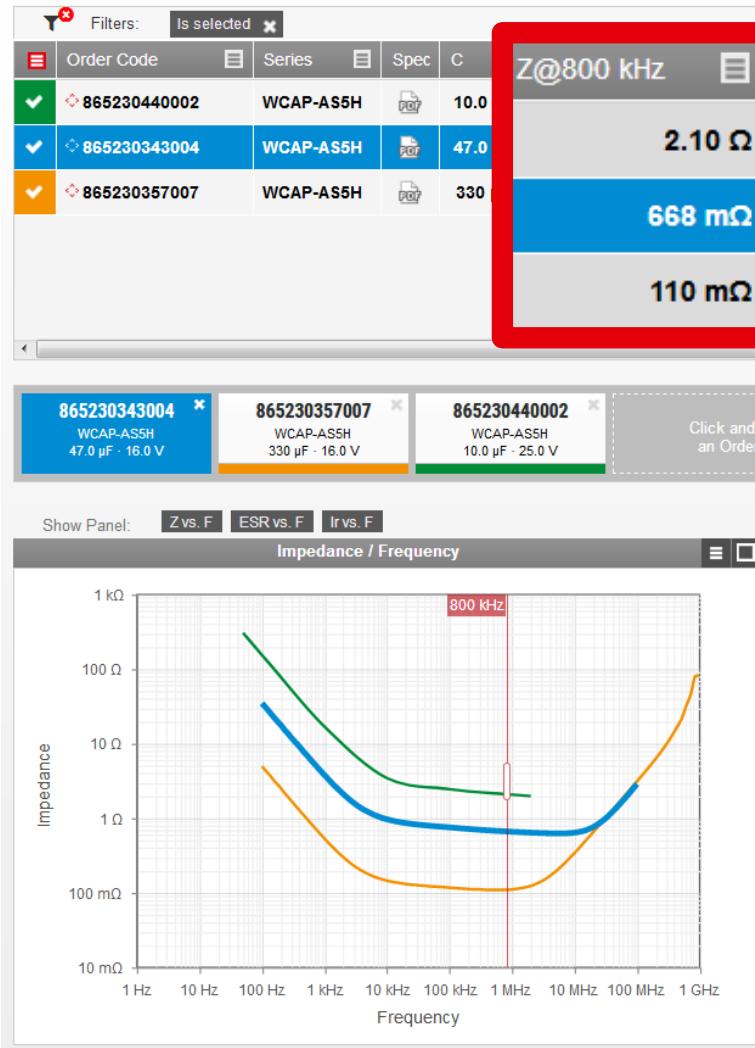

ZC

ΔIL

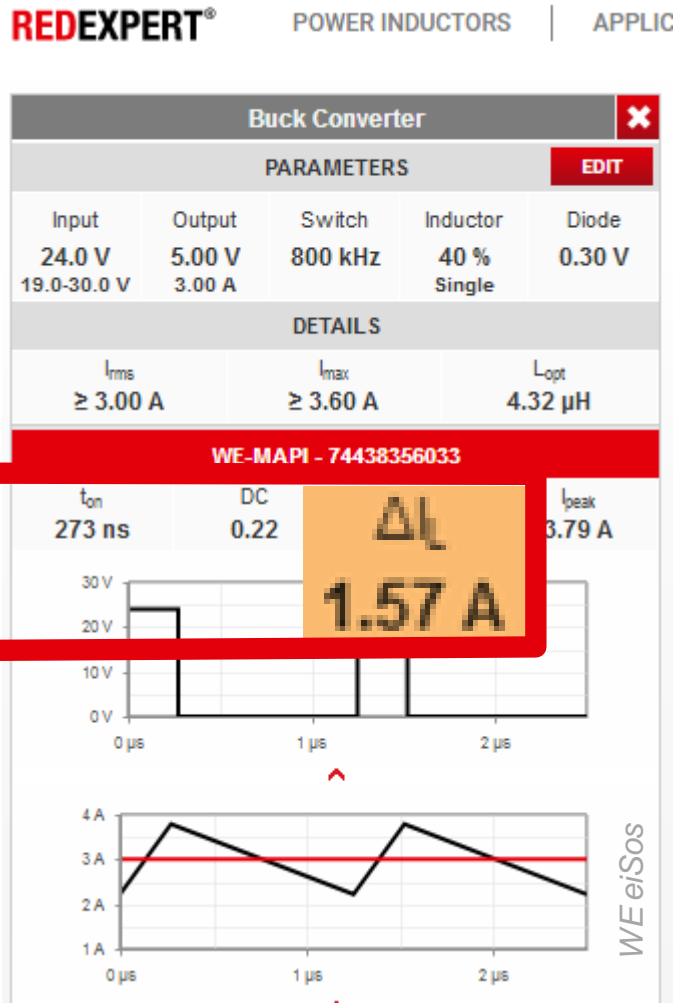

# Output ripple of a Buck


## Redexpert : an ode to laziness

REDEXPERT® ALUMINIUM ELECTROLYTIC CAPACITORS | APPLICATIONS | HOW TO |  SHARE

 ITEMS  LE BRAS


Order Code	Series	Sp...	C	V <sub>R</sub>	Z@800 kHz	DF	Z <sub>max</sub> @ 100kHz	I <sub>ripple</sub> @ T <sub>max</sub> °C 120Hz	I <sub>ripple</sub> @ T <sub>max</sub> 100kHz	Description	I <sub>leak</sub>
865230440002	WCAP-AS5H		10.0 µF	25.0 V	2.10 Ω	< 16 %		23.0 mA		ASDB055100M025DVCTAE000	3.00
865230343004	WCAP-AS5H		47.0 µF	16.0 V	668 mΩ	< 22 %		50.0 mA		ASDD055470M016DVCTBE000	7.52
865230357007	WCAP-AS5H		330 µF	16.0 V	110 mΩ	< 22 %		300 mA		ASDF105331M016DVCTEE000	52.8

Filters: Is selected  

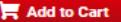
Click and type or drop an Order Code here  Add to Cart 

Show Panel: Z vs. F ESR vs. F Ir vs. F


**Impedance / Frequency**

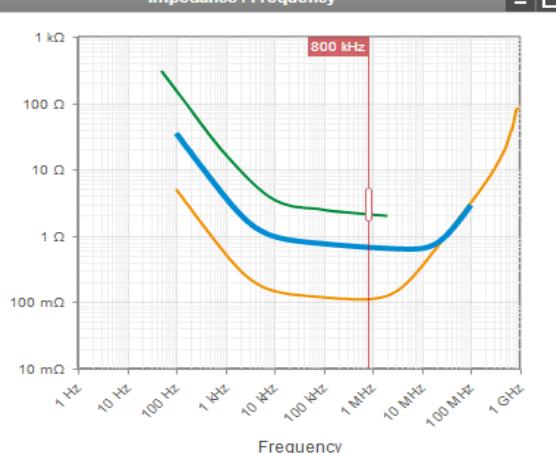

**ESR / Frequency**

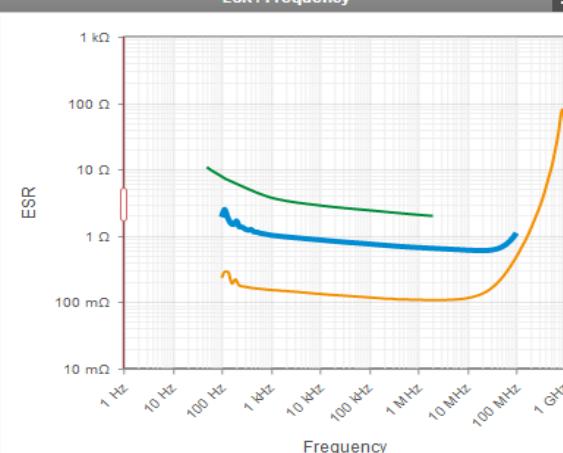

**Ripple Current / Frequency**

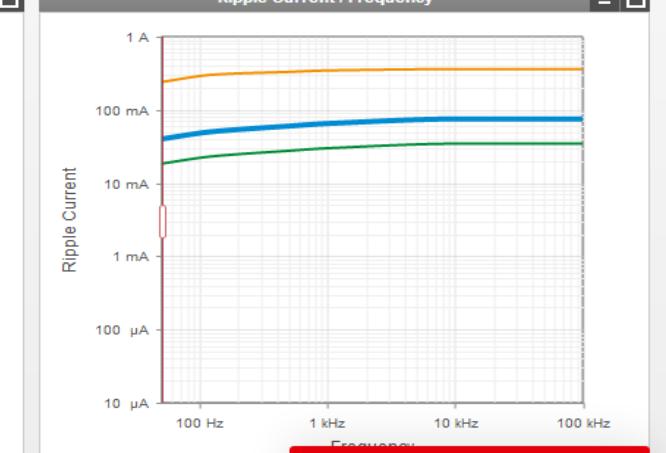

WE eiSos

ABOUT WÜRTH ELEKTRONIK SITEMAP CONTACT IMPRINT COPYRIGHT © 2018 WÜRTH ELEKTRONIK GMBH. ALL RIGHTS RESERVED.

 Schreiben Sie uns

[Link](#)

# Output ripple of a Buck

## Redexpert : an ode to laziness



REDEXPERT®

POWER INDUCTORS

APPLICATIONS

HOW TO

SHARE

ITEMS

LE BRAS

**Buck Converter**

PARAMETERS					EDIT				
Input 24.0 V 19.0-30.0 V	Output 5.00 V 3.00 A	Switch 800 KHz	Inductor 40 % Single	Diode 0.30 V					
<b>DETAILS</b>									
$I_{rms}$ $\geq 3.00 \text{ A}$	$I_{max}$ $\geq 3.60 \text{ A}$	$L_{opt}$ 4.32 $\mu\text{H}$							
<b>WE-MAPI - 74438356033</b>									
$t_{on}$ 273 ns	DC 0.22	$\Delta I_L$ 1.57 A	$I_{peak}$ 3.79 A						
<table border="1"> <tr> <td>AC Losses 179 mW</td> <td>DC Losses 359 mW</td> <td>Total Losses 538 mW</td> <td><math>\Delta T_{TOT}</math> 42.0 K</td> </tr> </table>						AC Losses 179 mW	DC Losses 359 mW	Total Losses 538 mW	$\Delta T_{TOT}$ 42.0 K
AC Losses 179 mW	DC Losses 359 mW	Total Losses 538 mW	$\Delta T_{TOT}$ 42.0 K						
<table border="1"> <tr> <td>P vs. <math>V_{in}</math></td> <td>P vs. <math>f_{sw}</math></td> <td>P vs. <math>I_{out}</math></td> </tr> </table>						P vs. $V_{in}$	P vs. $f_{sw}$	P vs. $I_{out}$	
P vs. $V_{in}$	P vs. $f_{sw}$	P vs. $I_{out}$							

**Filters:** Type = Single |  $I_R \geq 3.00 \text{ A}$  |  $I_{sat} \geq 3.60 \text{ A}$  |  $3.02 \mu\text{H} \leq L_0 \leq 5.62 \mu\text{H}$

Order Code	Series	Size	Sp...	Type	$L_0$	$R_{DC,typ}$	$I_R$	$I_{sat}$	$P_{AC}$	$P_{DC}$	$P_T$
74438356033	WE-MAPI	4020		Single	3.30 $\mu\text{H}$	39.9 mΩ	3.60 A	5.50 A	179 mW	359 mW	5
74438357047	WE-MAPI	4030		Single	4.70 $\mu\text{H}$	39.9 mΩ	3.90 A	6.40 A	102 mW	359 mW	4
74438357056	WE-MAPI	4030		Single	5.60 $\mu\text{H}$	46.5 mΩ	3.60 A	6.00 A	94.9 mW	418 mW	3
744071039	WE-TPC	8043		Single	3.90 $\mu\text{H}$	13.0 mΩ	4.90 A	4.50 A	241 mW	117 mW	2
744071047	WE-TPC	8043		Single	4.70 $\mu\text{H}$	17.0 mΩ	4.80 A	4.30 A	200 mW	153 mW	1
744071056	WE-TPC	8043		Single	5.60 $\mu\text{H}$	20.0 mΩ	4.00 A	4.00 A	168 mW	180 mW	0

Click and type or drop an Order Code here

Add to Cart

More...

Show Panel: **L vs. I(T)** | **K vs. I(T)**

**Inductance / DC Current (Ambient Temperature)**


T = 20°C

**Temperature Rise / DC Current (Ambient Temperature)**

T = 20°C

# Output ripple of a Buck
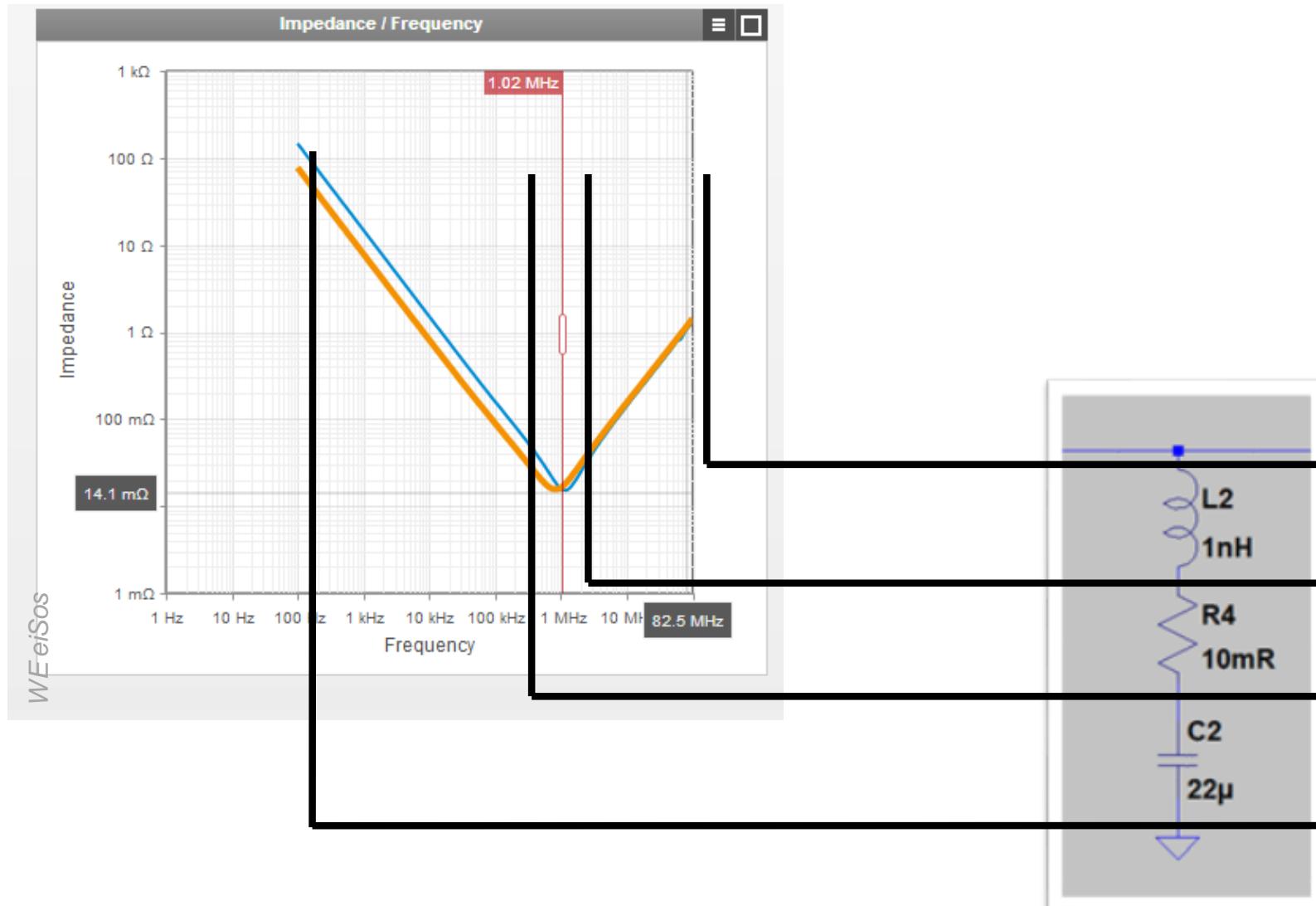
## Extracting EMC accurate data from REDEXPERT




# Output ripple of a Buck

Extracting EMC accurate data from REDEXPERT




## ESL identification

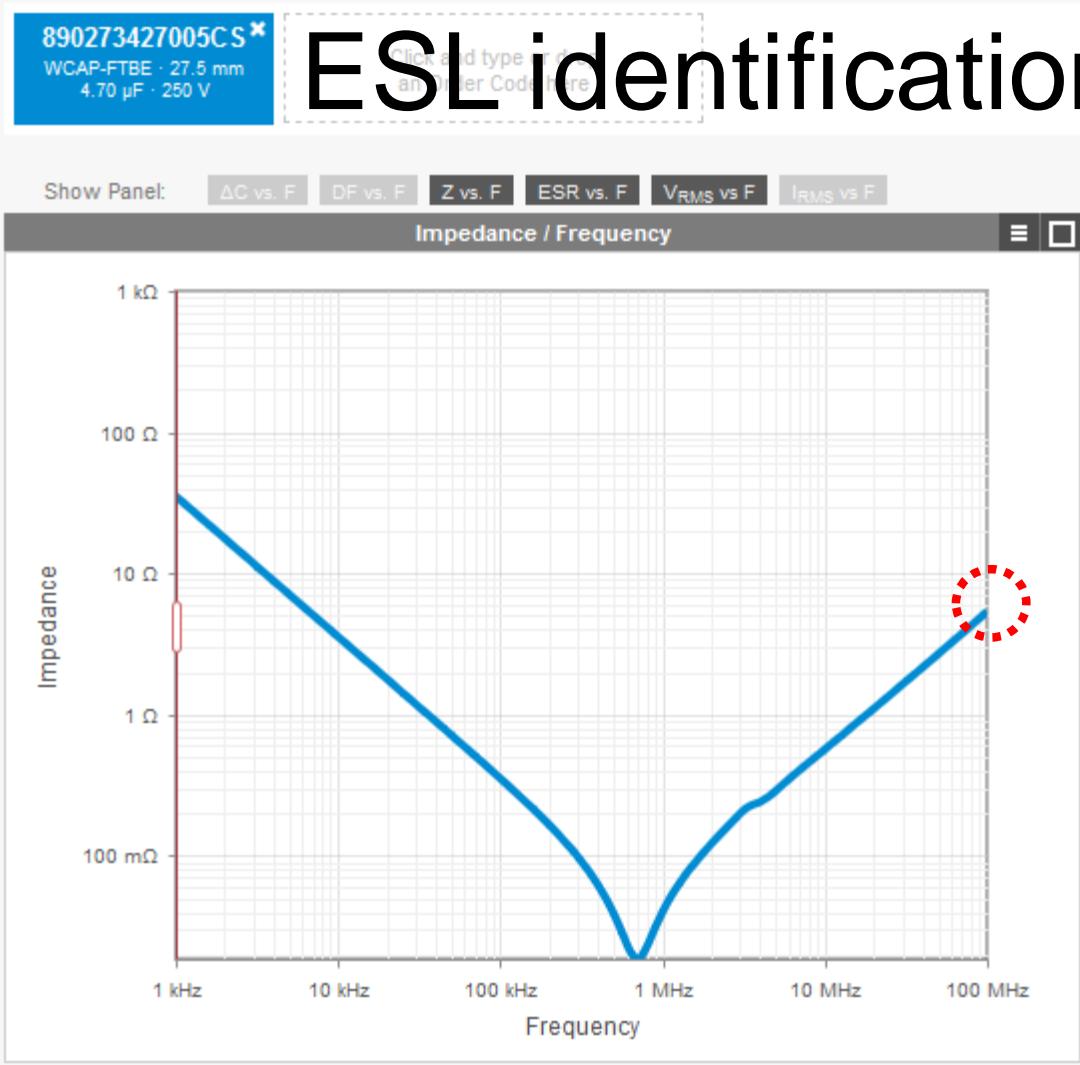

$$|Z_L| = L\omega$$


$$\frac{Z_L}{\omega} = L$$

$$L = \frac{|Z_L|}{2\pi F} = \frac{5}{100 \times 10^6 \times 2\pi} \cong 8 \text{ nH}$$

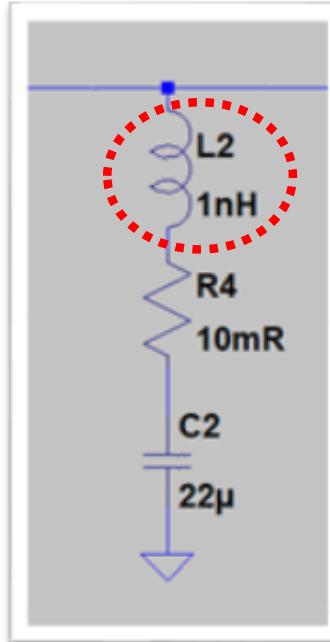
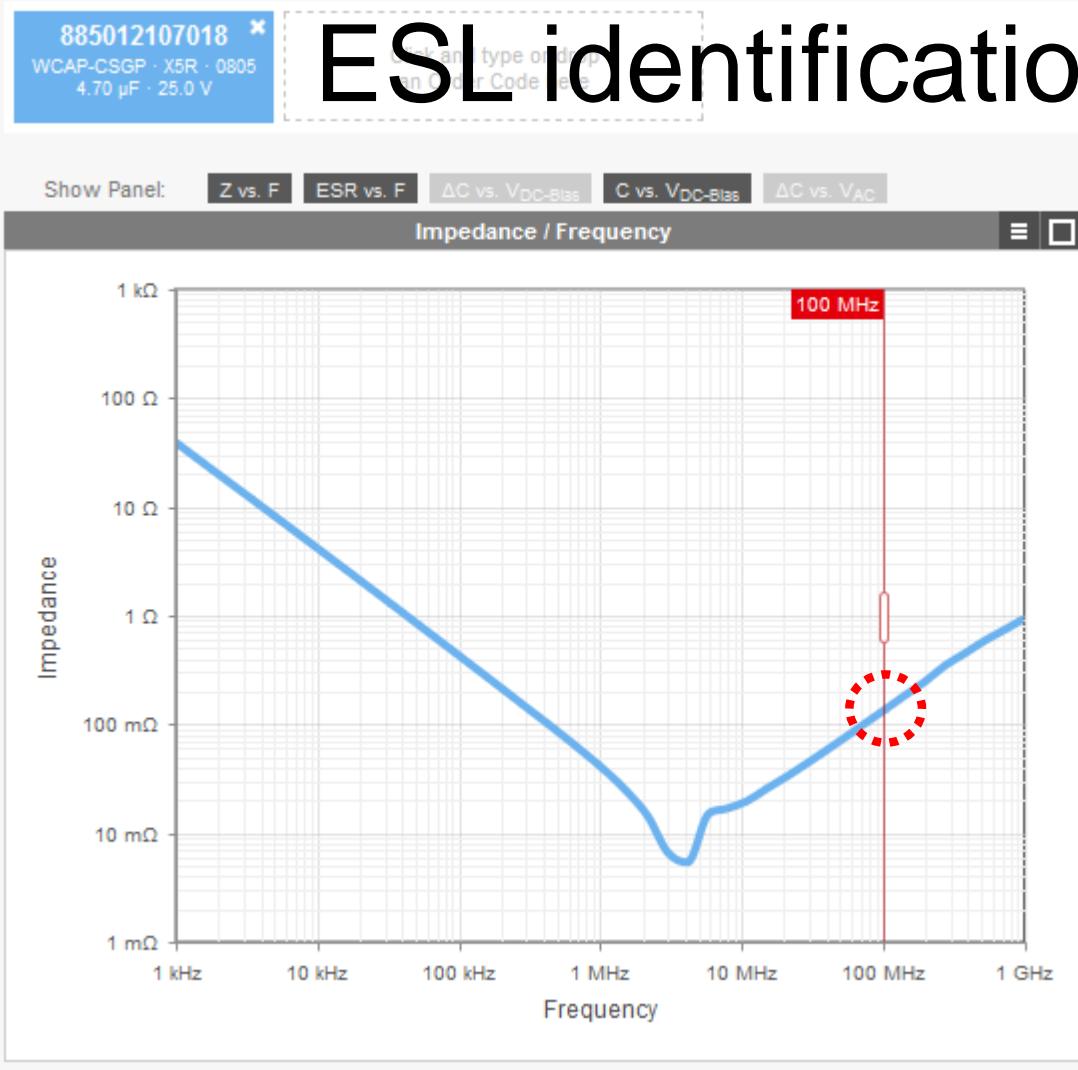
# Output ripple of a Buck


Extracting EMC accurate data from REDEXPERT



$$|Z_L| = L\omega$$



$$\frac{Z_L}{\omega} = L$$

$$L = \frac{|Z_L|}{2\pi F} = \frac{0,132}{100 \times 10^6 \times 2\pi} \cong 0.2 \text{ nH}$$

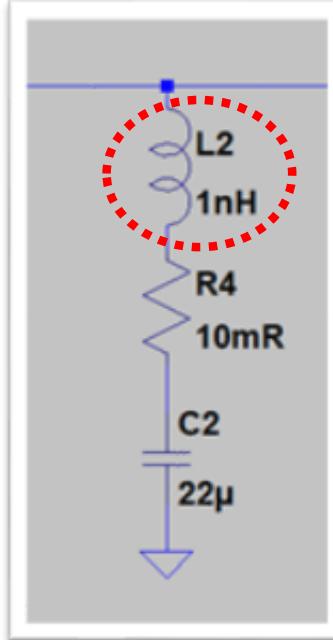

# Output ripple of a Buck

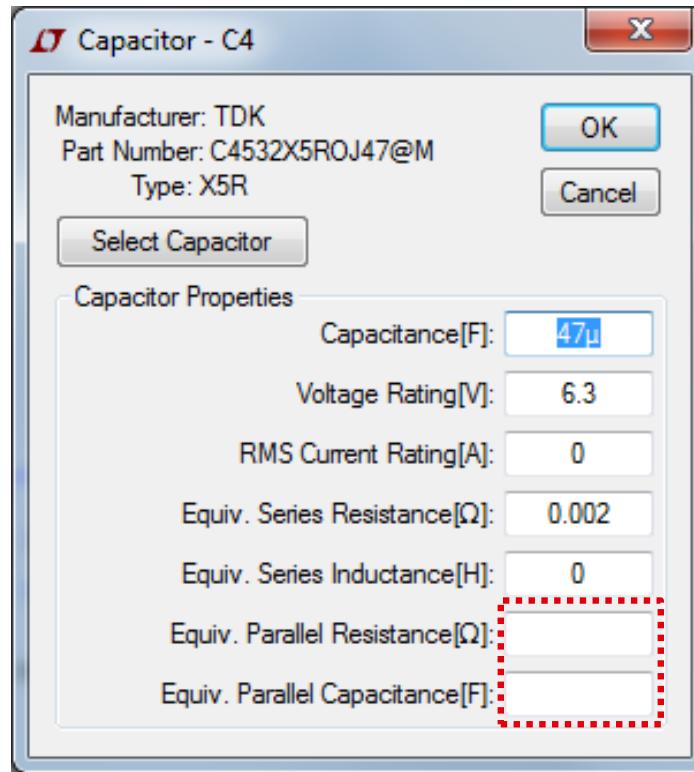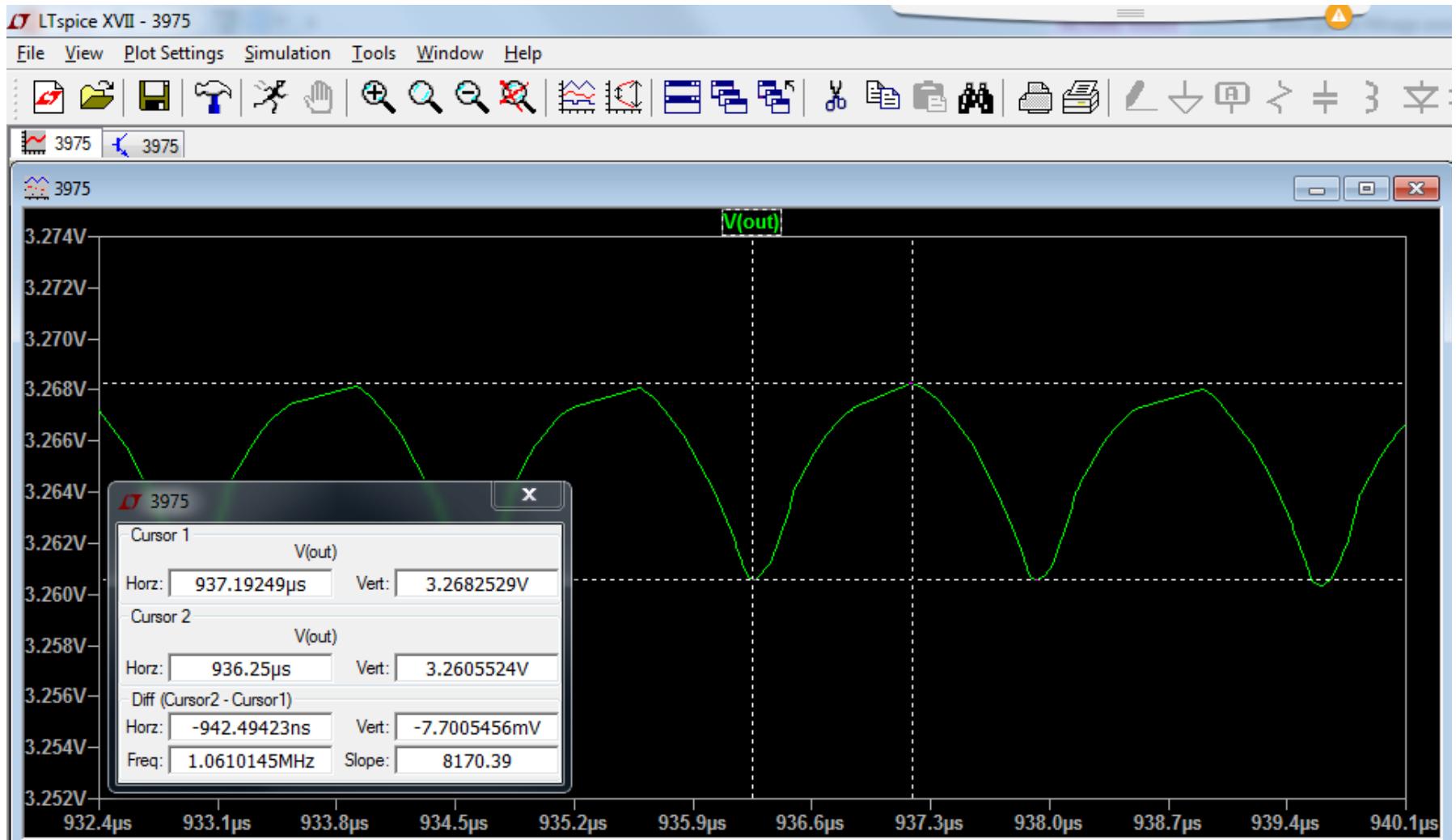
Example of (non) EMC accurate impact on simulation



- ESR = 2 mOhms
  - ESL = 0 nH
  - DC bias
- (DC ? Like don't care ?)

# Output ripple of a Buck

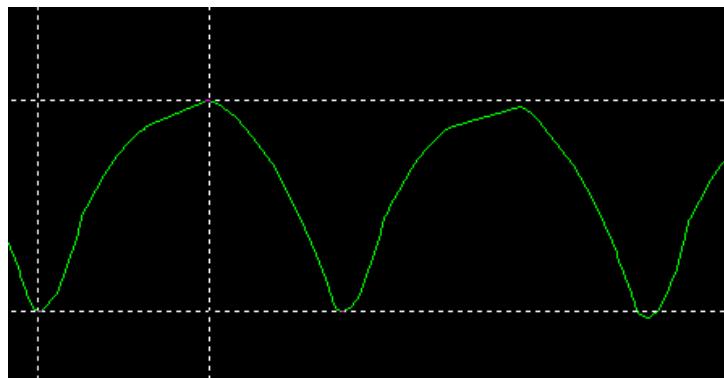Example of (non) EMC accurate impact on simulation



# Output ripple of a Buck

Example of EMC accurate simulation

Charge and discharge of cap



$14 \text{ mV}_{p-p}$





$16 \text{ mV}_{p-p}$





$10 \text{ mV}_{p-p}$  at low frequencies

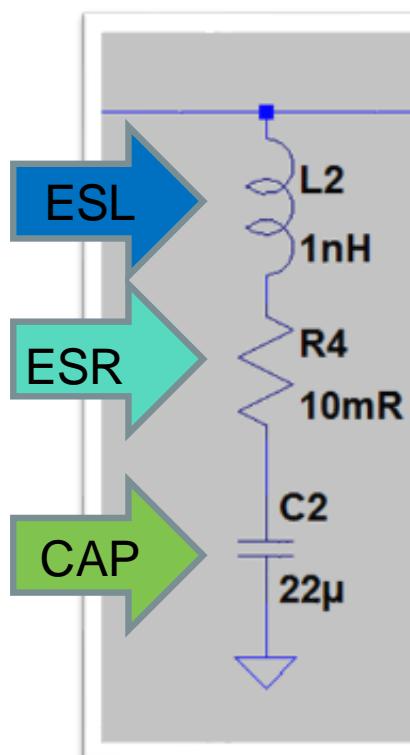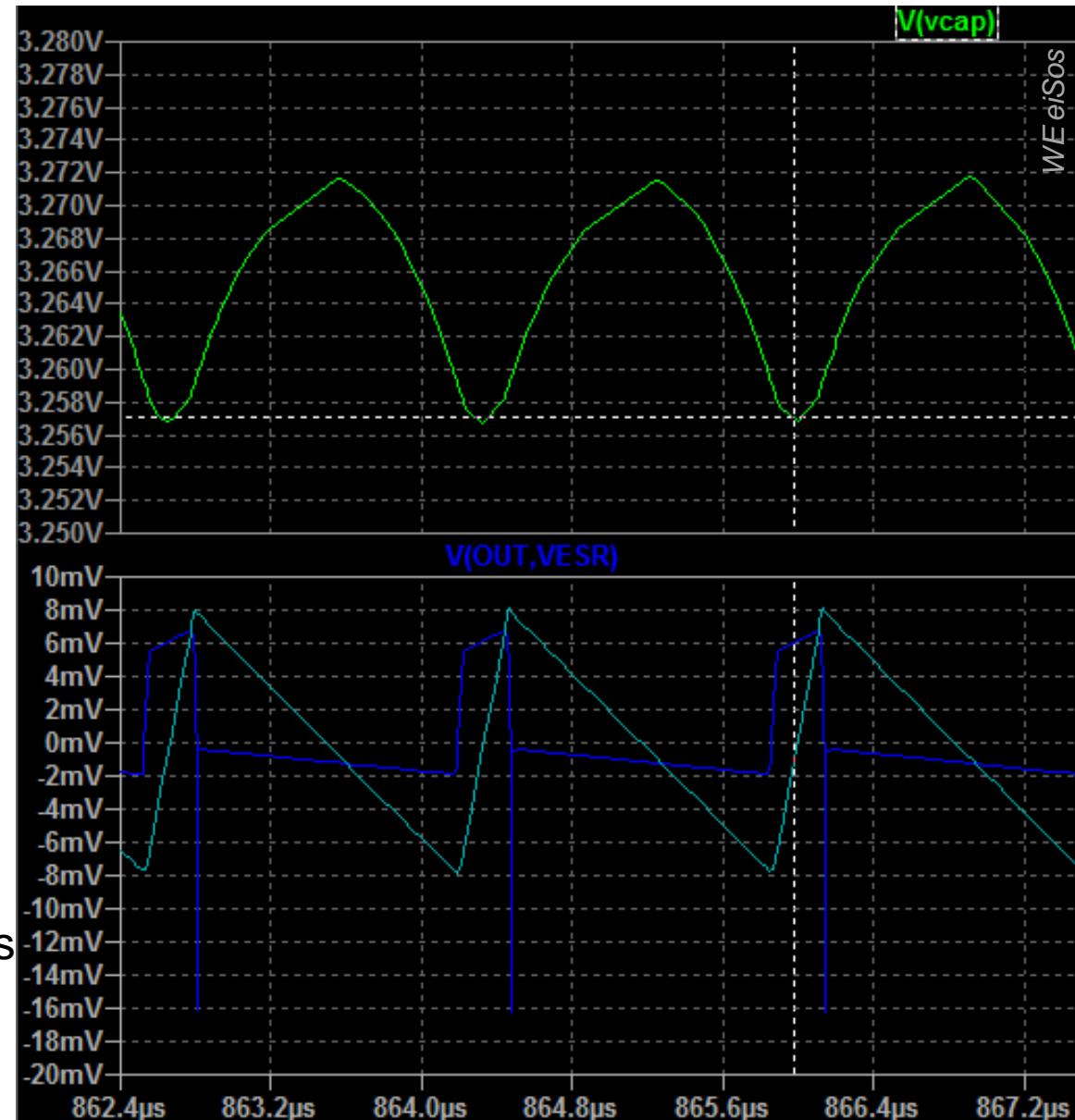$25 \text{ mV}_{p-p}$  at high frequencies



# Capacitor ripple voltage example
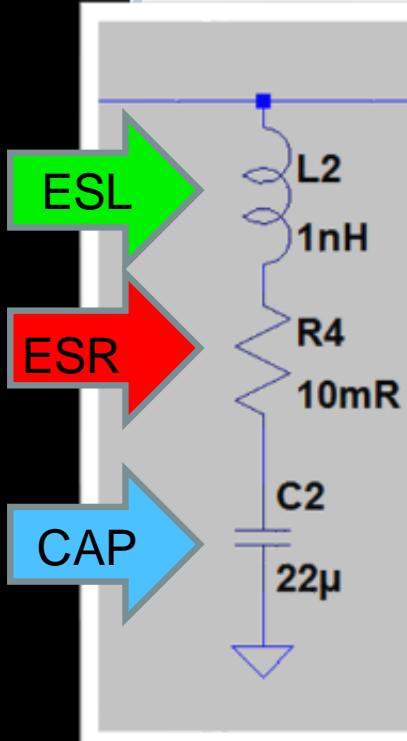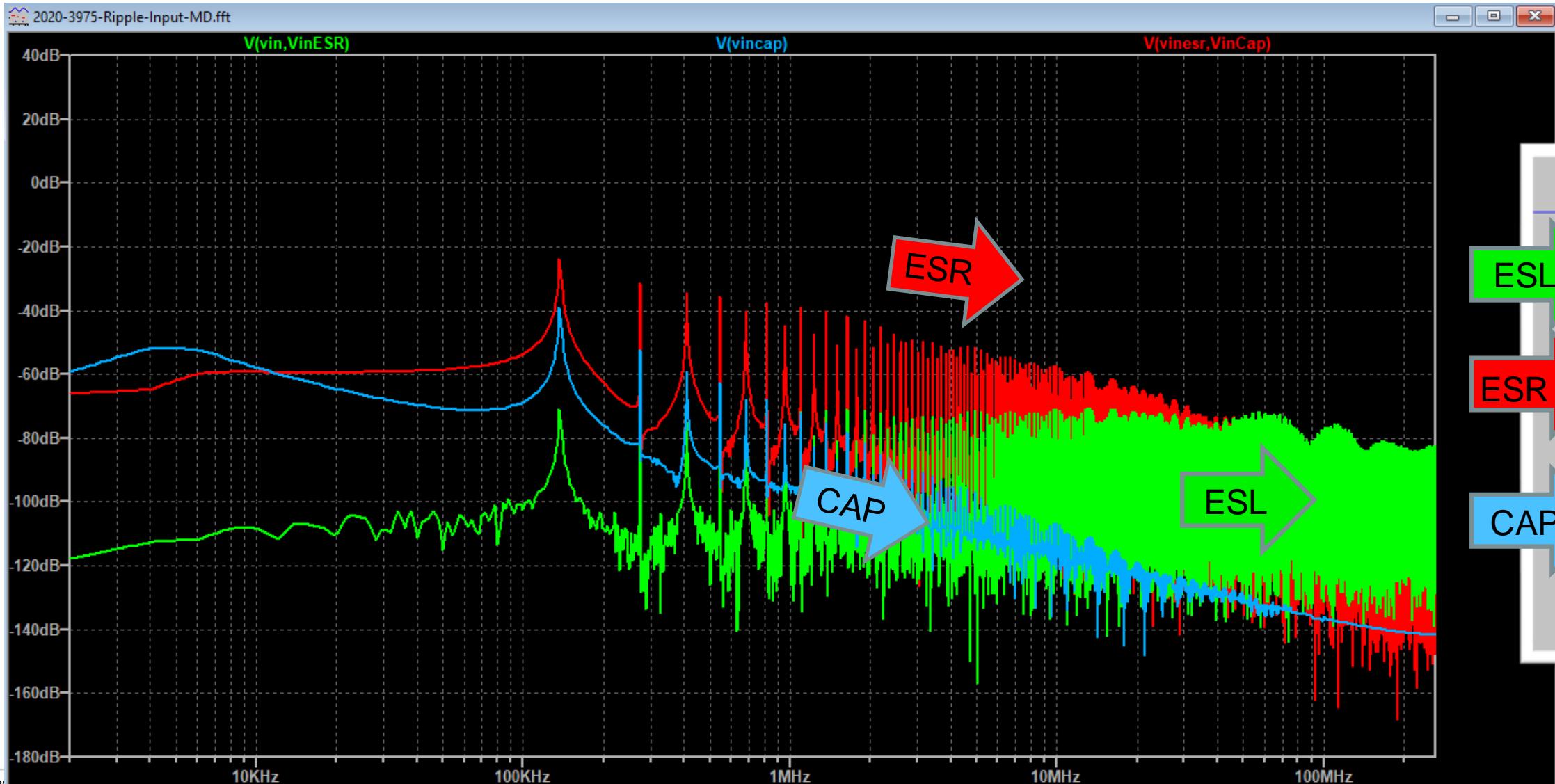
## ESR / ESL / CAP breakdown in frequency




# ... To EMC simulation

The missing link




WE eiSos / Sylvain LE BRAS

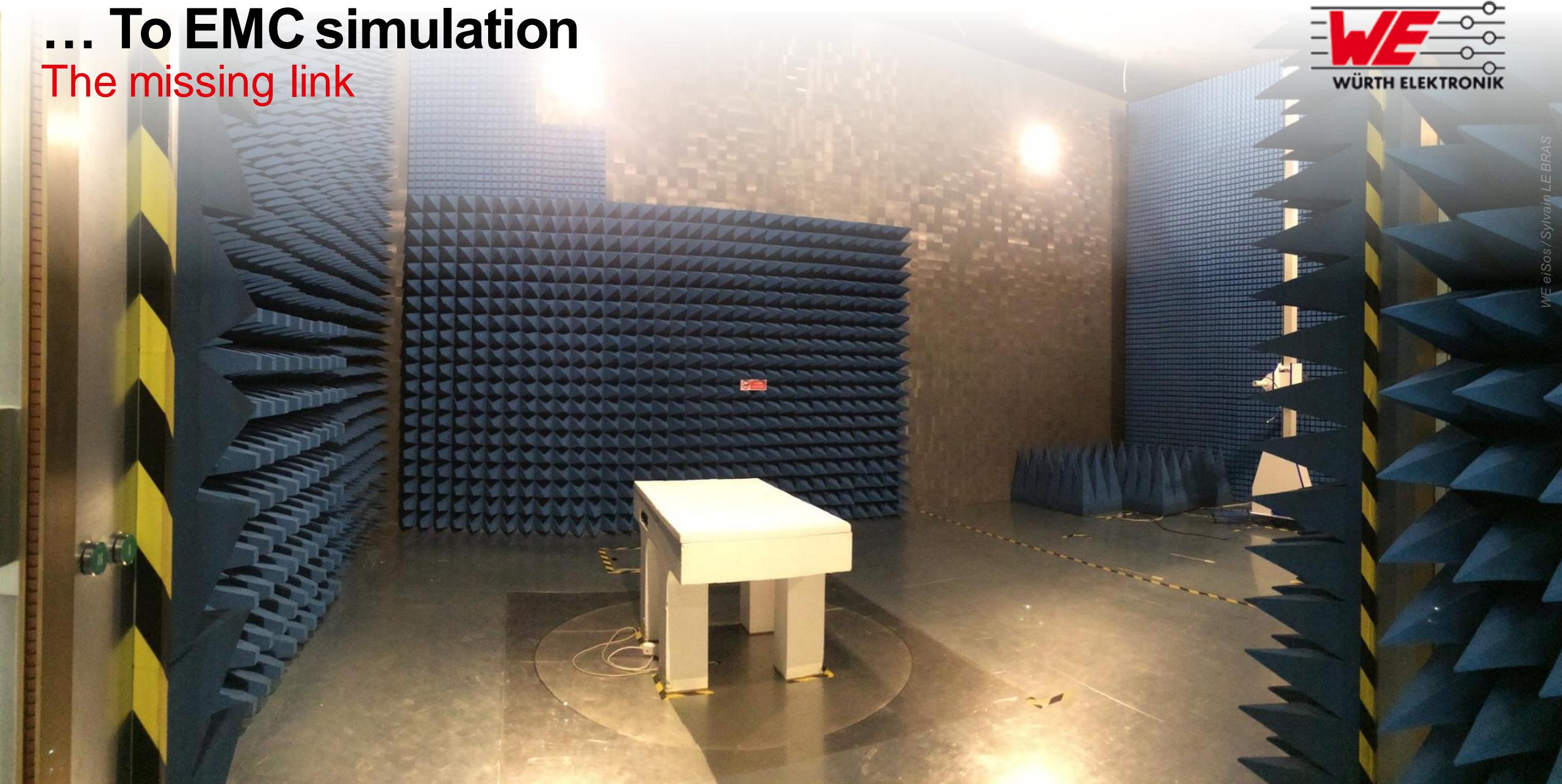


# Enabling EMC accurate measurement in LTSpice
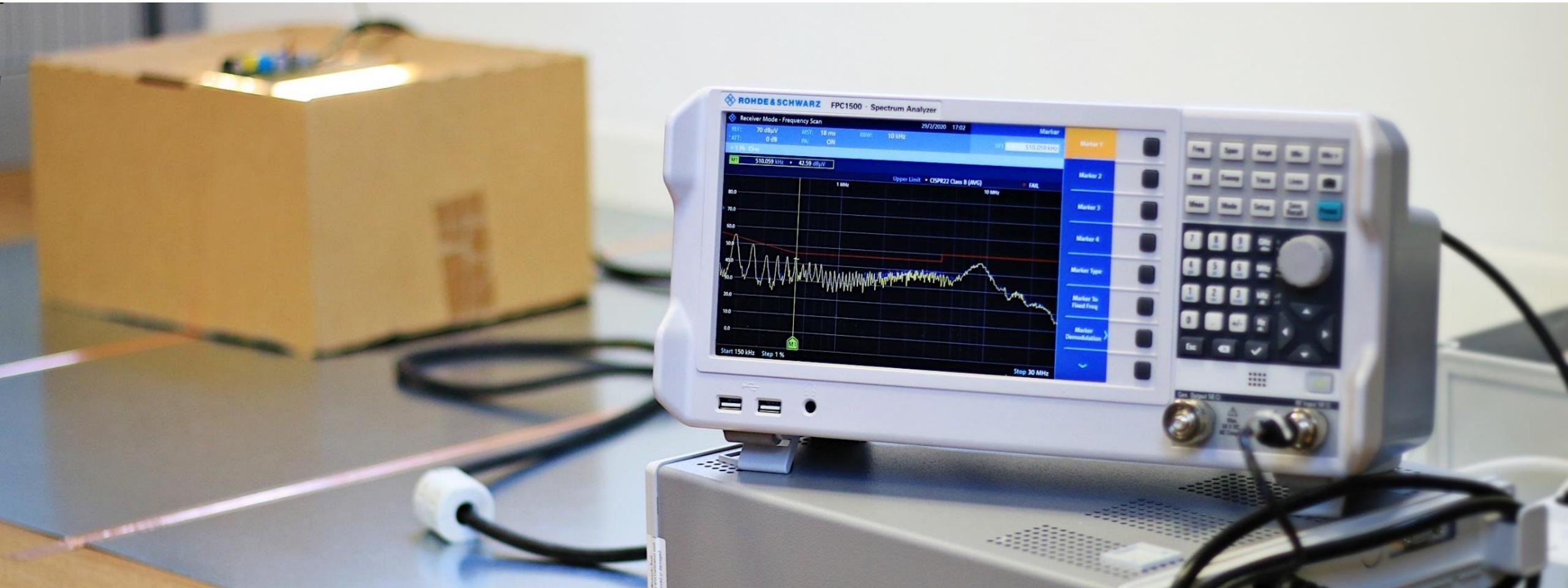
## What is the keystone of conducted emissions ?


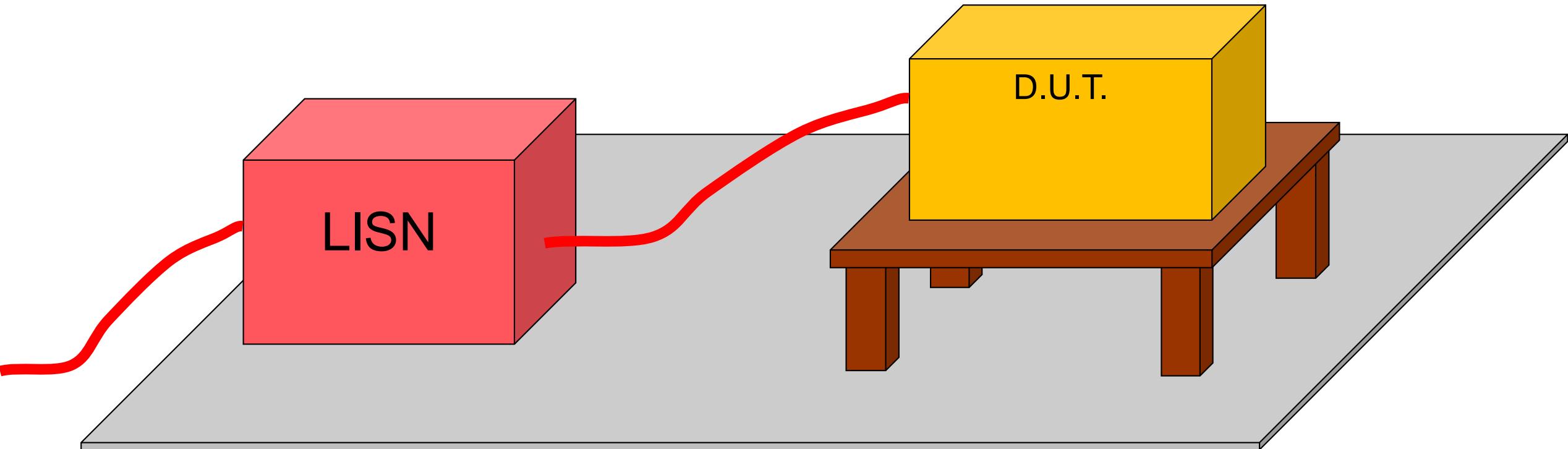
# Enabling EMC accurate measurement in LTSpice

What is the keystone of conducted emissions ?




# Enabling EMC accurate measurement in LTSpice

What is the keystone of conducted emissions ?



- ▶ Low Frequency
- ▶ High Frequency

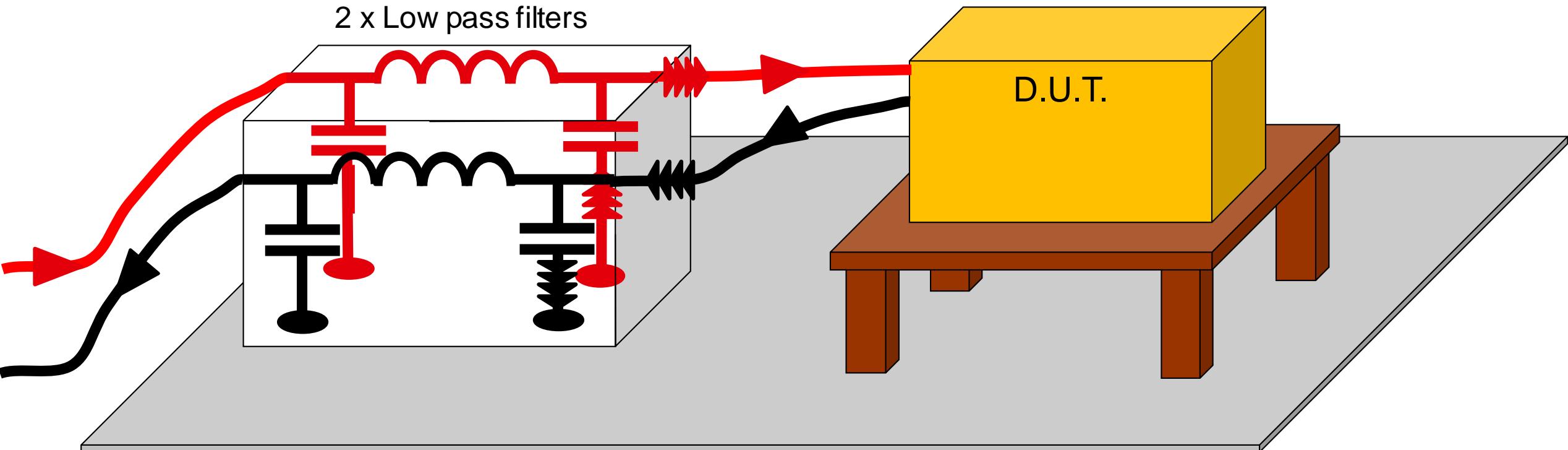


# Enabling EMC accurate measurement in LTSpice

What is the keystone of conducted emissions ?




- ▶ Low Frequency
- ▶ High Frequency

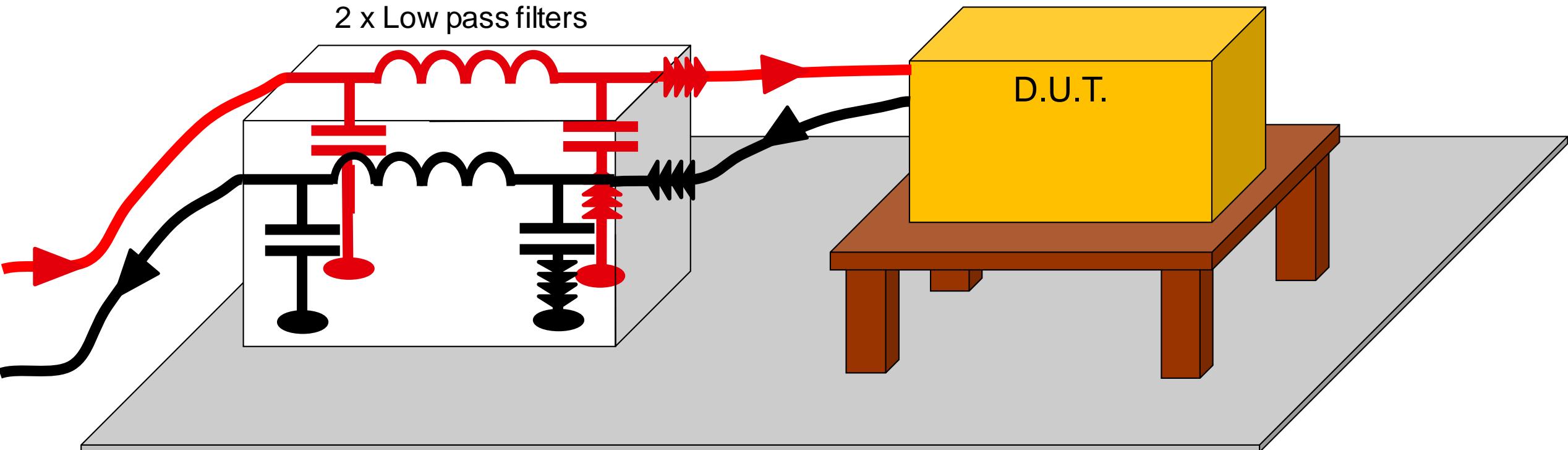

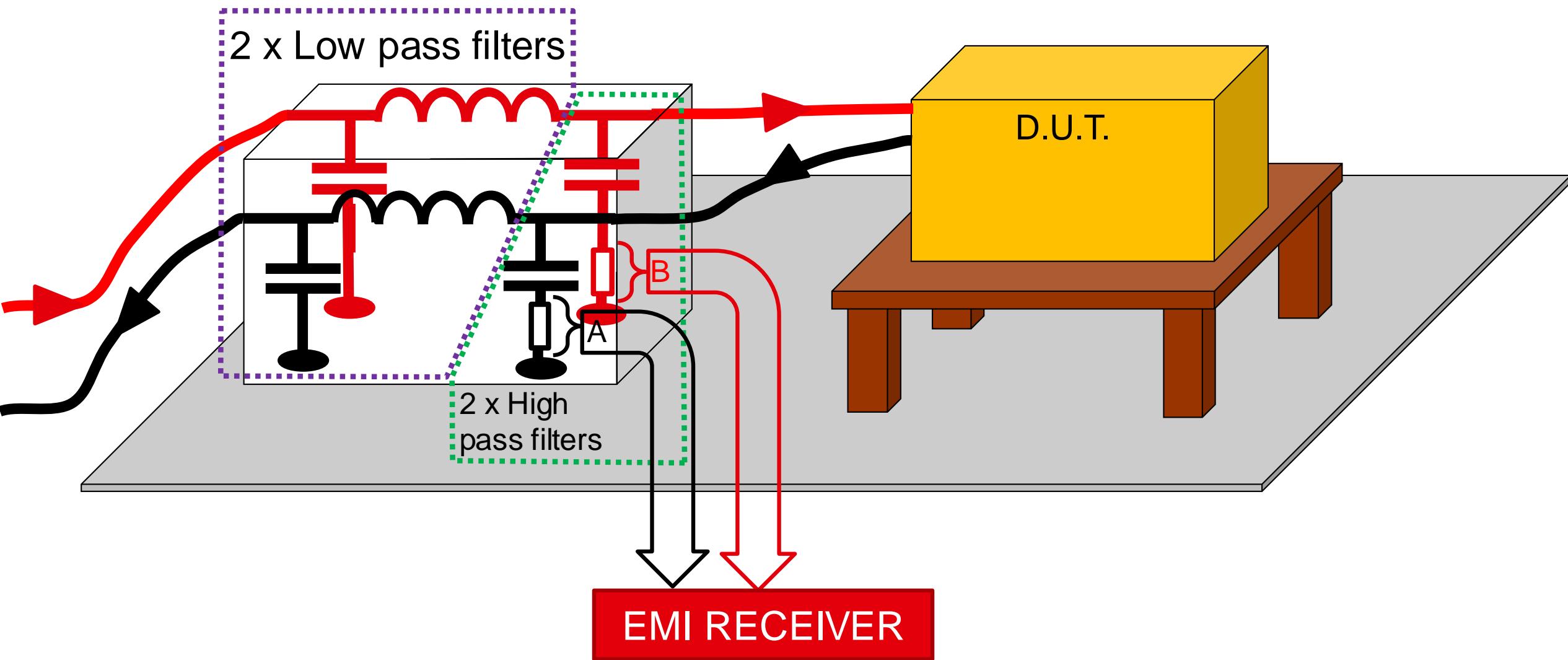
# Enabling EMC accurate measurement in LTSpice

What is the keystone of conducted emissions ?




# Enabling EMC accurate measurement in LTSpice

## FFT with simplified LISN

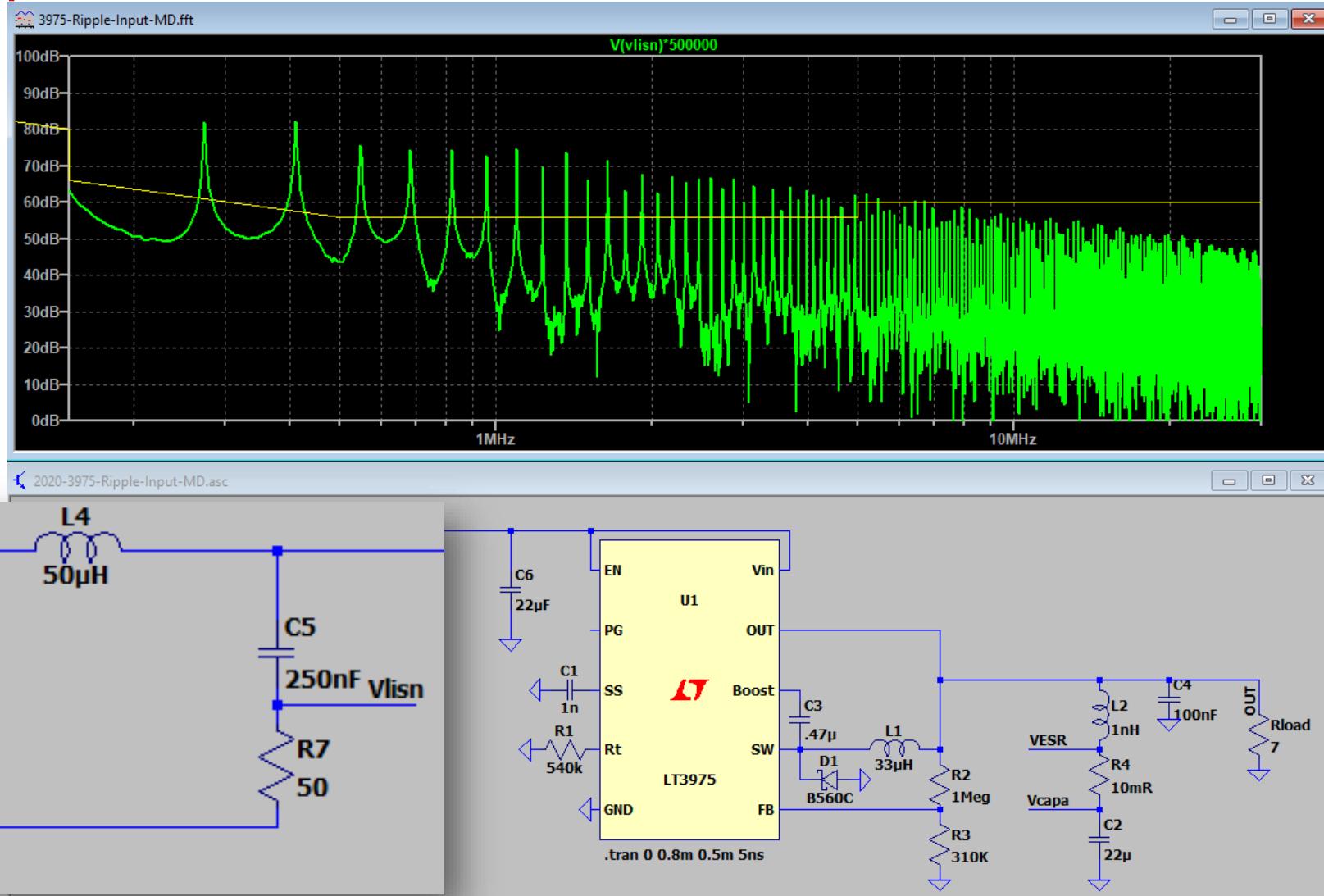

# Reality VS Simulation

## FFT with simplified LISN

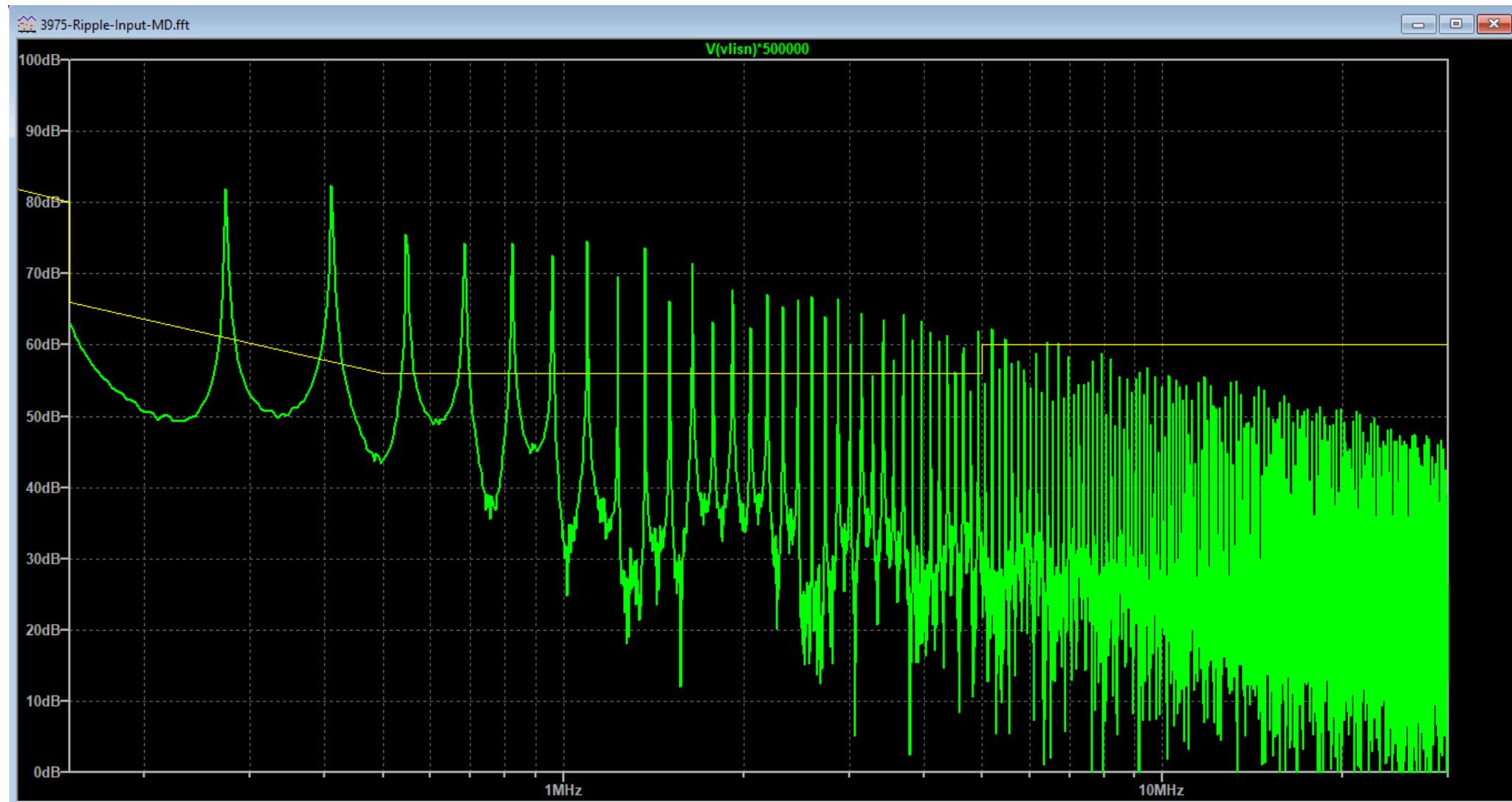



# Reality VS Simulation

## Conducted Emissions measurement




# Reality VS Simulation

## Conducted Emissions measurement



# Reality VS Simulation
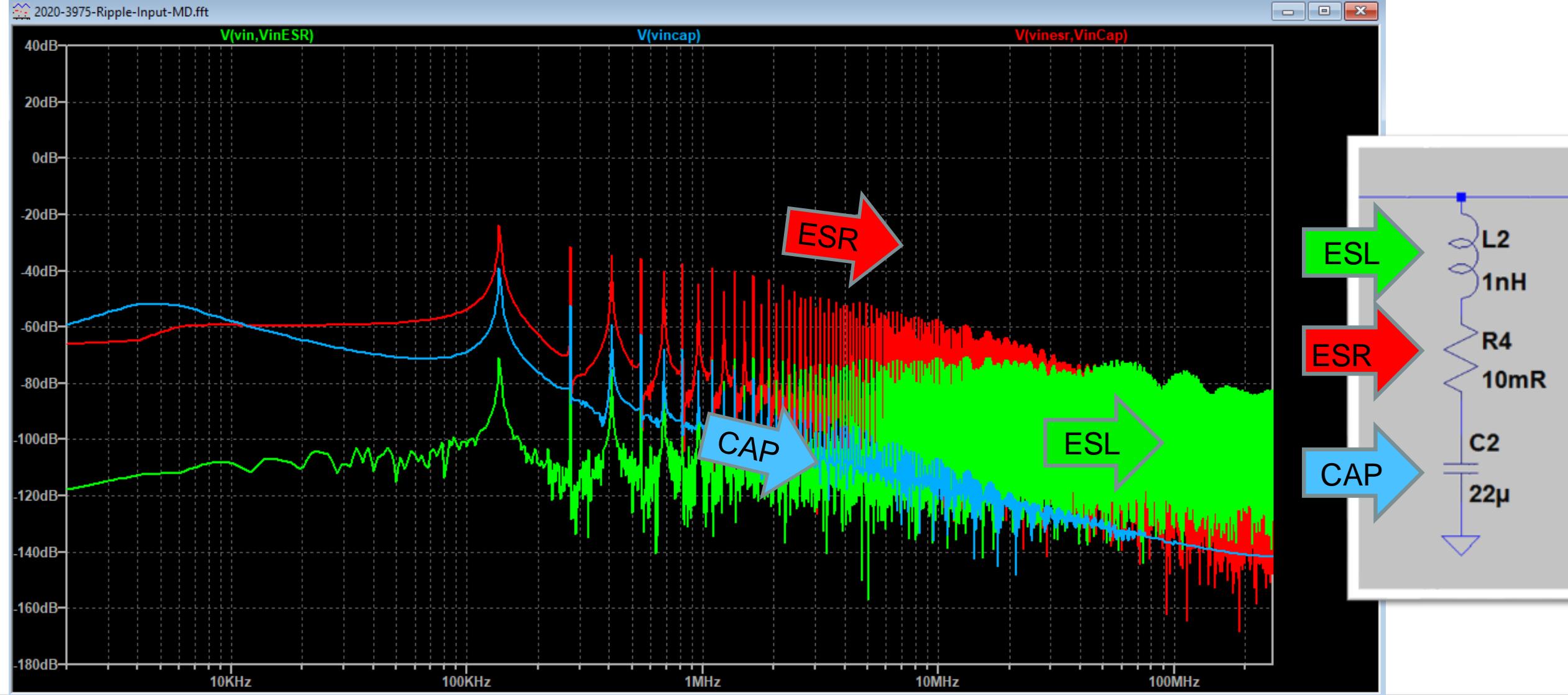
## ESR / ESL / CAP breakdown in frequency



# Reality VS Simulation




EMI measurement =  $\sum$  (Common Mode + Differential Mode)




# ... To EMC simulation

## Getting Seriously Accurate ?

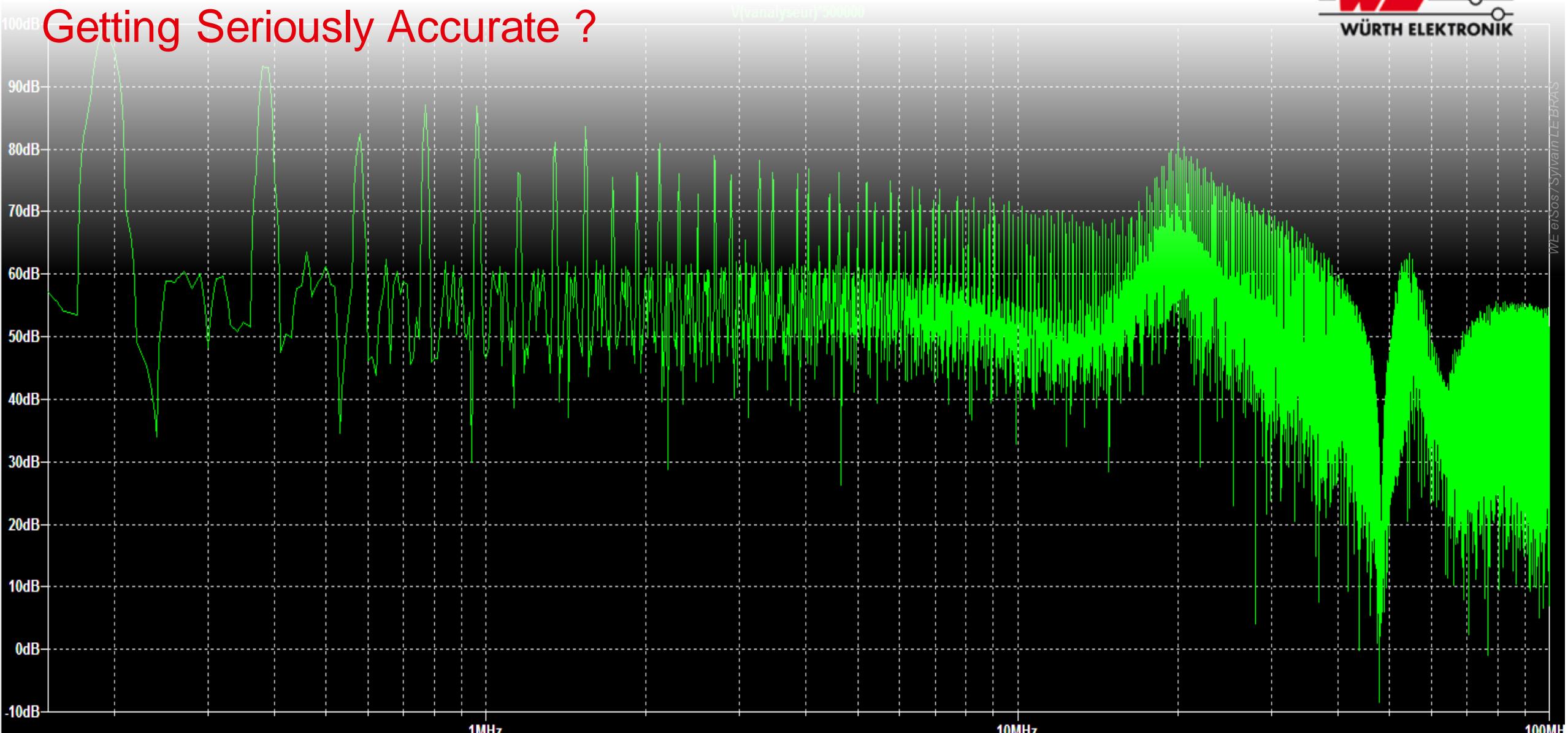


# Getting Seriously Accurate ?

## Actual LISN design

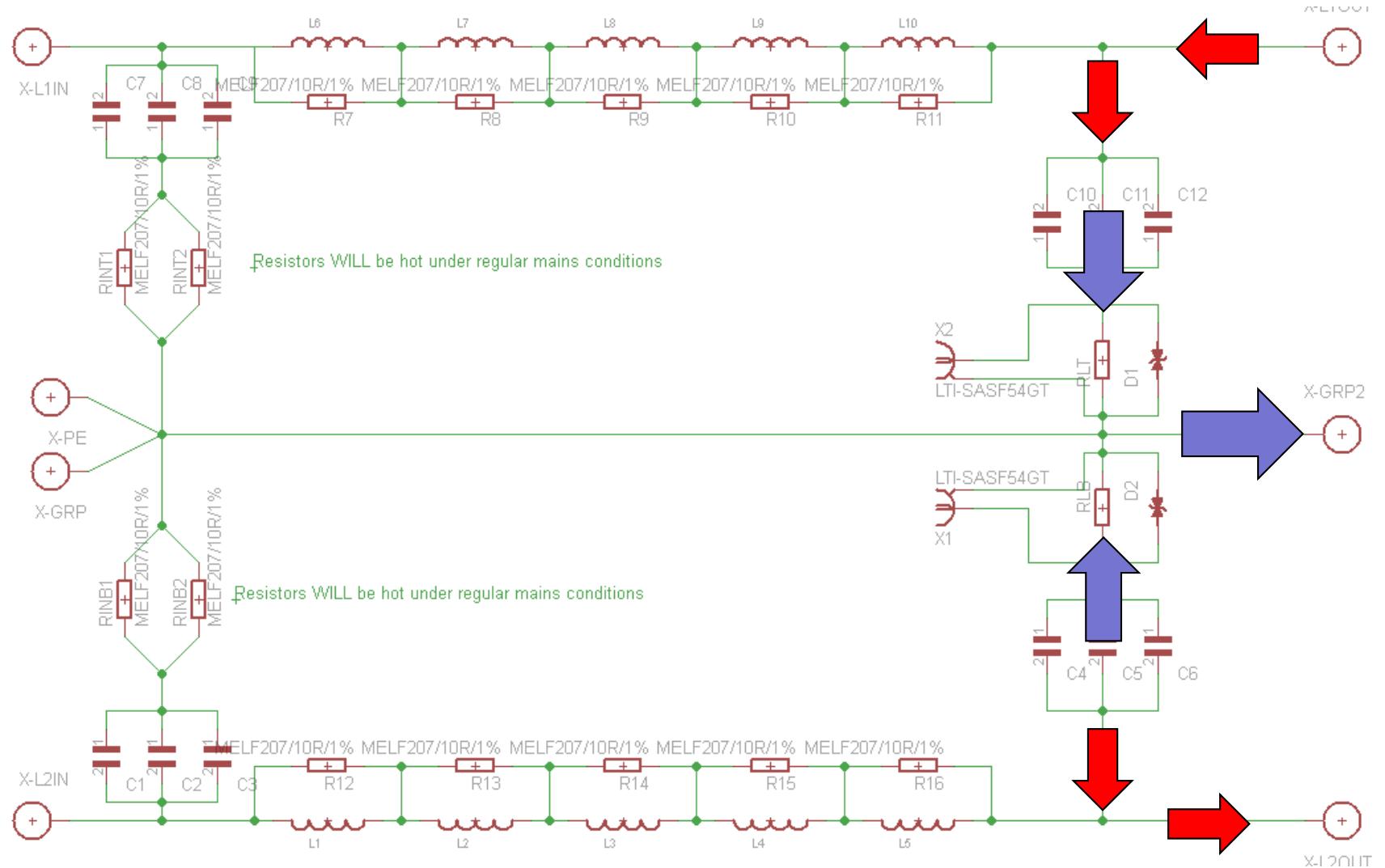


# Getting Seriously Accurate ?

Actual LISN design

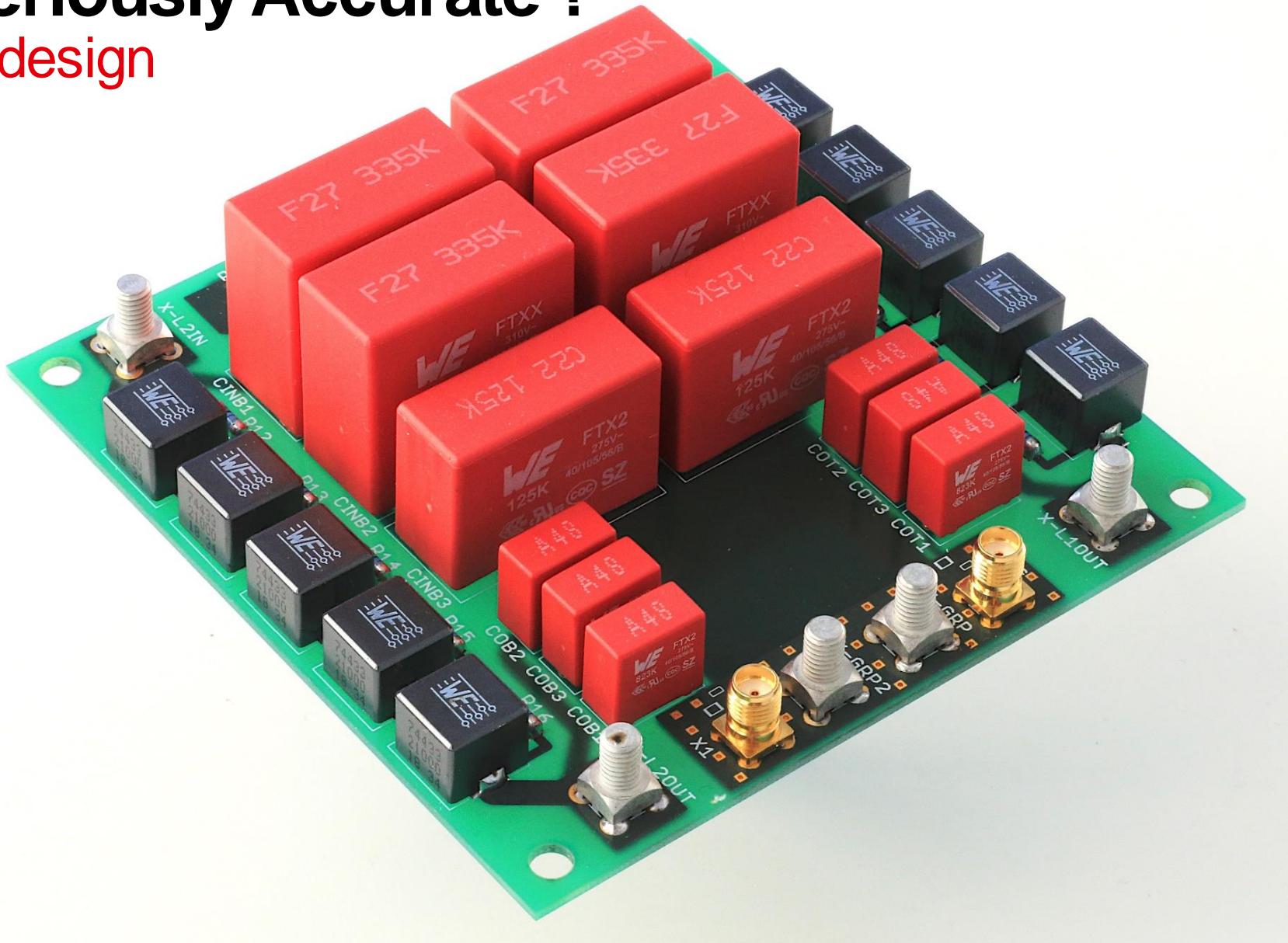


# Getting Seriously Accurate ?

## Simulation Ready LISN design

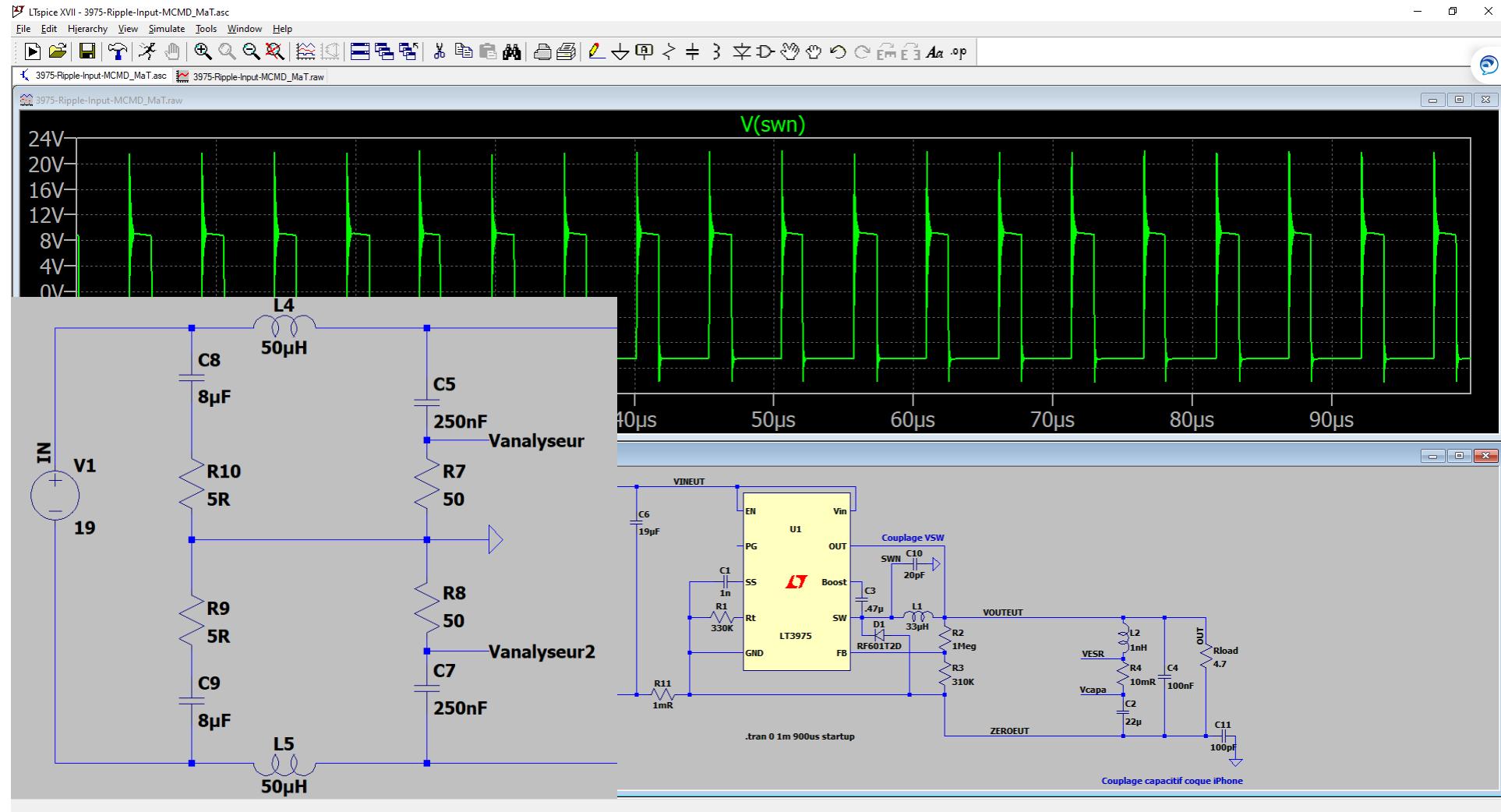


# Getting Seriously Accurate ?

## Adding E-Field parasitic coupling

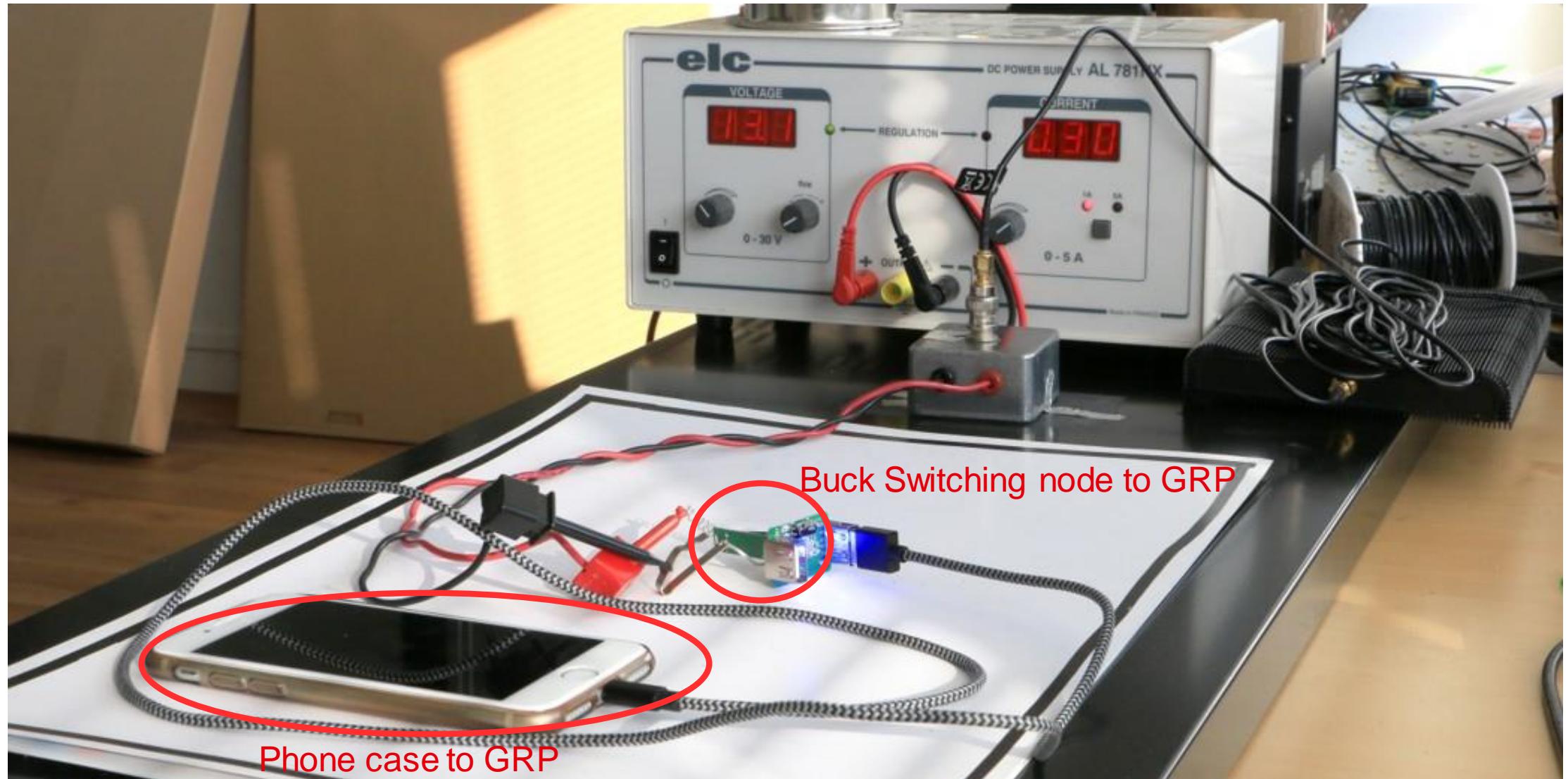

# Getting Seriously Accurate ?

Adding E-Field parasitic coupling

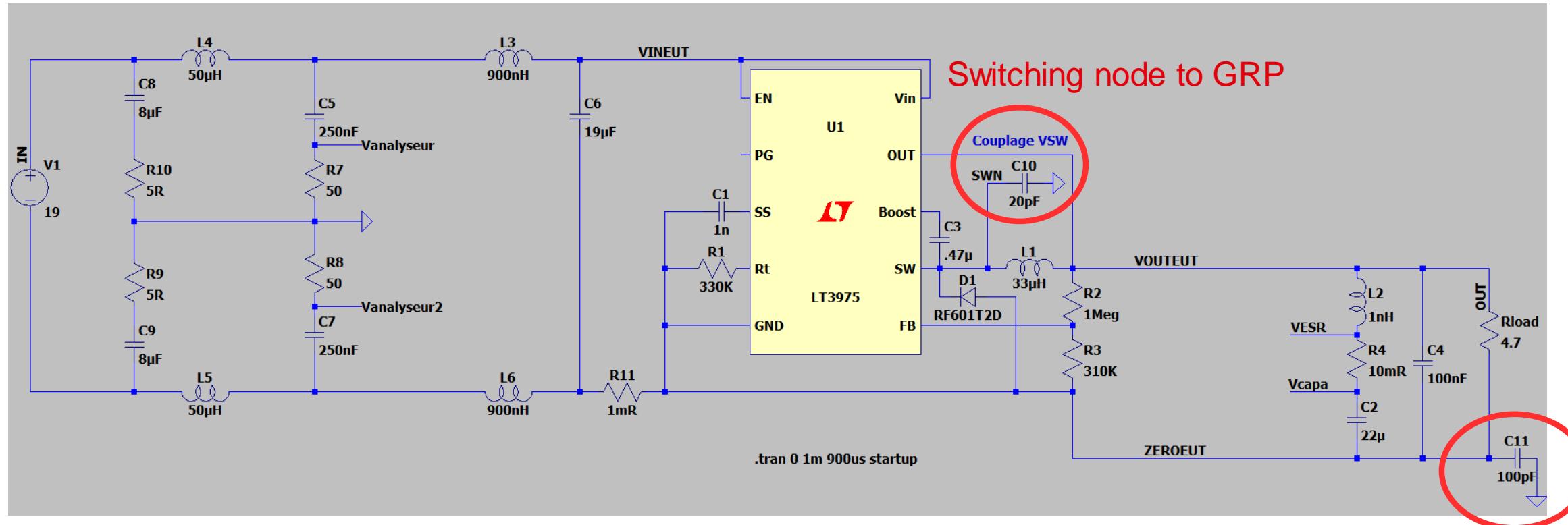

# Getting Seriously Accurate ?



## Reality VS Simulation


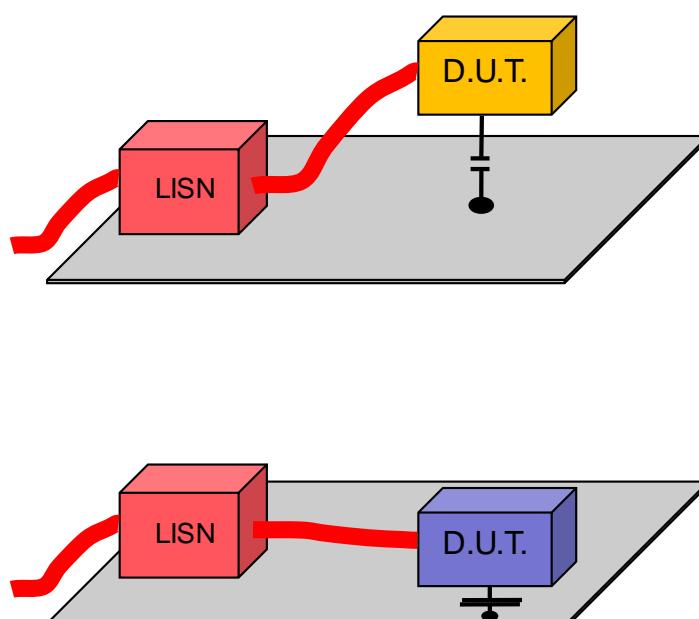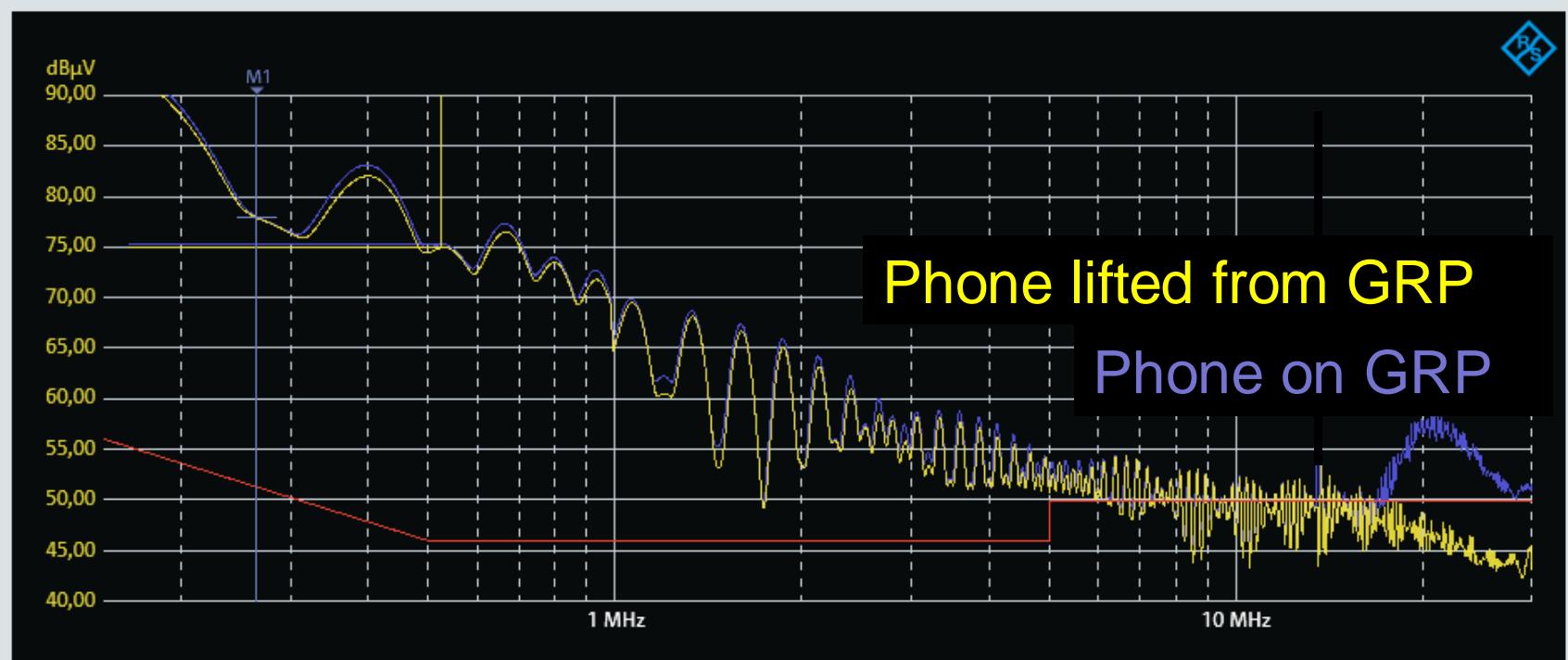
### Frequency Scan


Ref Level 80 dB $\mu$ V  
 ■ RF Attenuator 10 dB  
 RBW 100 kHz  
 Start Frequency 150 kHz  
 Stop Frequency 30 MHz

Measurement Time 10 ms  
 Trace Mode Clear / Write  
 Trigger Mode Free Run  
 Trace Detector Average  
 Scan step 0,5 %




# Getting Seriously Accurate ?

## Reality VS Simulation

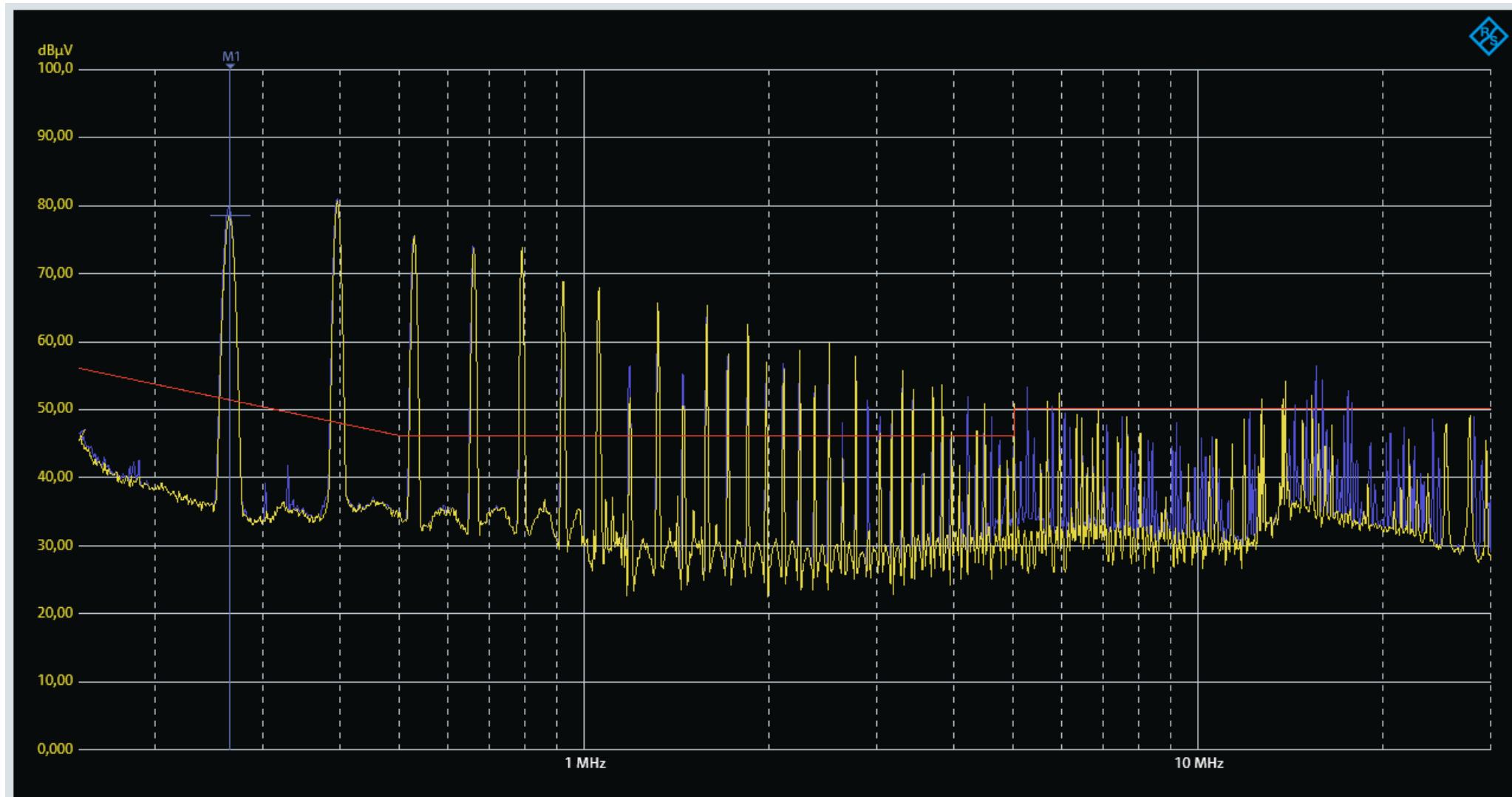


# Getting Seriously Accurate ?

## Reality VS Simulation

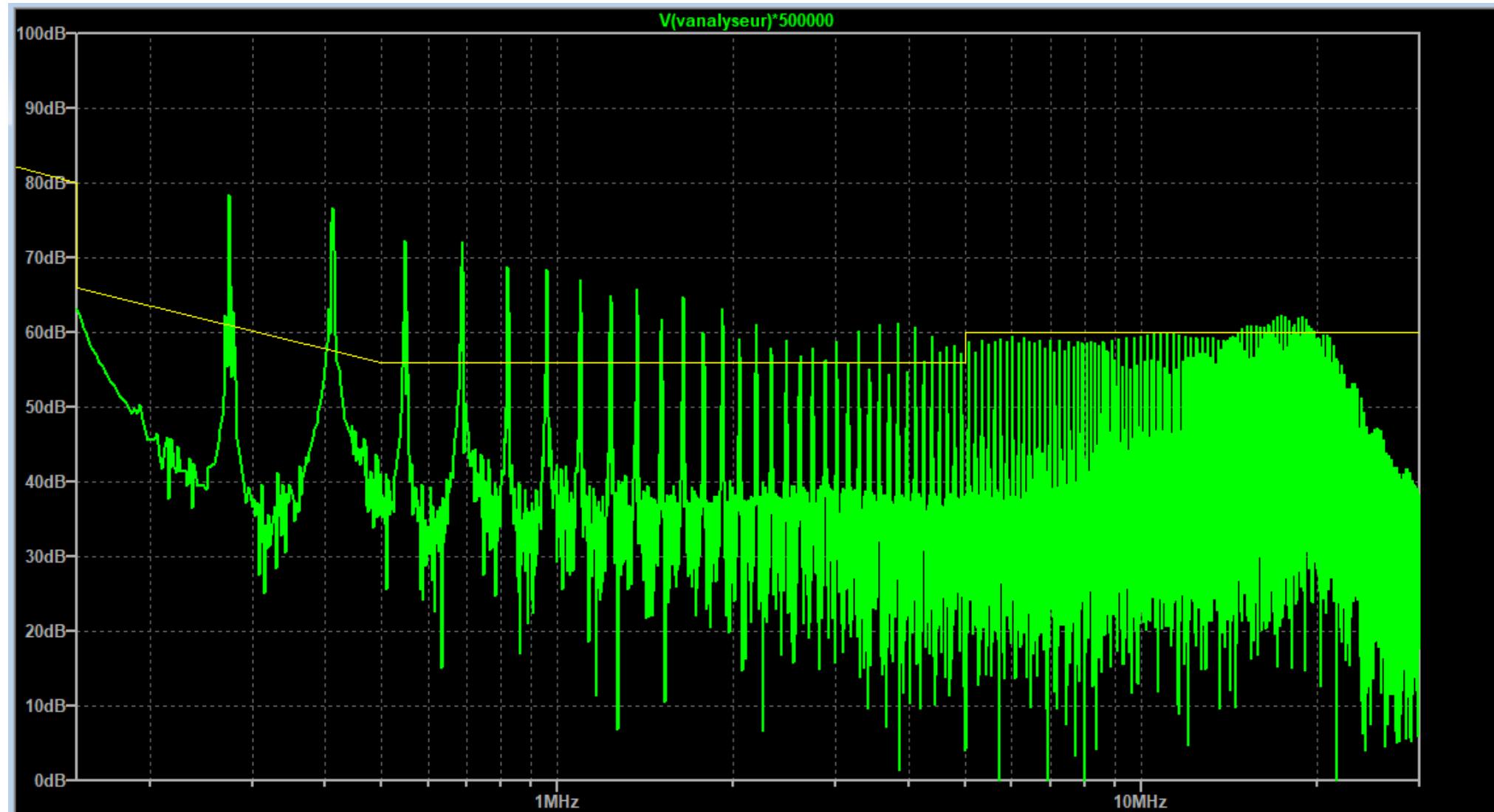


# Getting Seriously Accurate ?

Reality VS Simulation

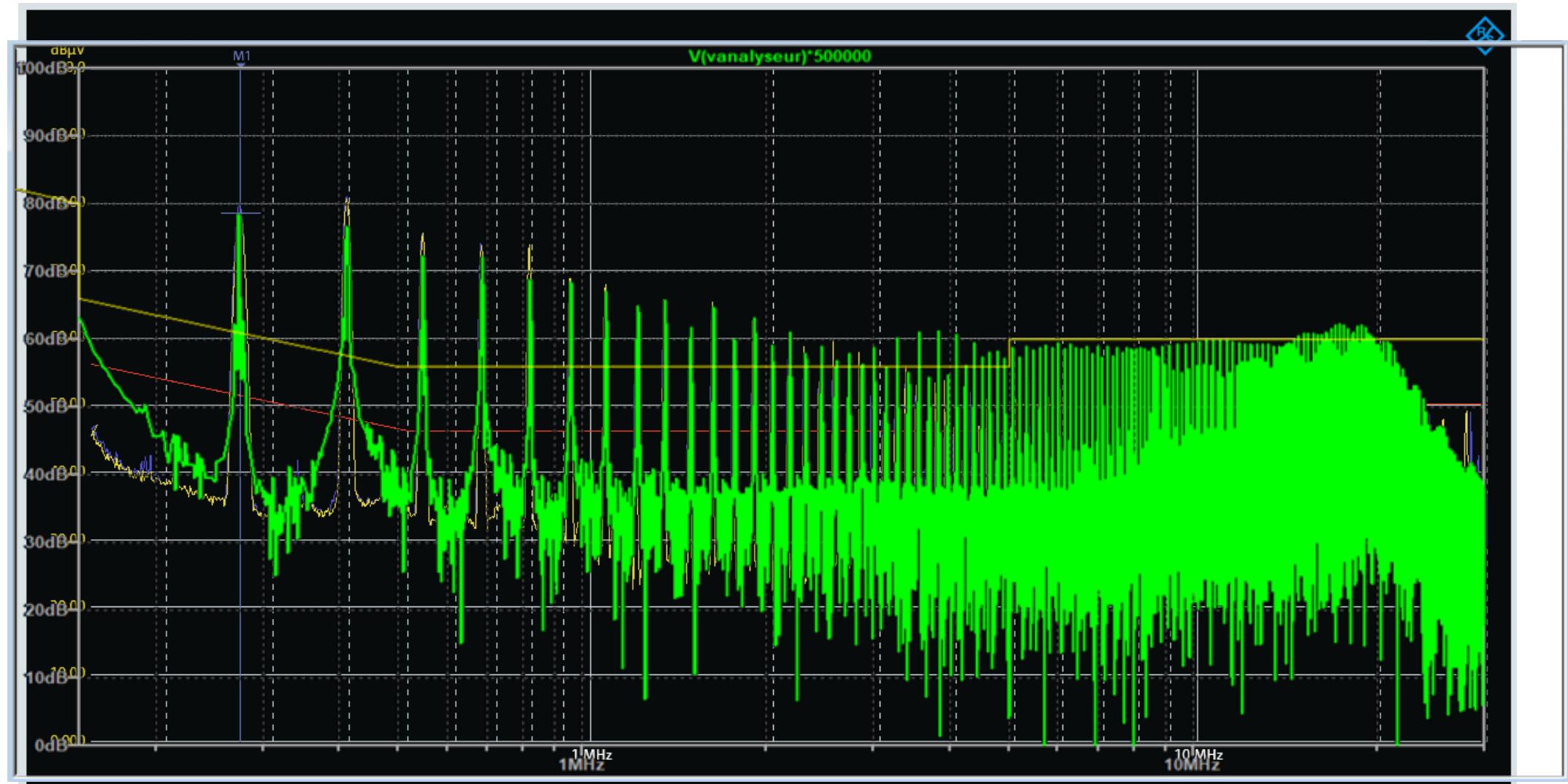

# Going further with simulation


Splitting CM and DM

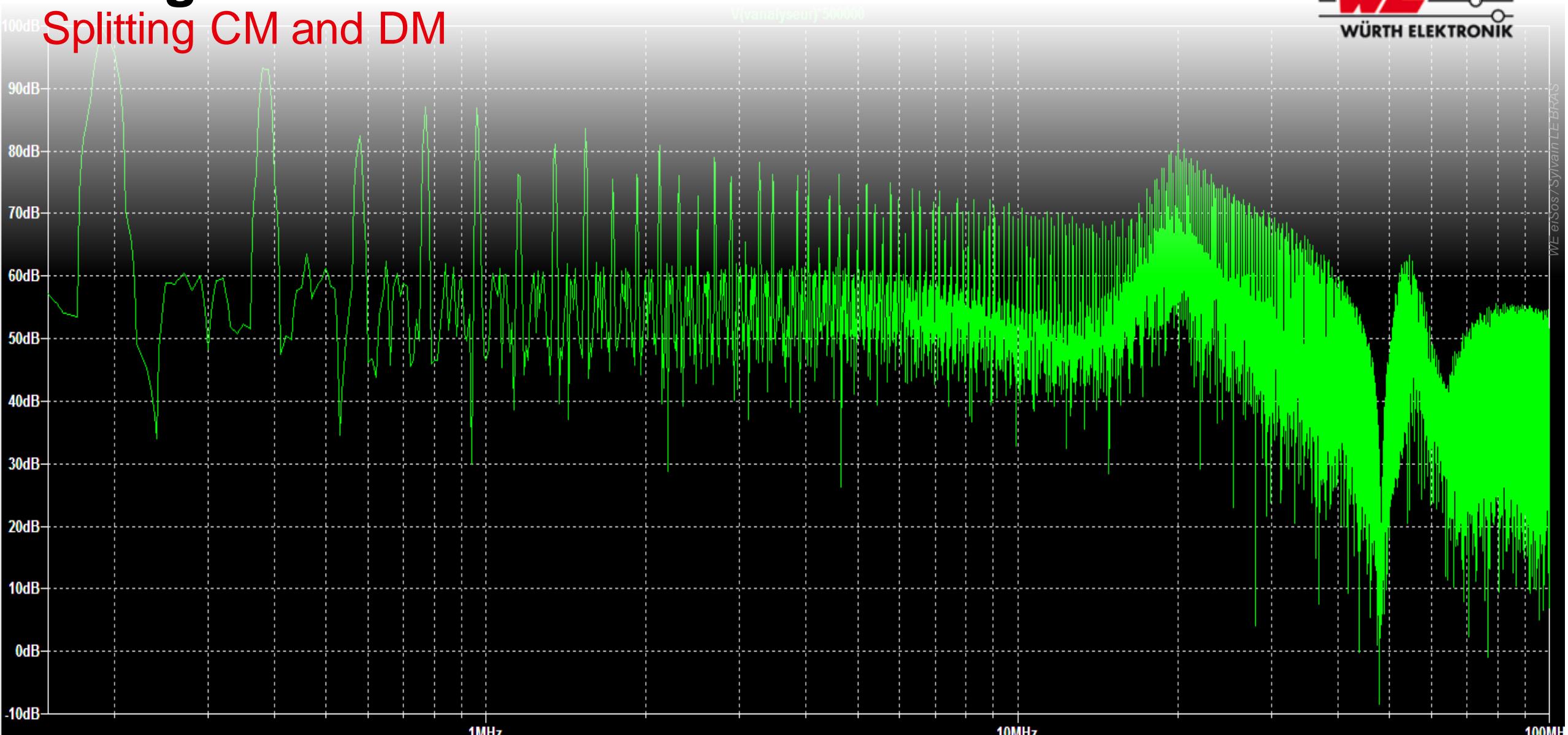

# Going further with simulation

## Splitting CM and DM


- Symetrical interference ?

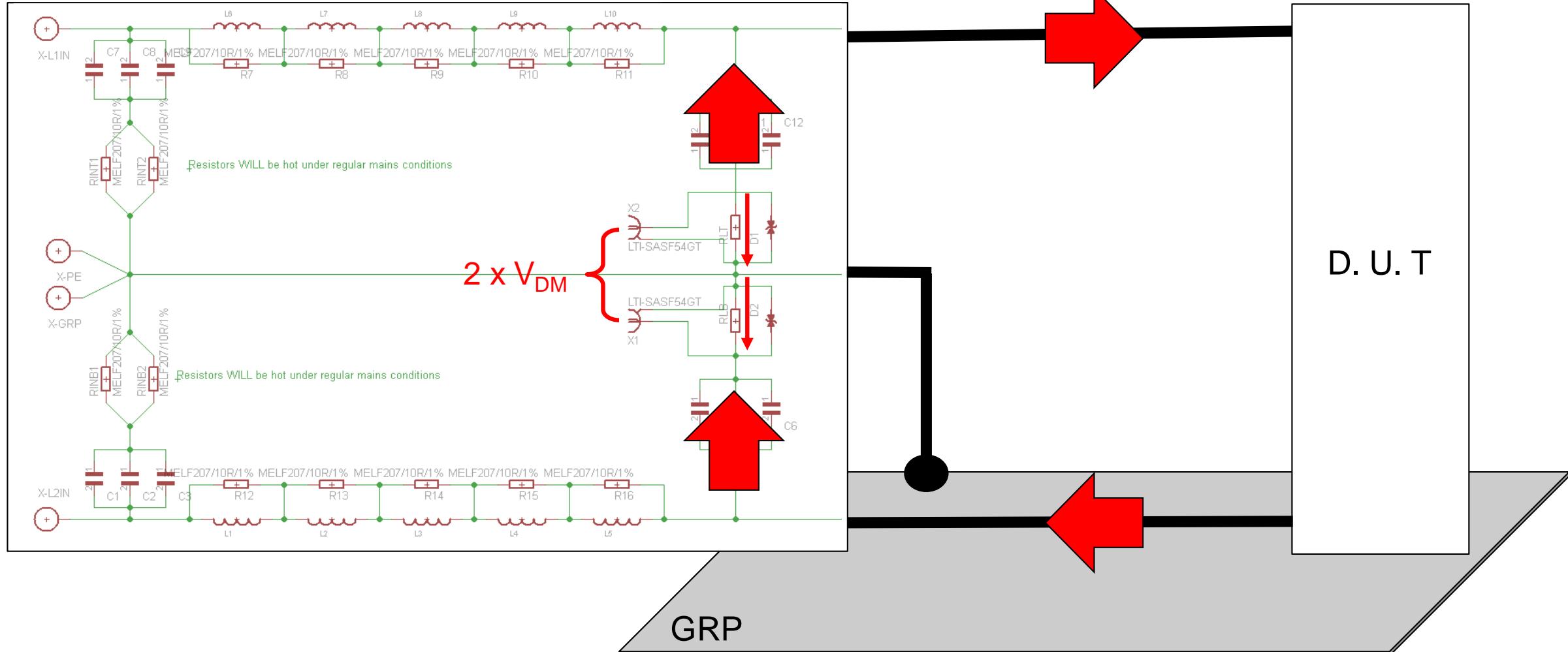

# Going further with simulation

## Splitting CM and DM


- Asymmetrical interference ?

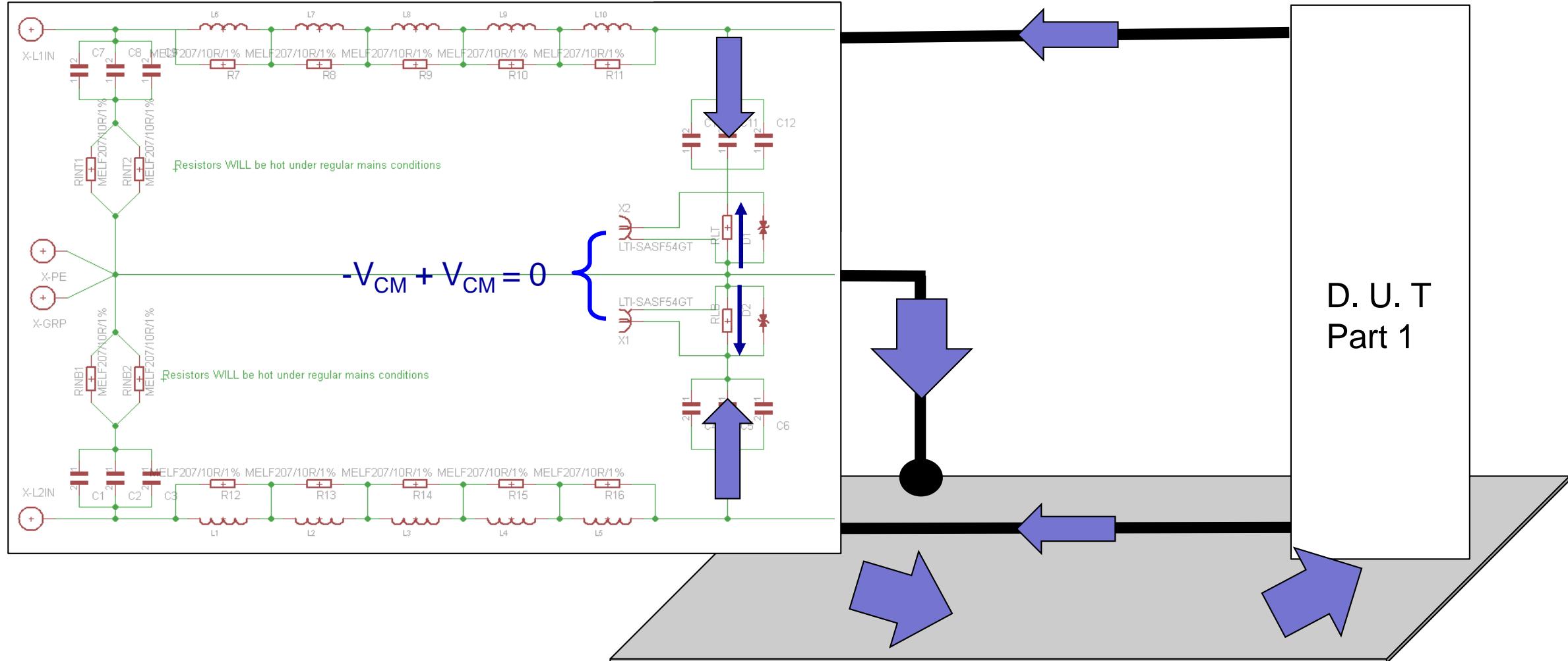

# Going further with simulation

## Splitting CM and DM


- Asymmetrical interference ?

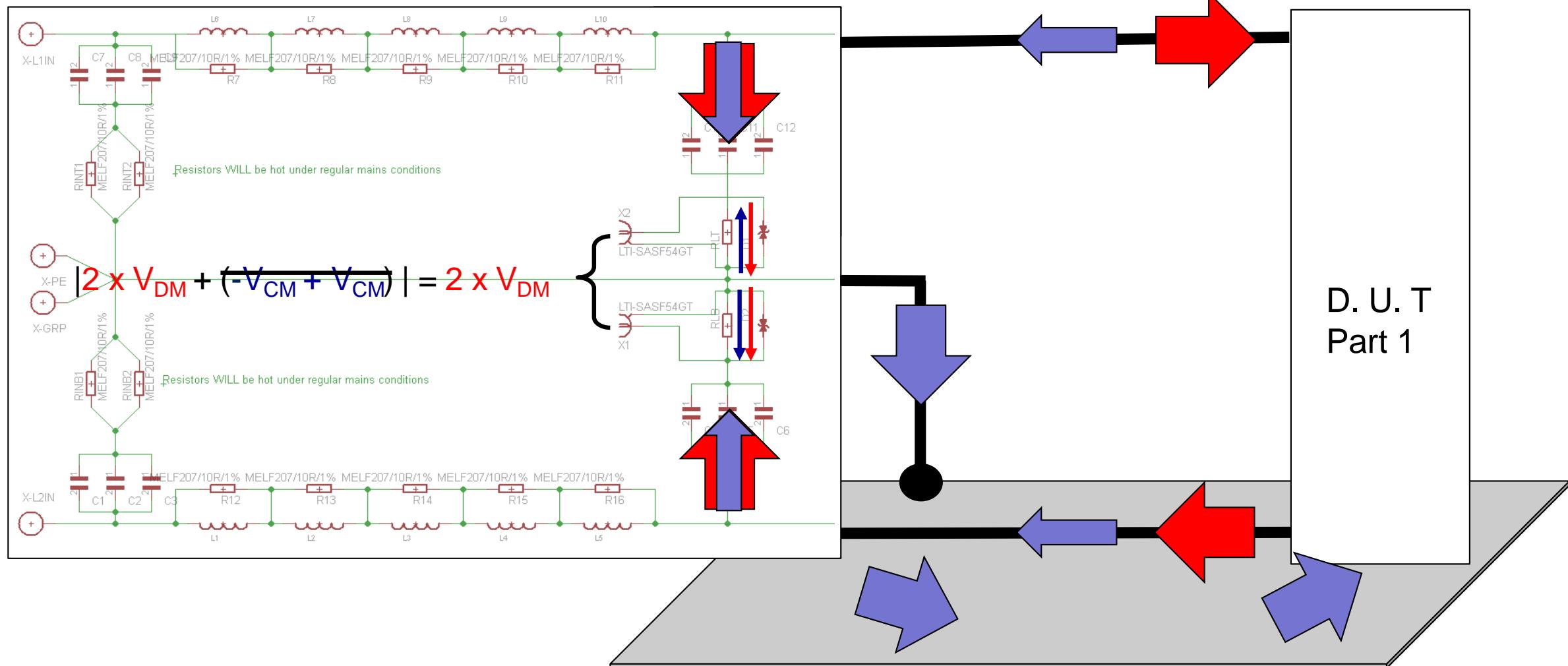

# Going further with simulation

## Splitting CM and DM


- Symetrical interference ?

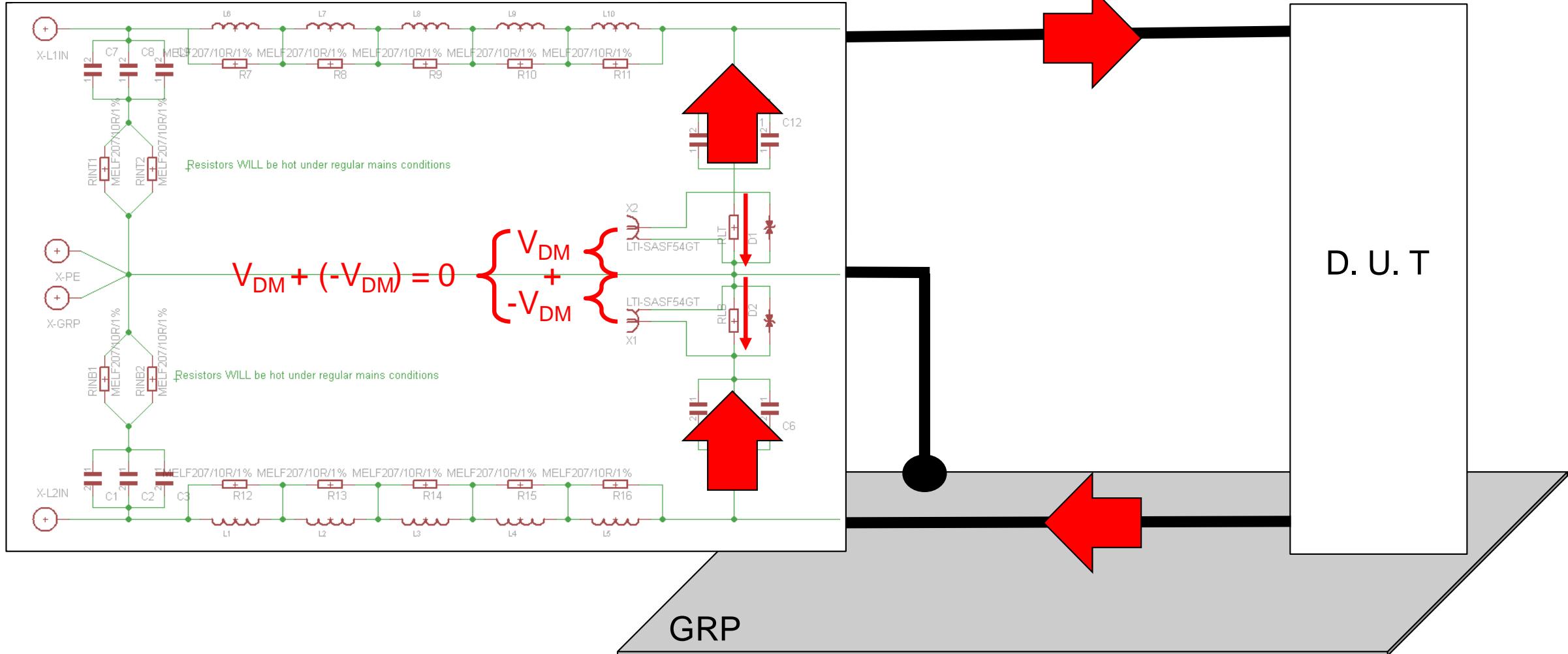

# Going further with simulation

## Splitting CM and DM


- Asymetrical interference ?

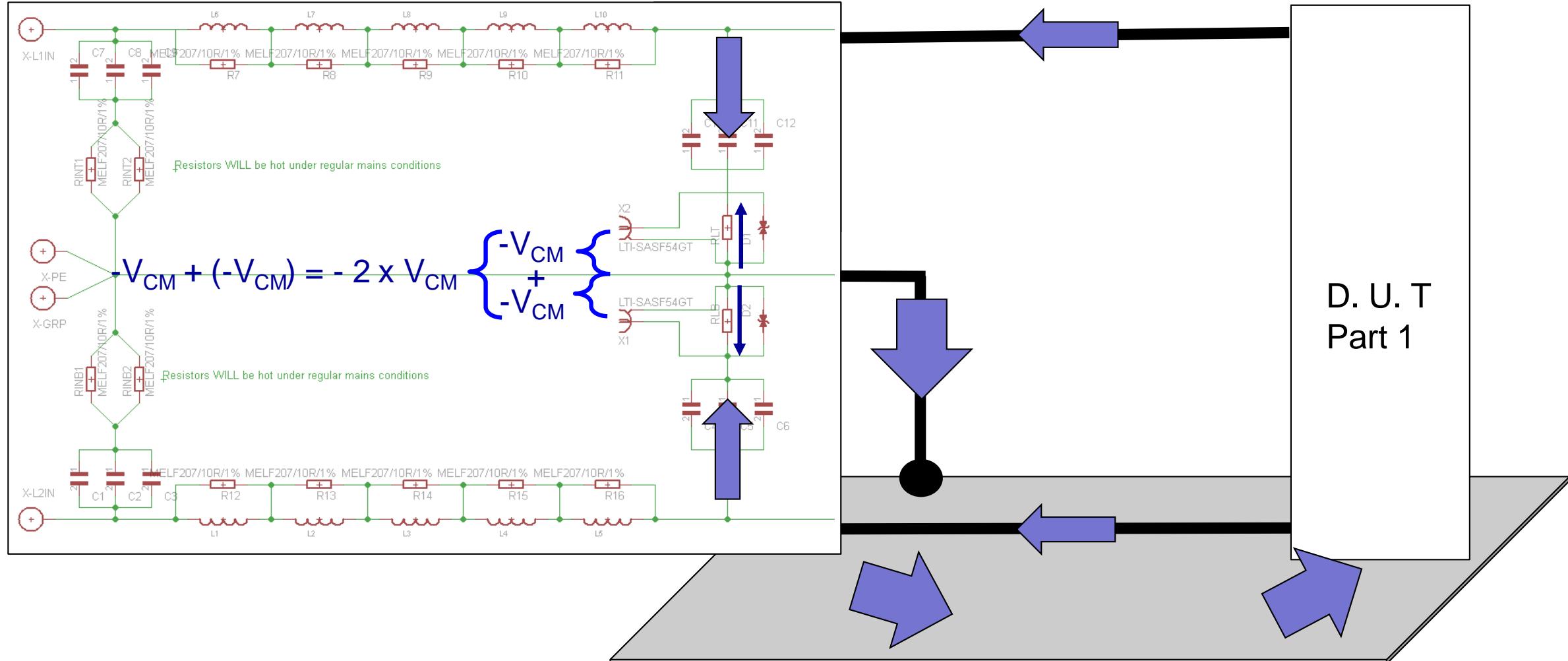

# Going further with simulation


## Splitting CM and DM

- Asymetrical interference ?

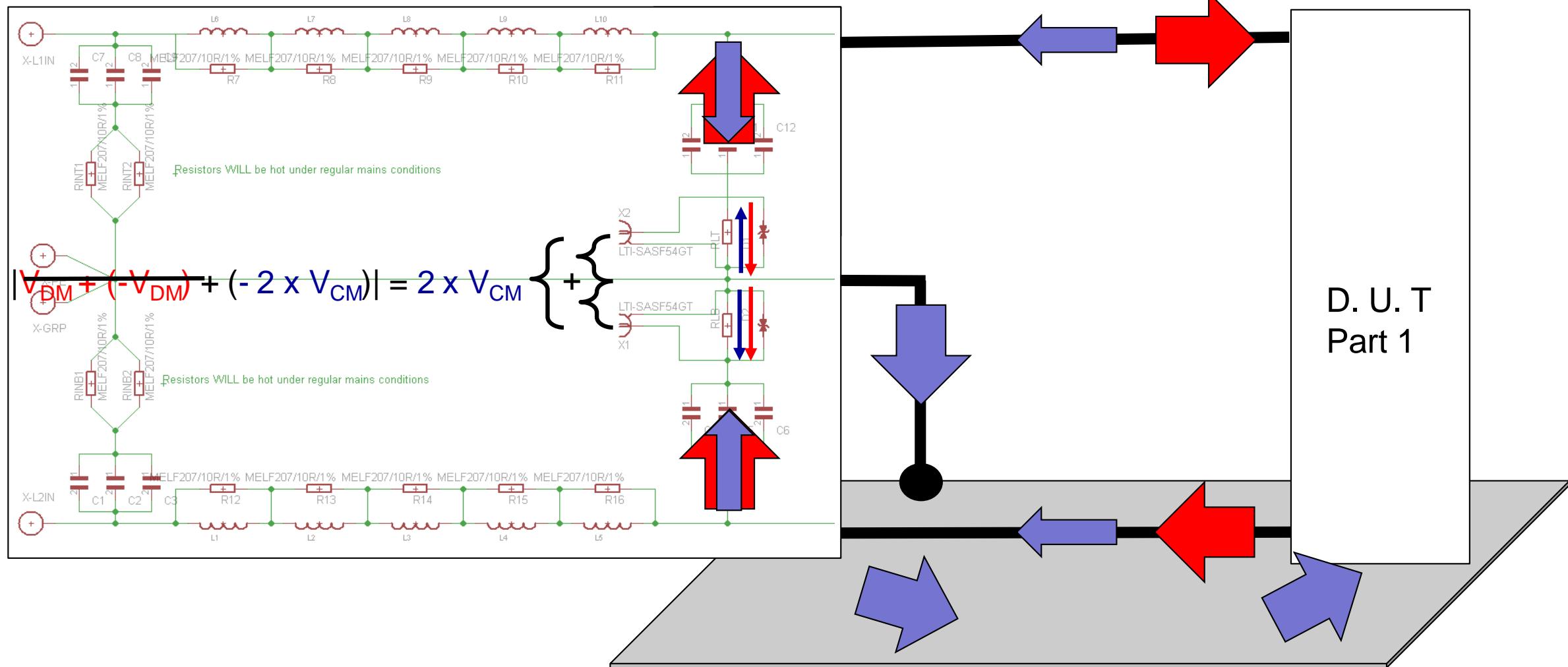



# Going further with simulation

## Splitting CM and DM

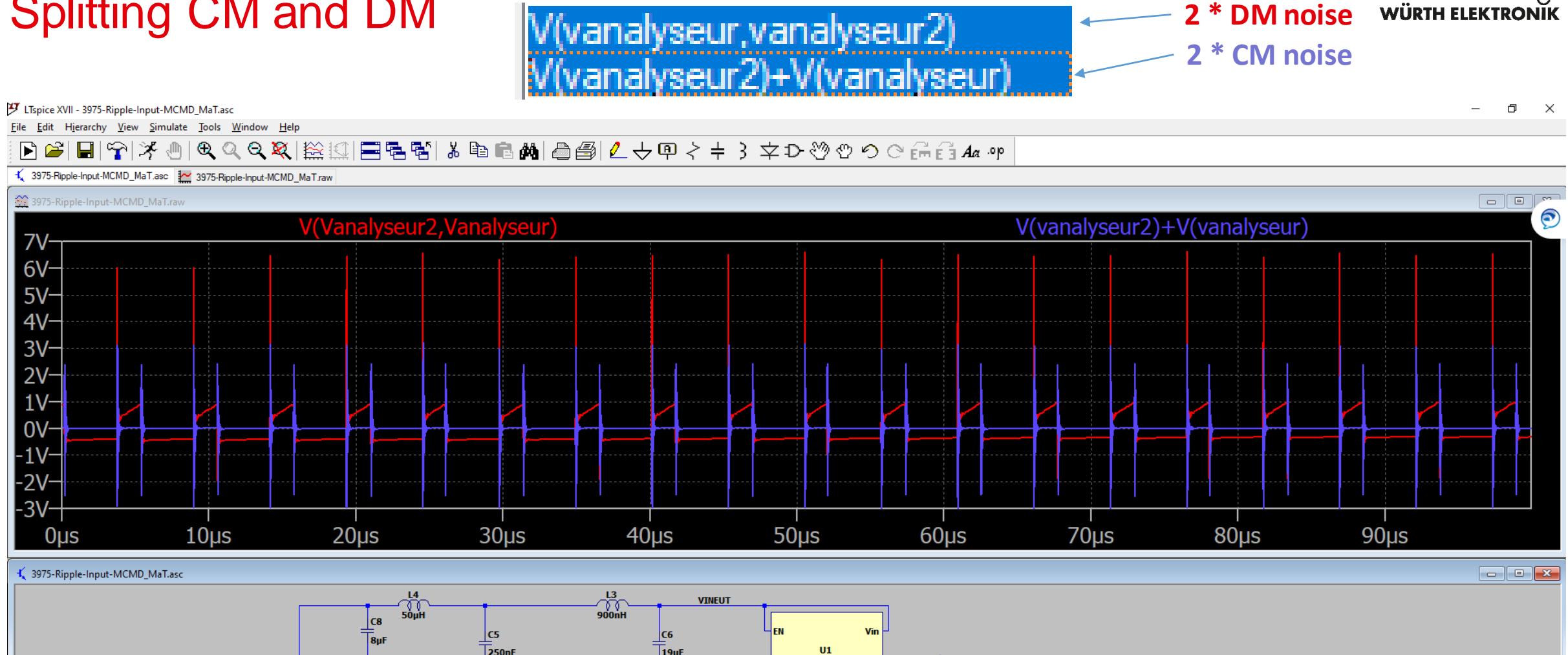


# Going further with simulation

## Splitting CM and DM

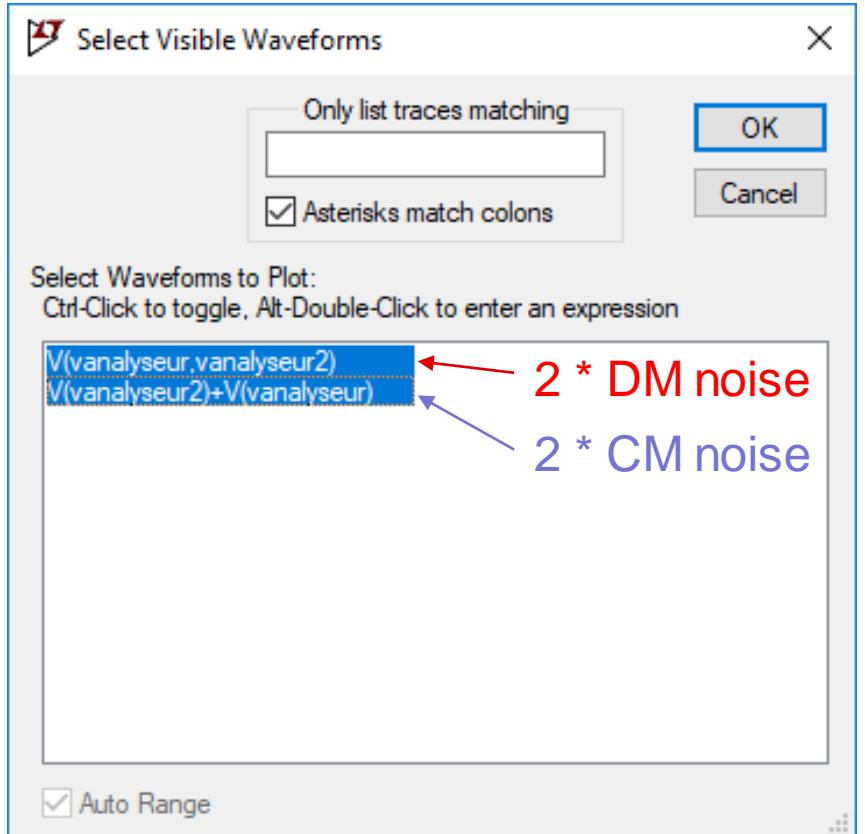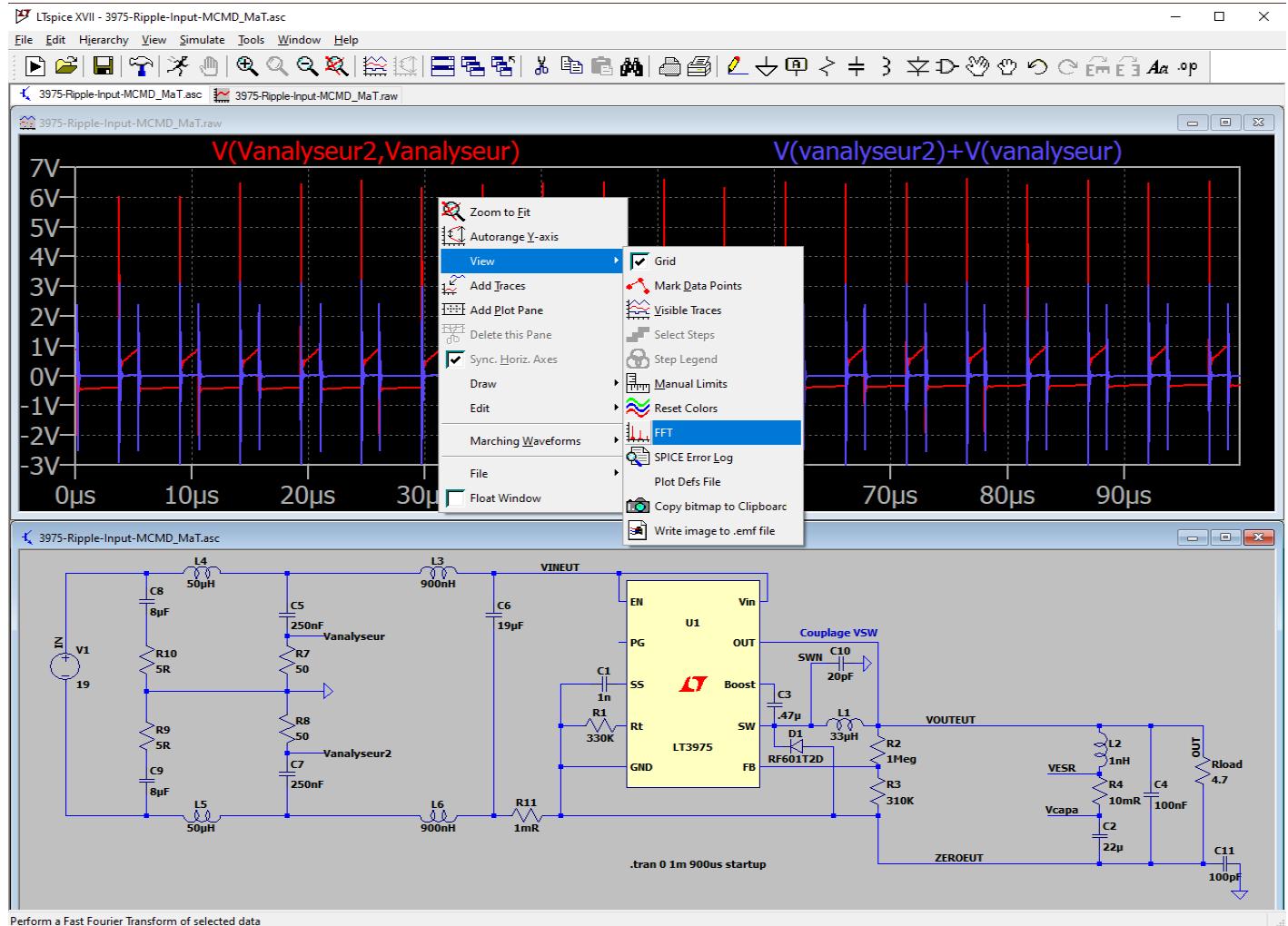

# Going further with simulation

## Splitting CM and DM

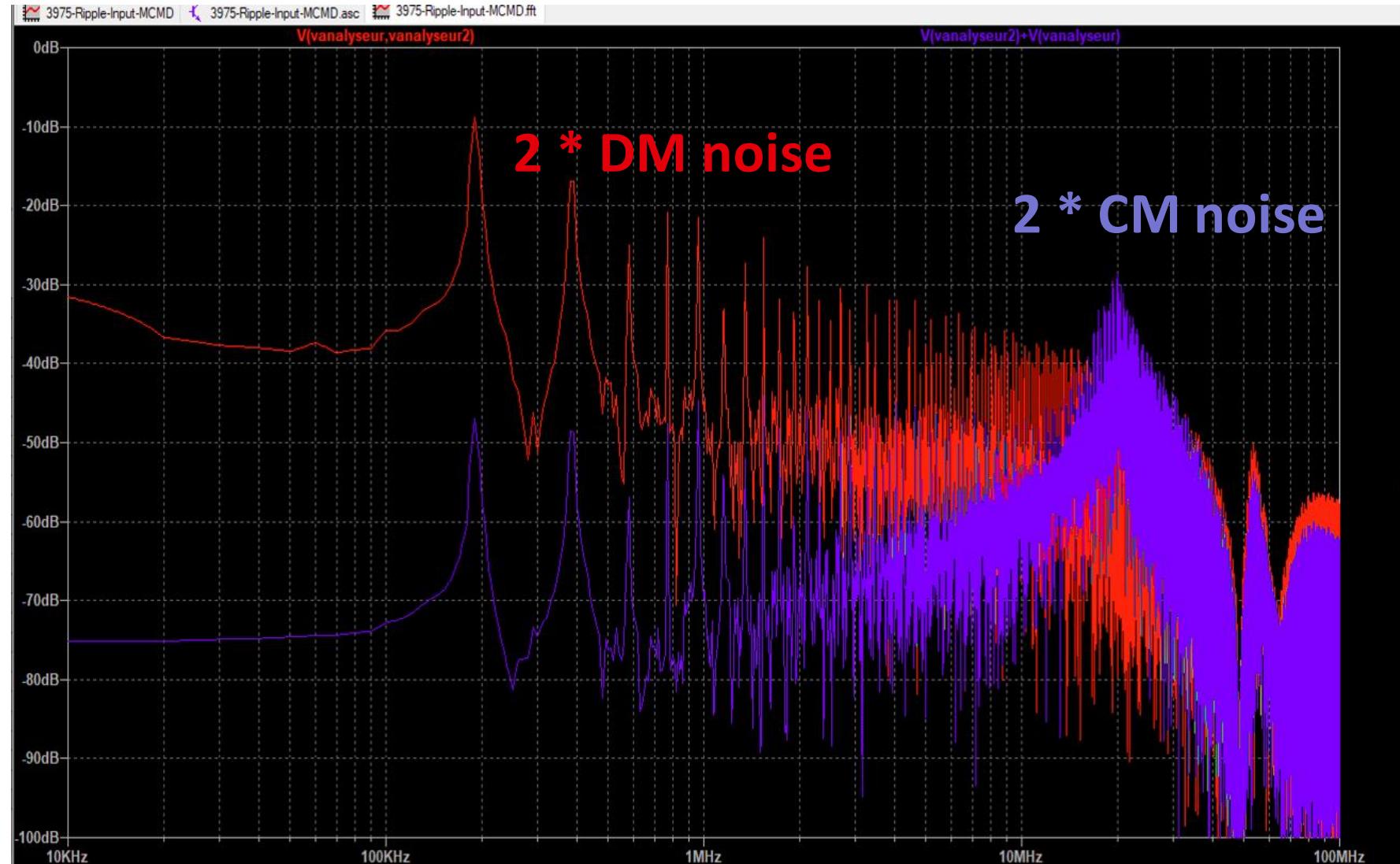


# Going further with simulation
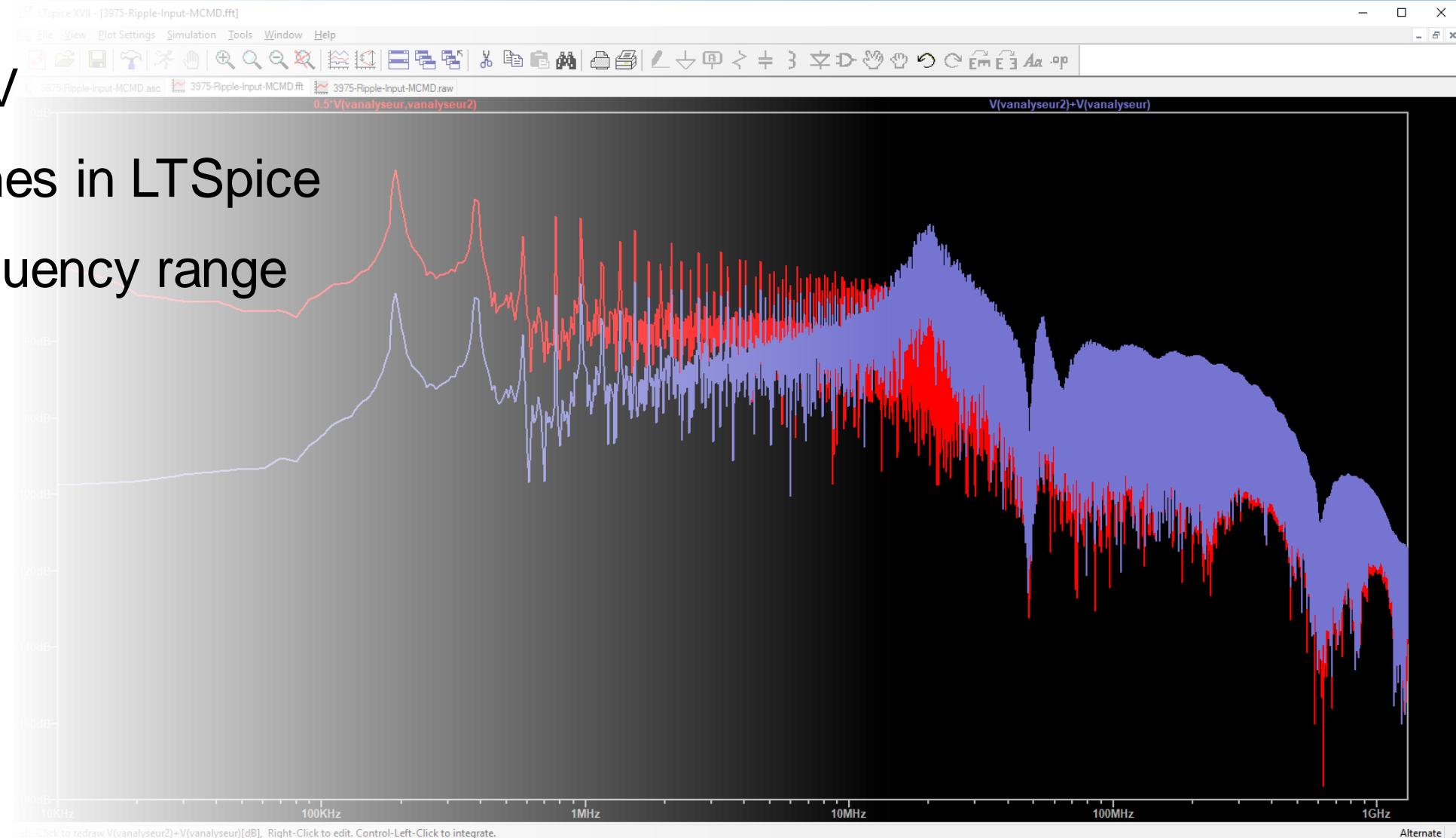
## Making simulation look real




- Scaling to dB $\mu$ V
- Loading limit lines in LTSpice
- Defining a Frequency range



# Going further with simulation


## Making simulation look real

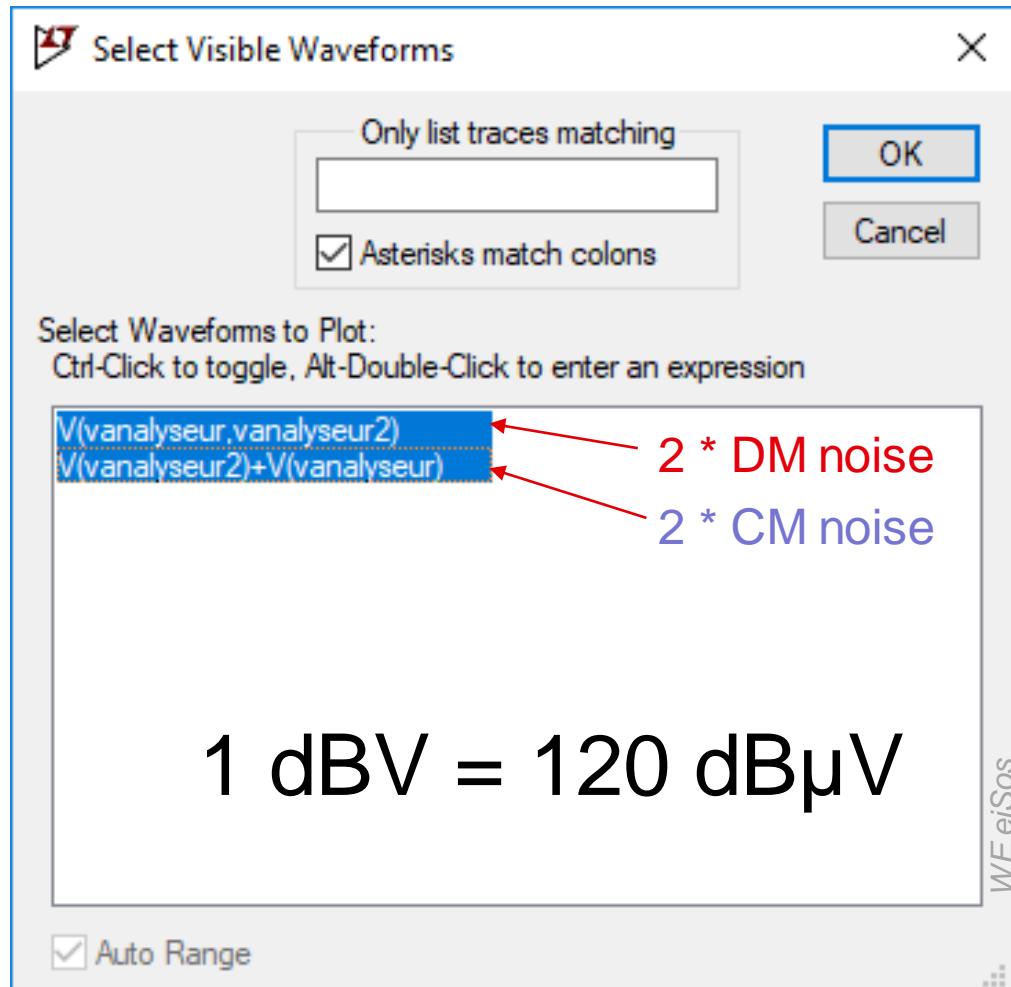

$$1 \text{ dBV} = 120 \text{ dB}\mu\text{V}$$

# Going further with simulation

## Making simulation look real

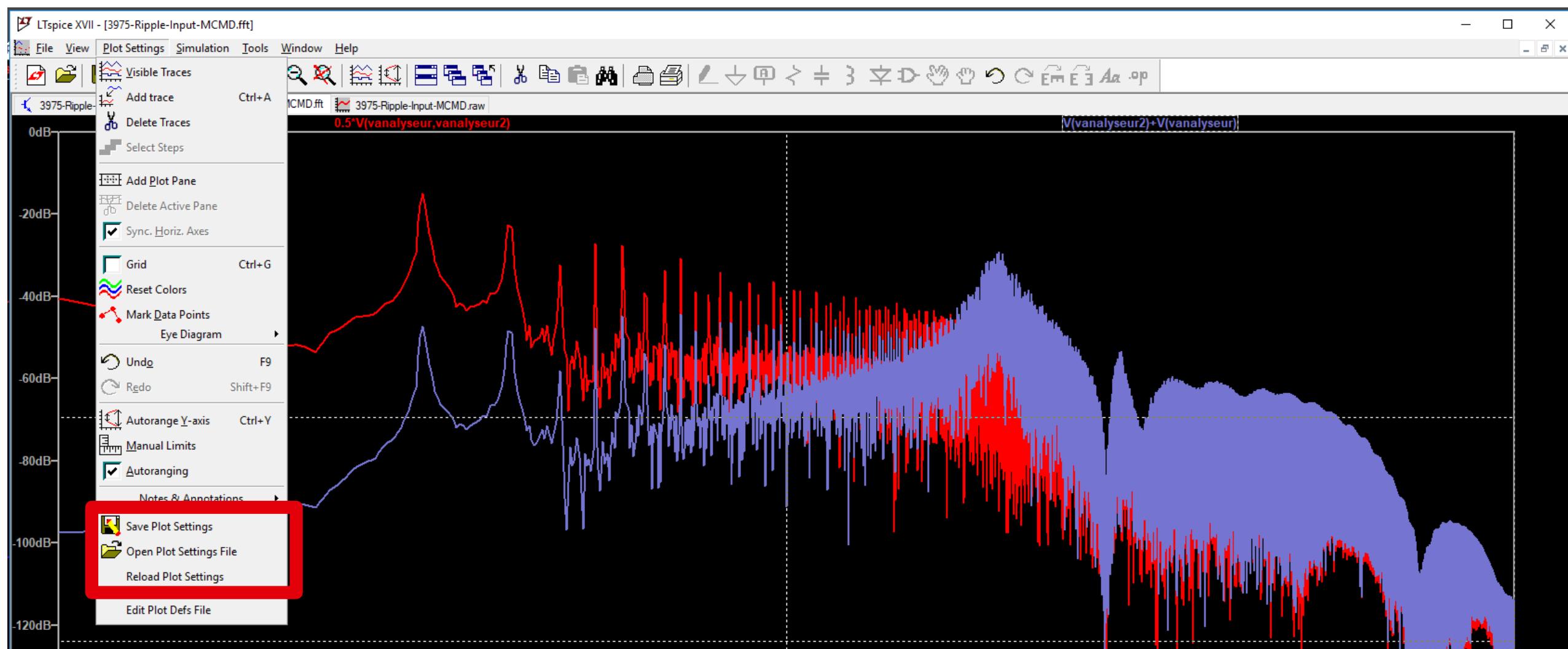

# Going further with simulation

## Making simulation look real – Adding limit lines



Line	Start	End	Amp dB $\mu$ V start	Amp dB $\mu$ V stop	Line def for LTSPICE
Line 1	1	9000	50000	110	110 (9000,0.316227766016838) (50000,0.316227766016838)
Line 2	2	50000	150000	90	80 (50000,0.0316227766016838) (150000,0.01)
Line 3	3	150000	500000	66	56 (150000,0.00199526231496888) (500000,0.000630957344480192)
Line 4	4	500000	5000000	56	56 (500000,0.000630957344480192) (5000000,0.000630957344480192)
Line 5	5	5000000	30000000	60	60 (5000000,0.001) (30000000,0.001)

Fill according to  
EMC standards

Copy the result

Paste it here

```
Flyback-example-2-base - Bloc-notes
Fichier Édition Format Affichage Aide
[FFT of time domain data]
{
    Npanes: 1
    {
        traces: 1 {2,0,"V(vanalyseur2)+V(vanalyseur)"}
        X: ('M',0,9000,0,30000000)
        Y[0]: (' ',0,1e-006,10,1)
        Y[1]: (' ',0,-200,40,200)
        Log: 1 2 0
        PltMag: 1
        Line: "dB" 4 0 (9000,0.3162277660168) (50000,0.316227766)
        Line: "dB" 4 0 (50049.8435712172,0.0317065818612387) (150407.110289202,0.0100397786508485)
        Line: "dB" 4 0 (150000,0.00199526231496888) (500000,0.000630957344480192)
        Line: "dB" 4 0 (500000,0.000630957344480192) (5000000,0.000630957344480192)
        Line: "dB" 4 0 (5000000,0.001) (30000000,0.001)
    }
}
```

# Going further with simulation

## Making simulation look real – Defining a range



10kHz to 30 MHz

0 to 120dB $\mu$ V


```

3975-Ripple-Input-MCMD-dbuV.plt - Bloc-notes
Fichier Edition Format Affichage ?
[FFT of time domain data]
{
    Npanes: 1
    {
        traces: 2 {65540,0,"500000*V(vanalyseur,vanalyseur2)"} {65547,0,"1000000*(V(vanalyseur2)+V(vanalyseur))"}
        X: ('M',0,10000,0,3e+007)
        Y[0]: (' ',0,1,20,1e+006)
        Log: 1 2 0
        GridStyle: 1
        PltMag: 1
        Line: "dB" 13 0 (8983.92329505352,319040.747263751) (49889.5367382049,319040.747263751)
        Line: "dB" 13 0 (50000,316227.766016838) (50000,31622.7766016838)
        Line: "dB" 13 0 (50000,31622.7766016838) (150000,10000)
        Line: "dB" 13 0 (150000,10000) (150000,1995.26231496888)
        Line: "dB" 13 0 (150000,1995.26231496888) (500000,630.957344480193)
        Line: "dB" 13 0 (500000,630.957344480193) (5000000,630.957344480193)
        Line: "dB" 13 0 (5000000,630.957344480193) (5000000,1000)
        Line: "dB" 13 0 (5000000,1000) (30000000,1000)
    }
}

```


# Going further with simulation

# Making simulation look real – Result 😊

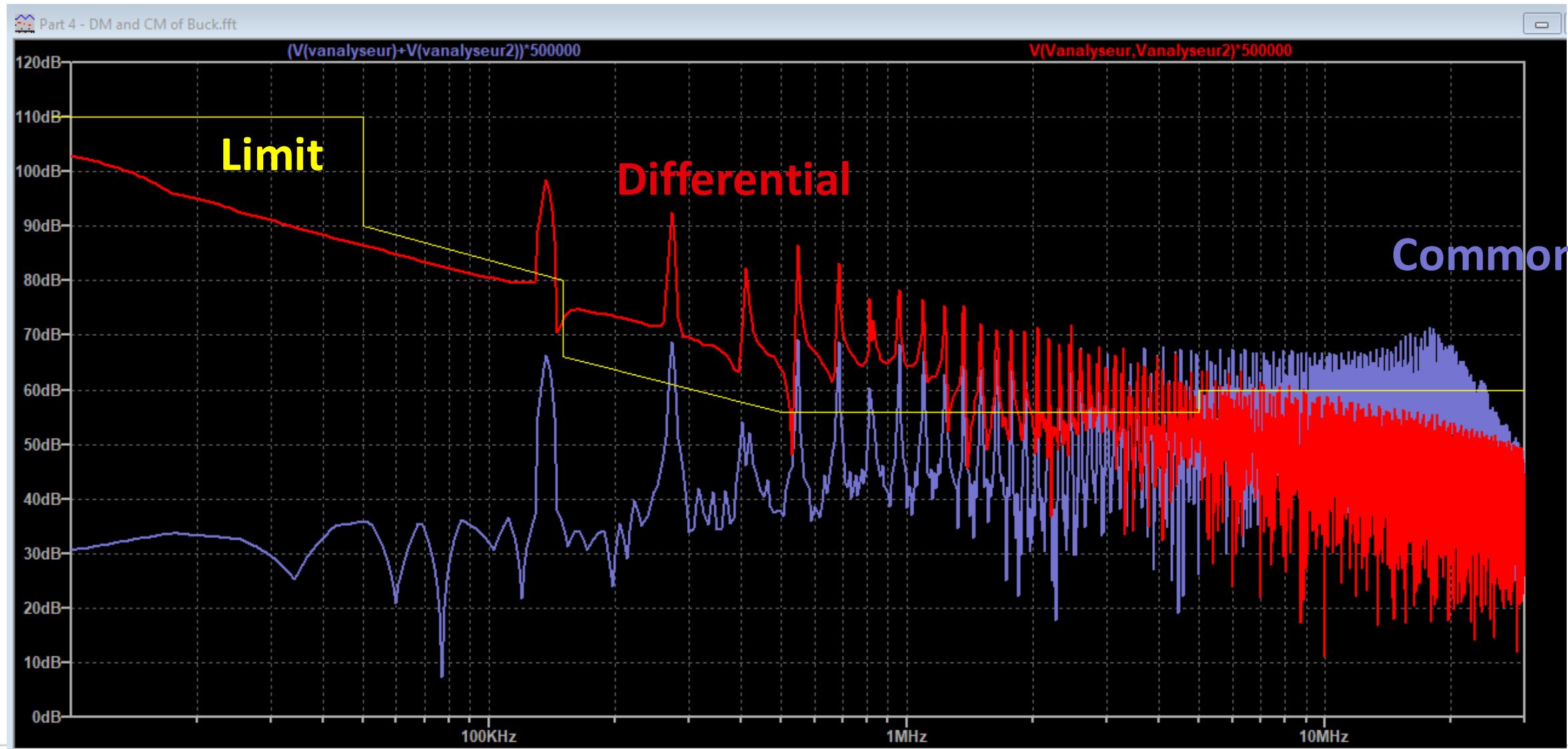

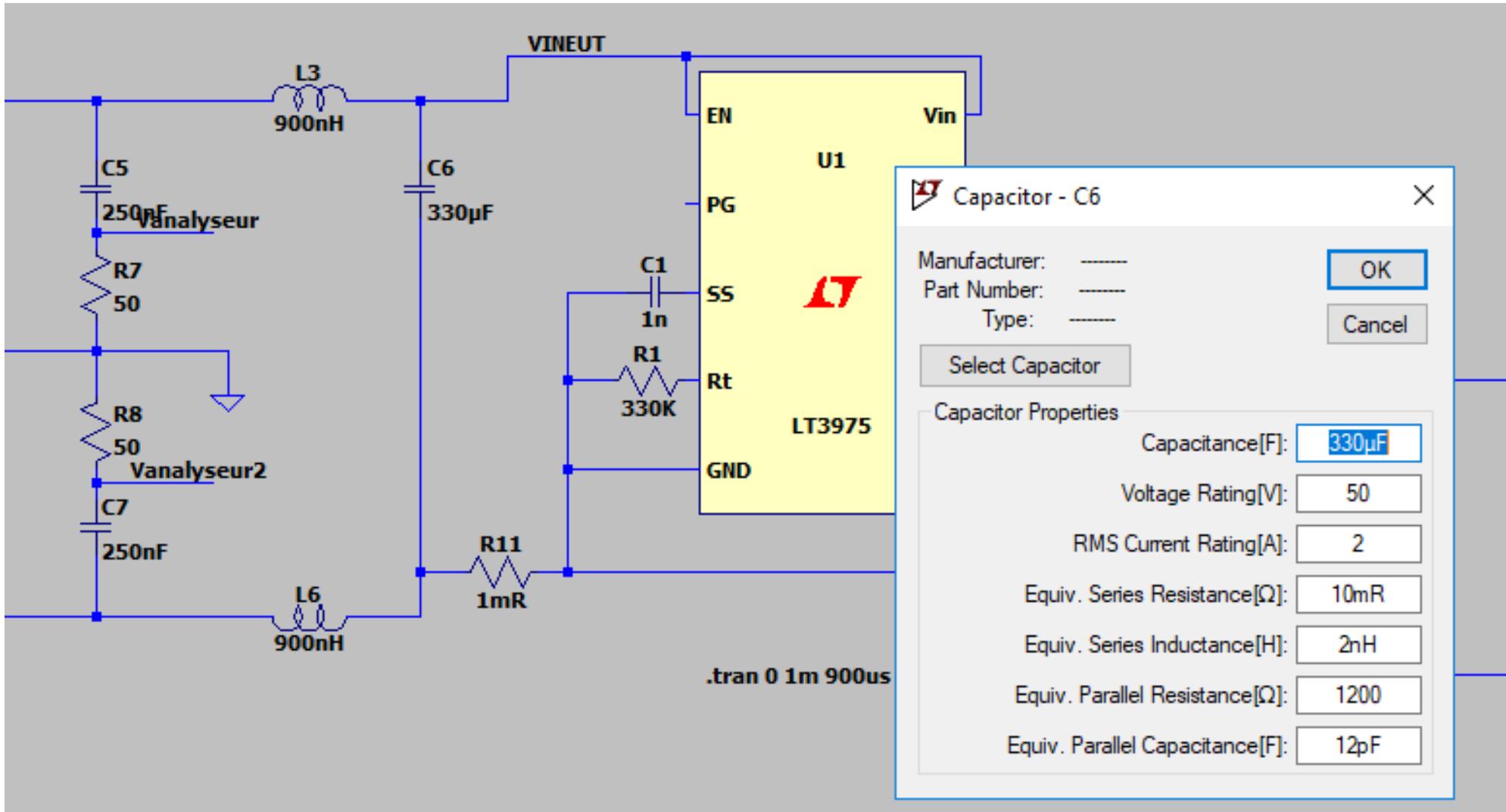
# Going further with simulation

Fixing that buck in the simulation – Polymer input cap



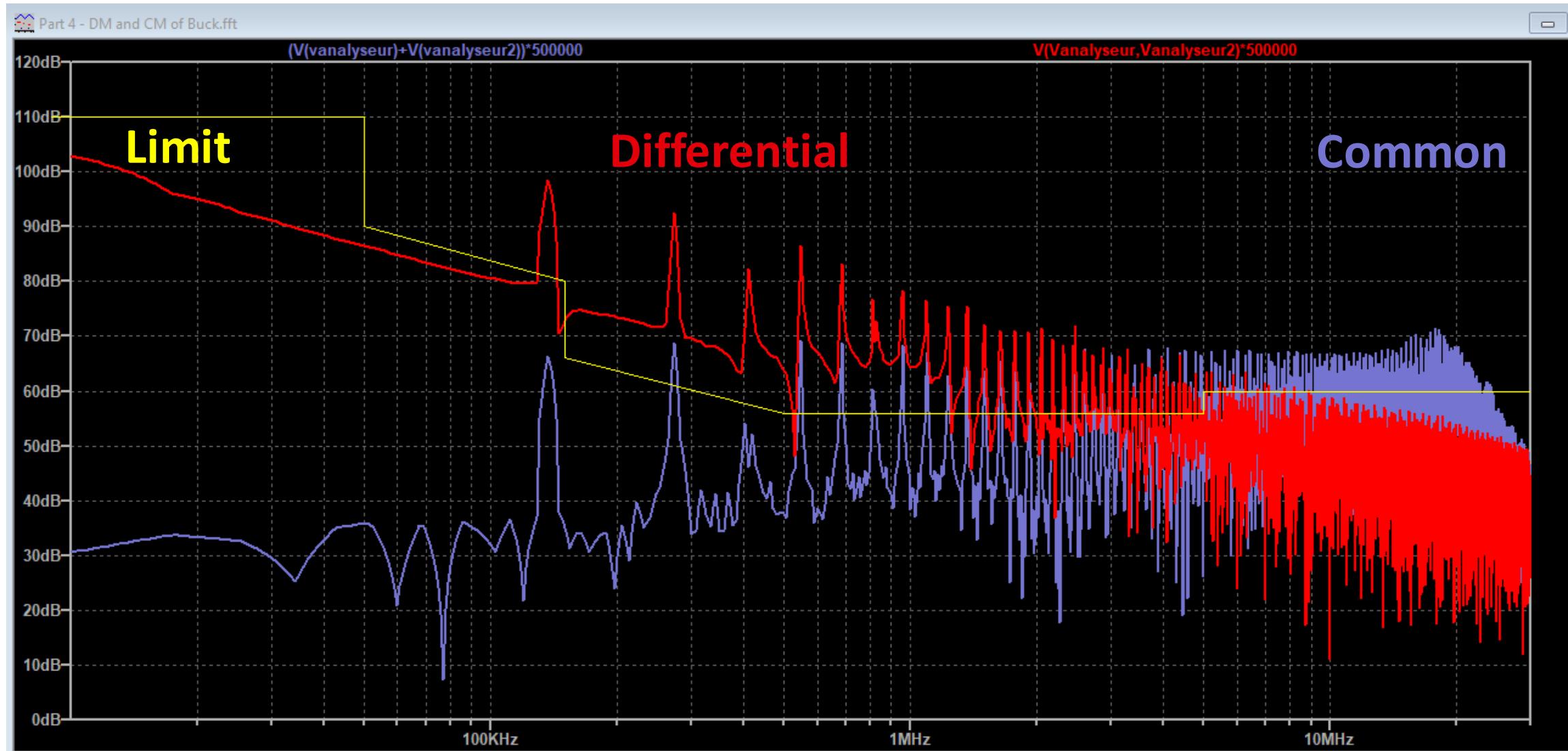
# Going further with simulation

Fixing that buck in the simulation – Before Polymer Cap


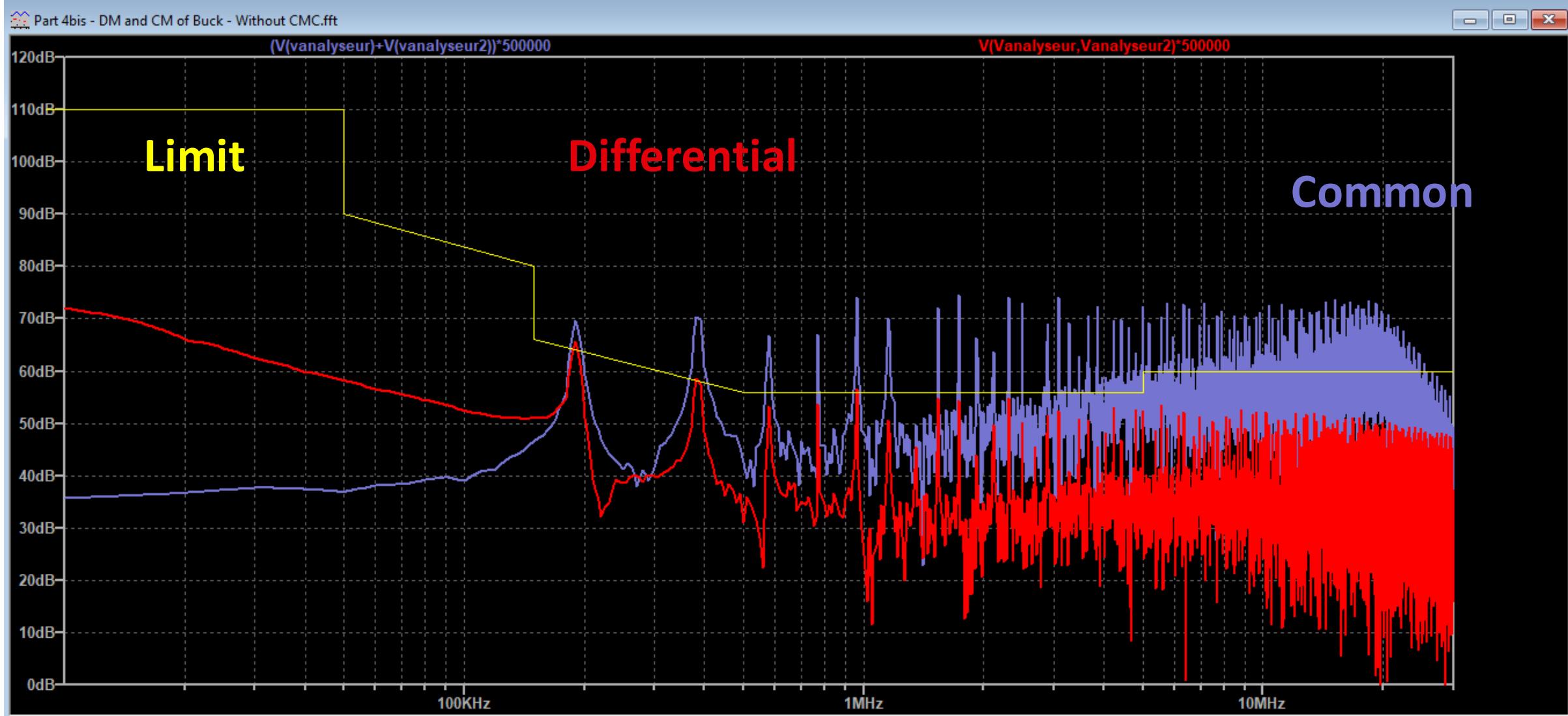
# Going further with simulation

Fixing that buck in the simulation – After Polymer Cap





Limit

Differential

Common
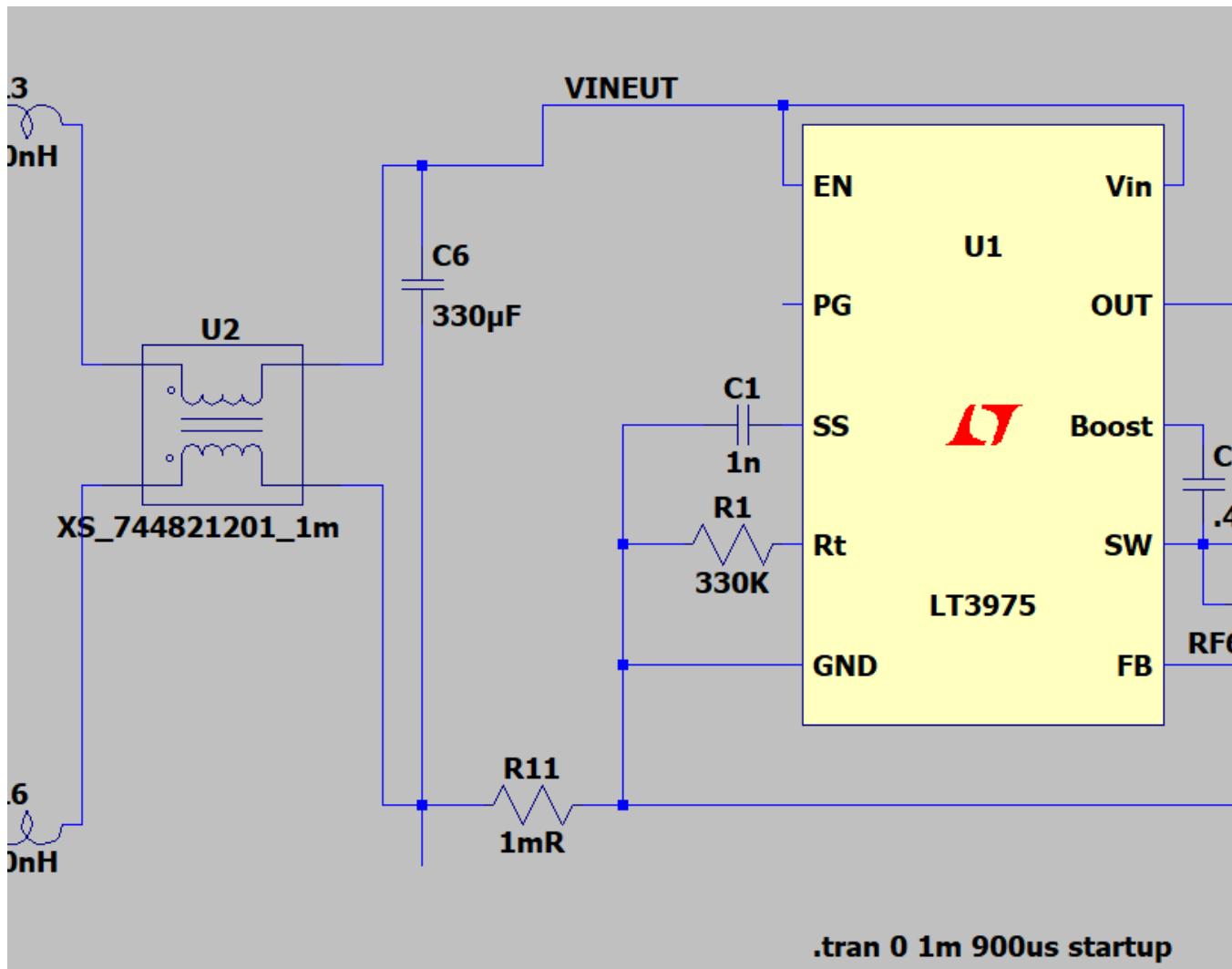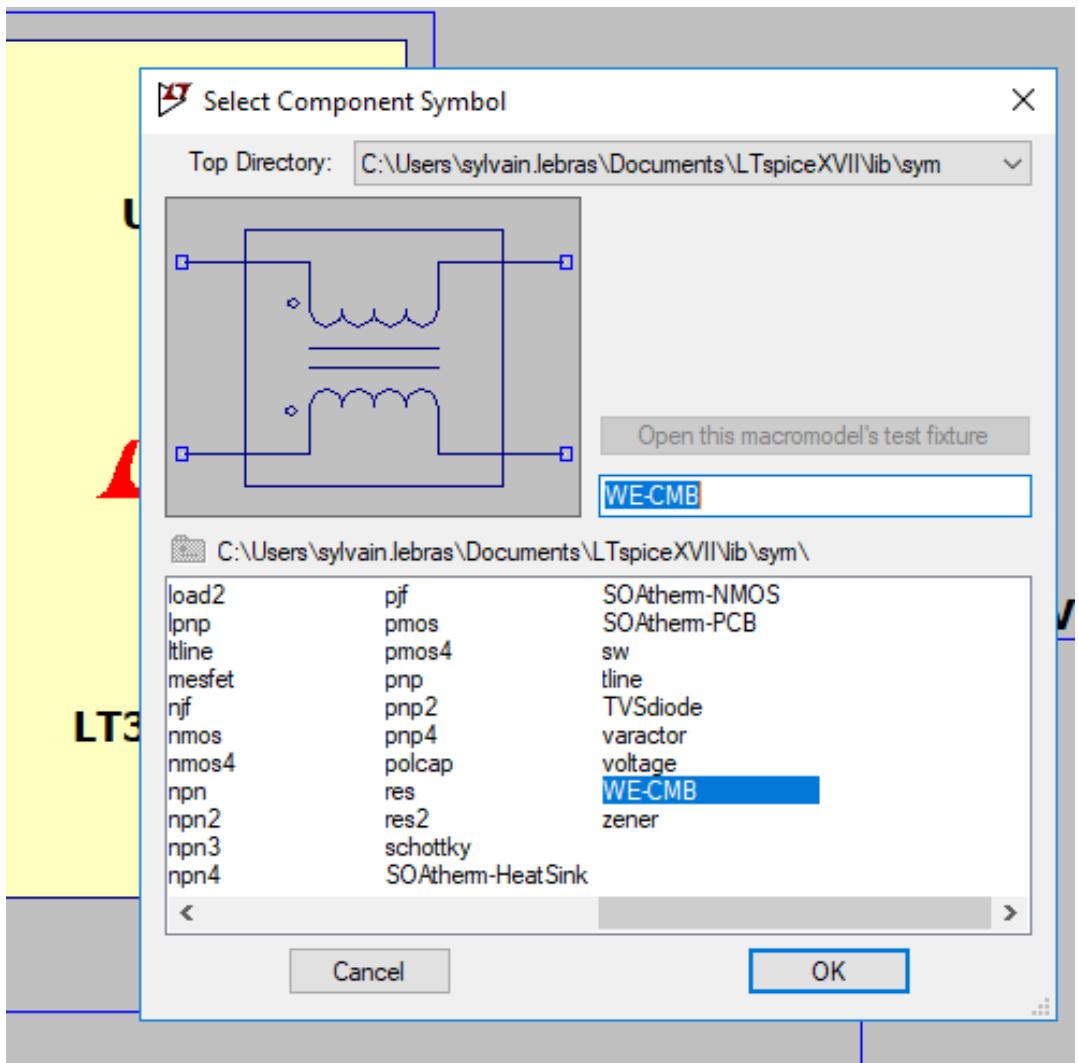
# Going further with simulation


Fixing that buck in the simulation – Common mode choke



.tran 0 1m 900us startup

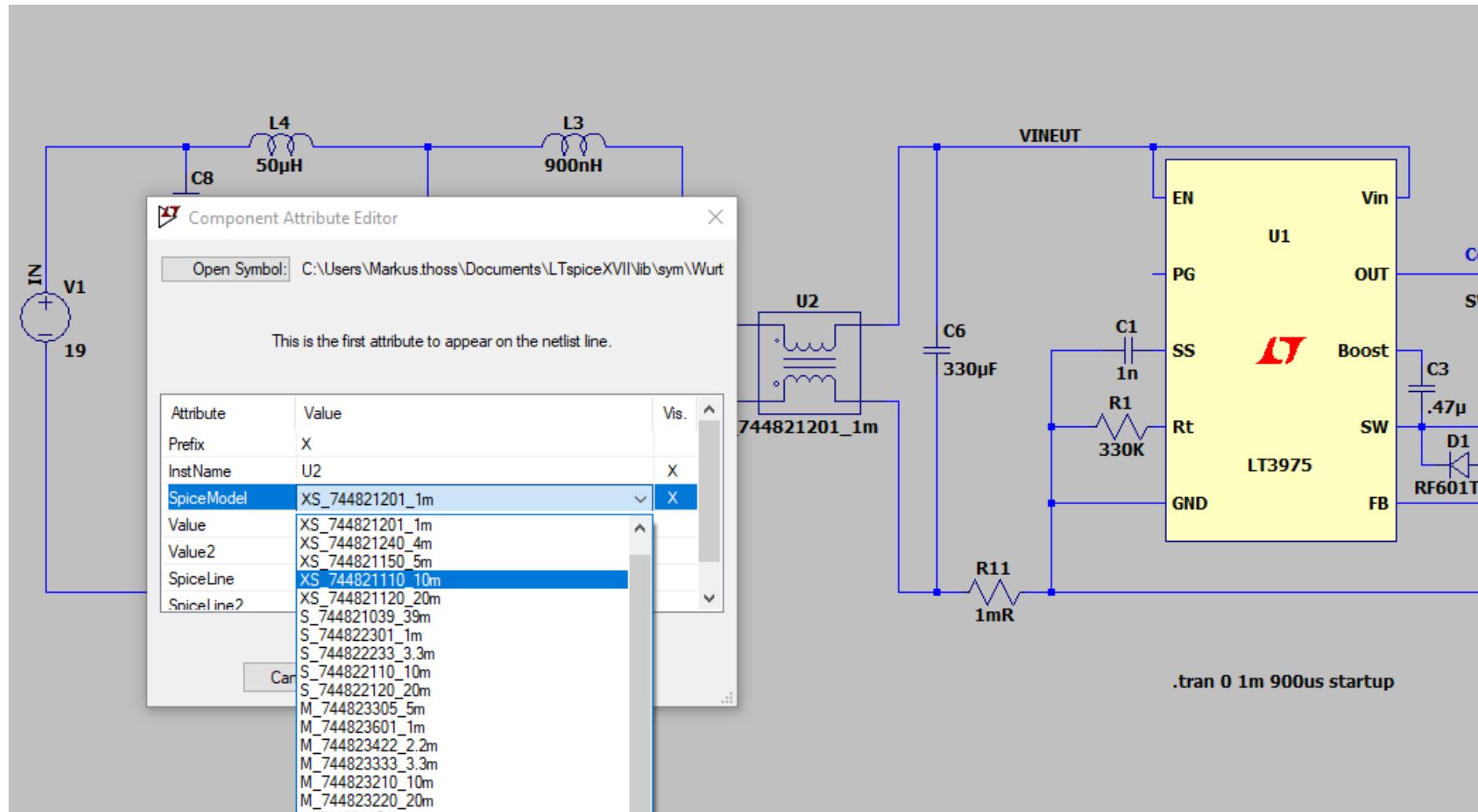
# Going further with simulation

Fixing that buck in the simulation – Input Common mode choke



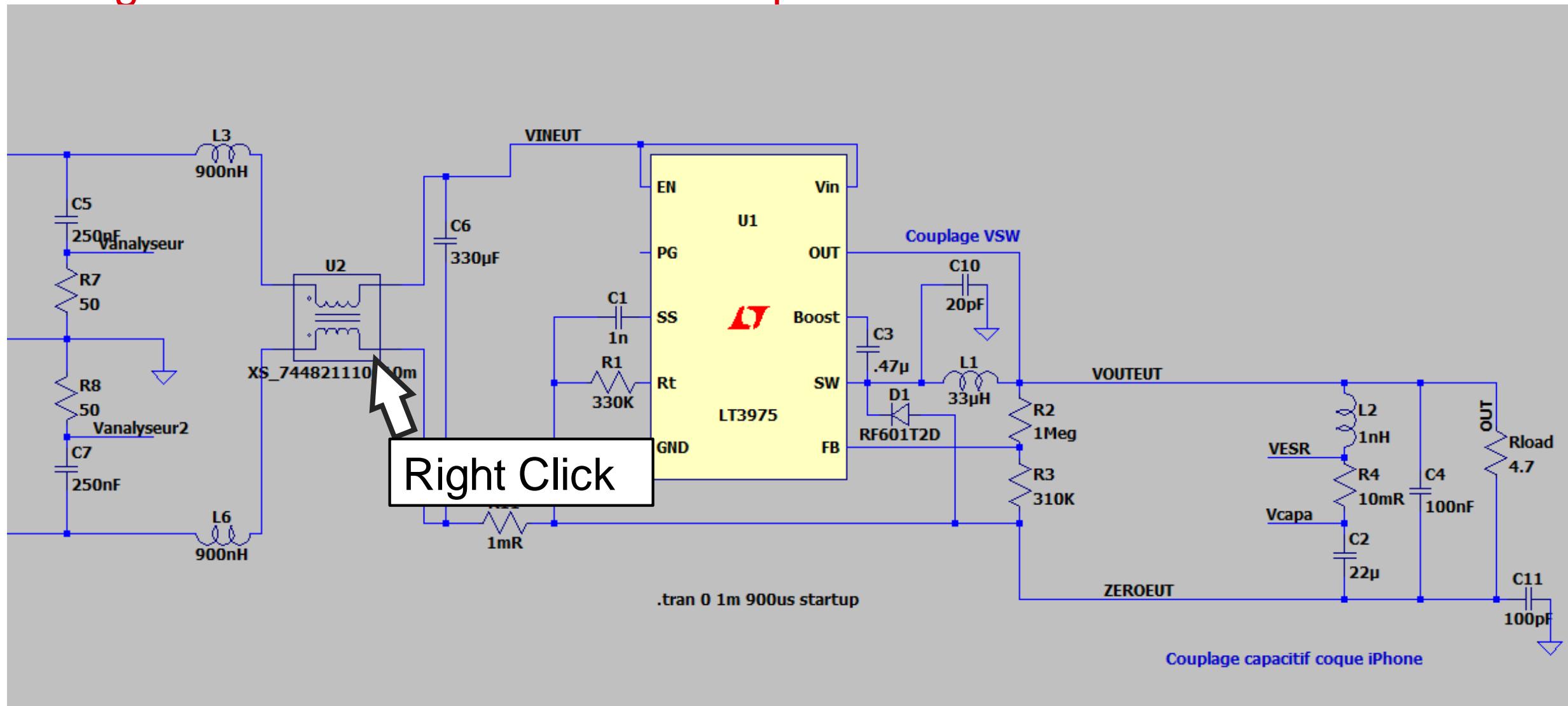
# Going further with simulation

Fixing that buck in the simulation – Input Common mode choke



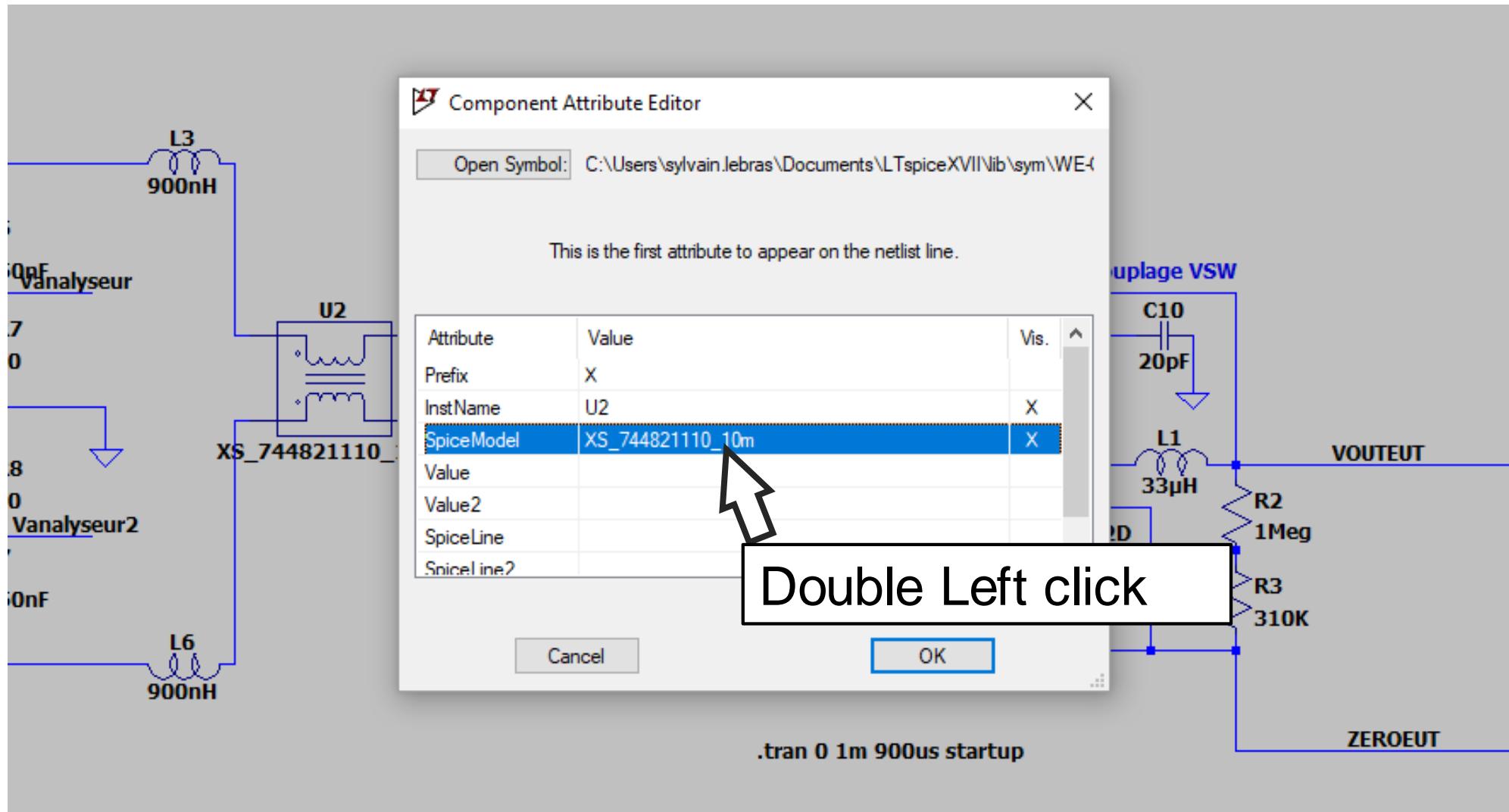
# Going further with simulation

Fixing that buck in the simulation – Input Common mode choke



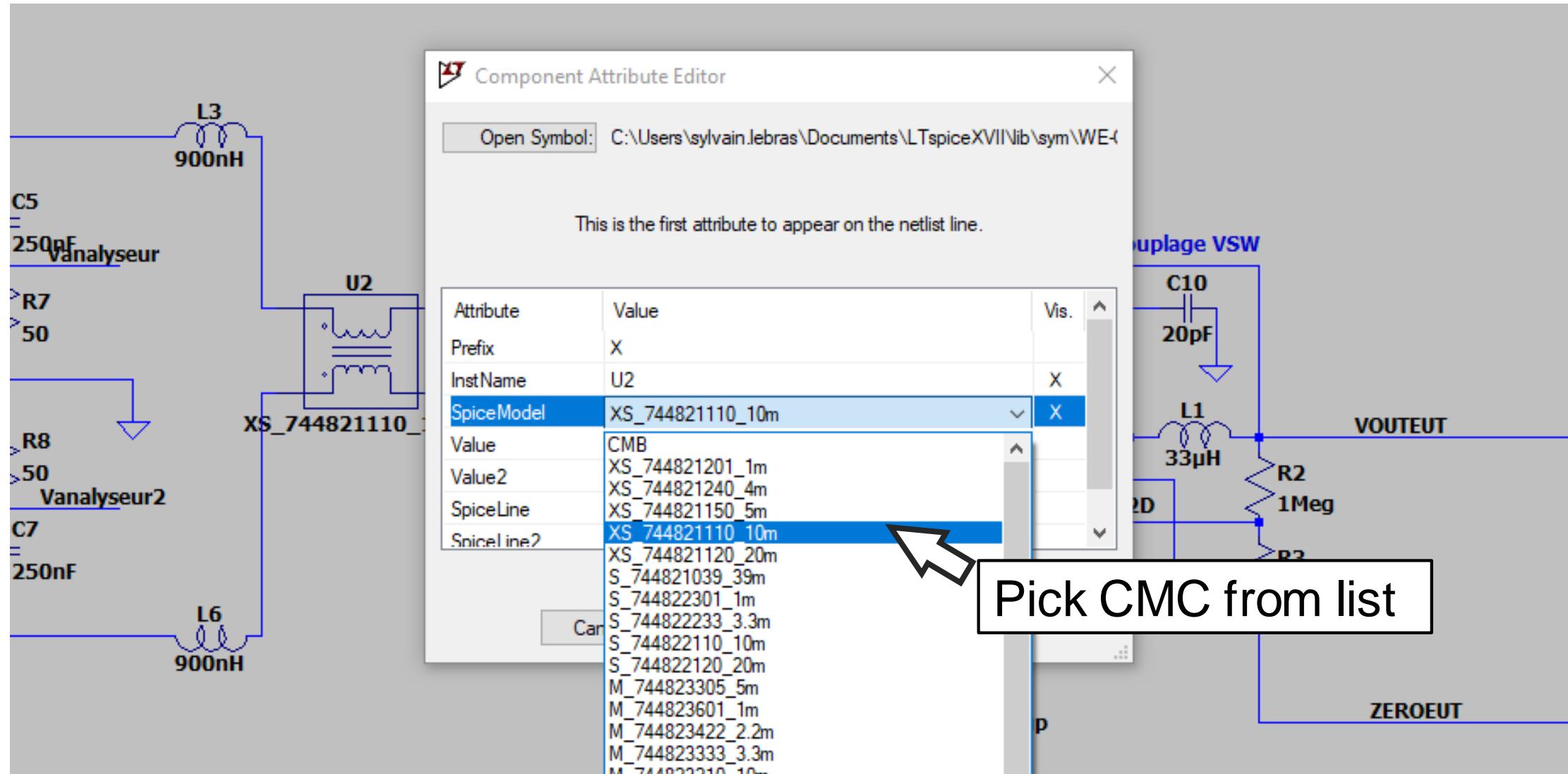
# Going further with simulation

Fixing that buck in the simulation – Input Common mode choke



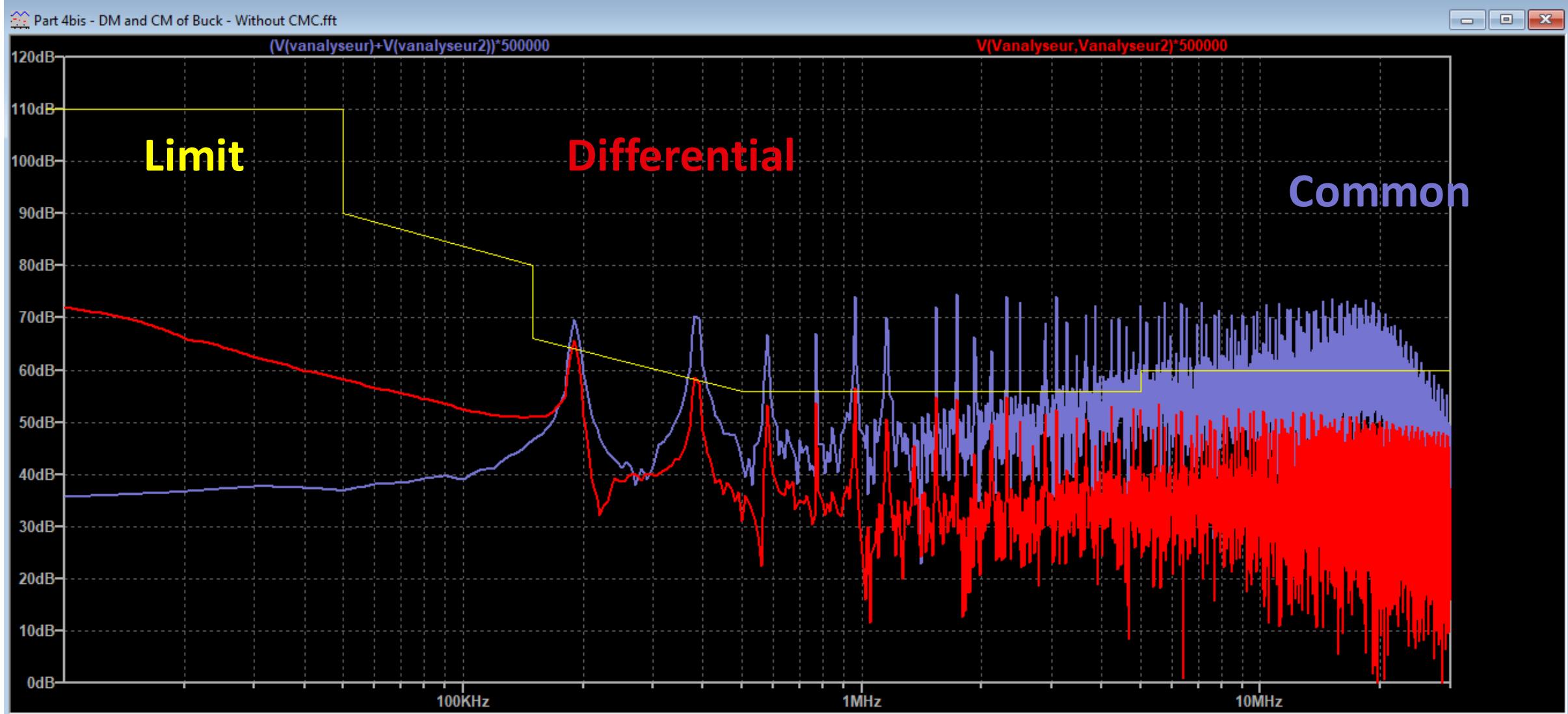
# Going further with simulation

Fixing that buck in the simulation – Without Common mode choke



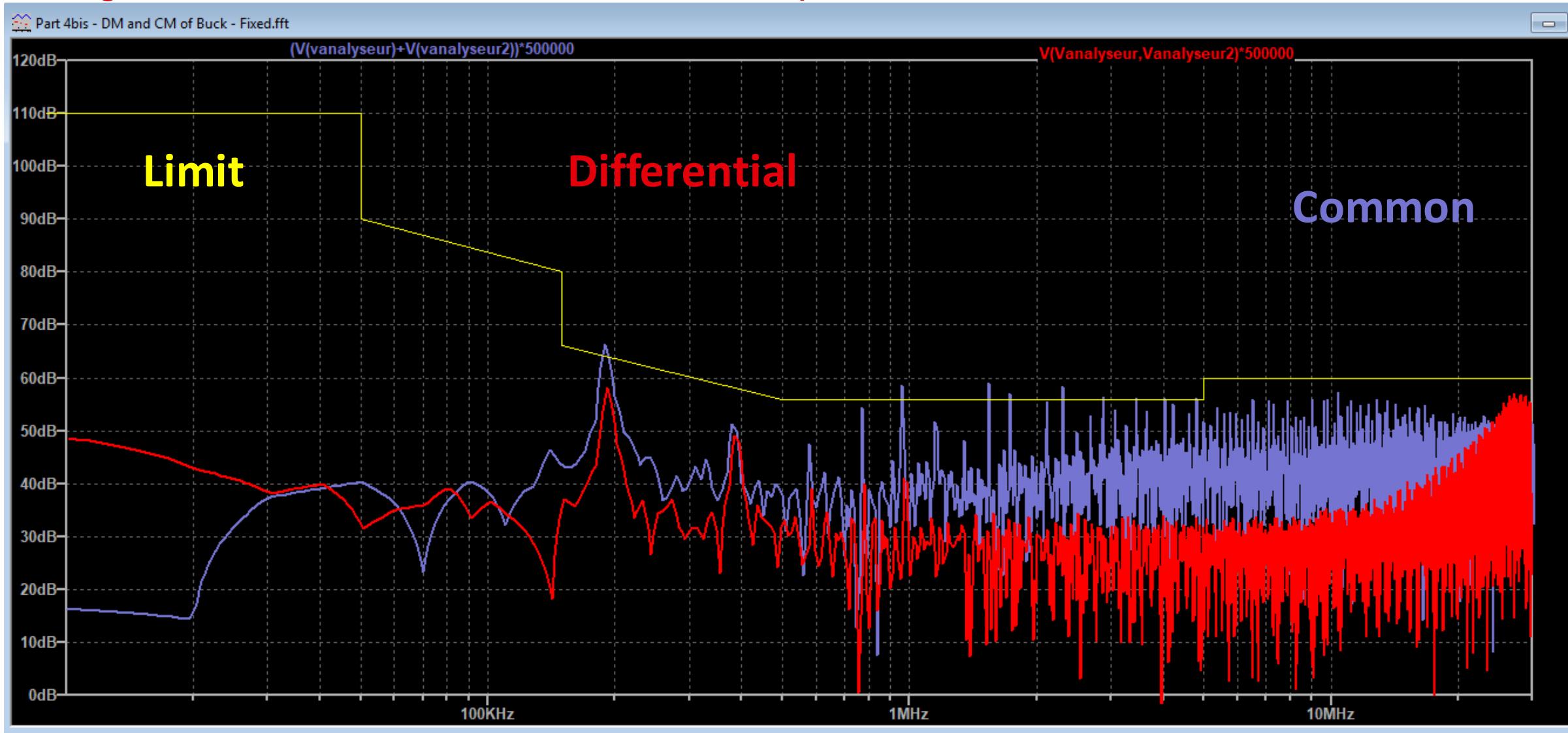
# Going further with simulation

Fixing that buck in the simulation – With input Common mode choke




# Going further with simulation
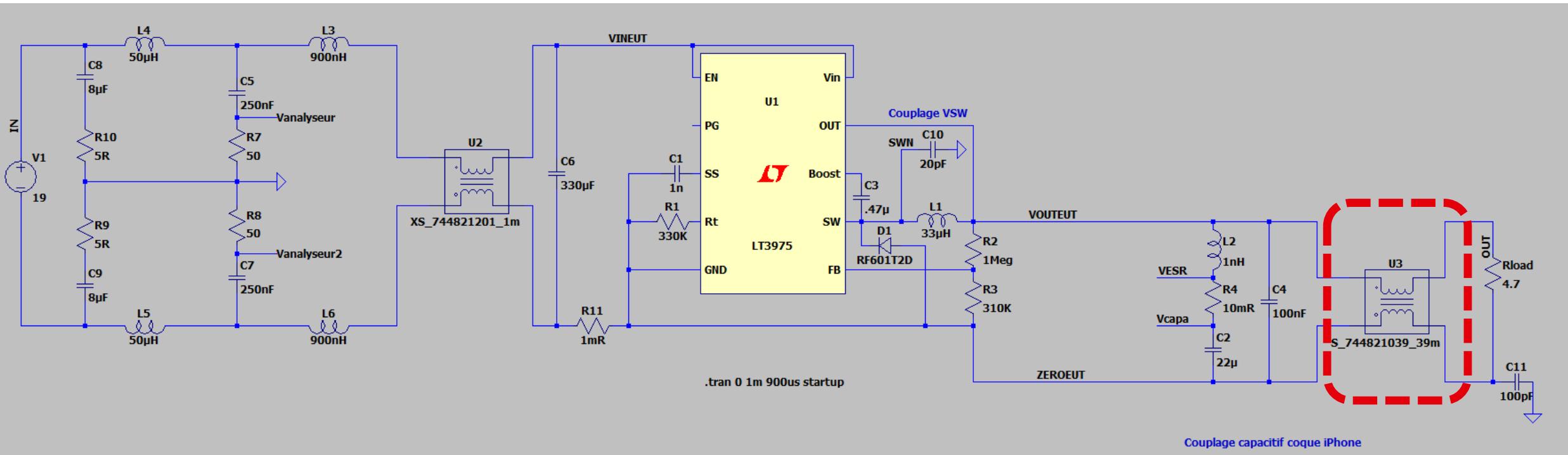
## Fixing that buck in the simulation – With output CMC



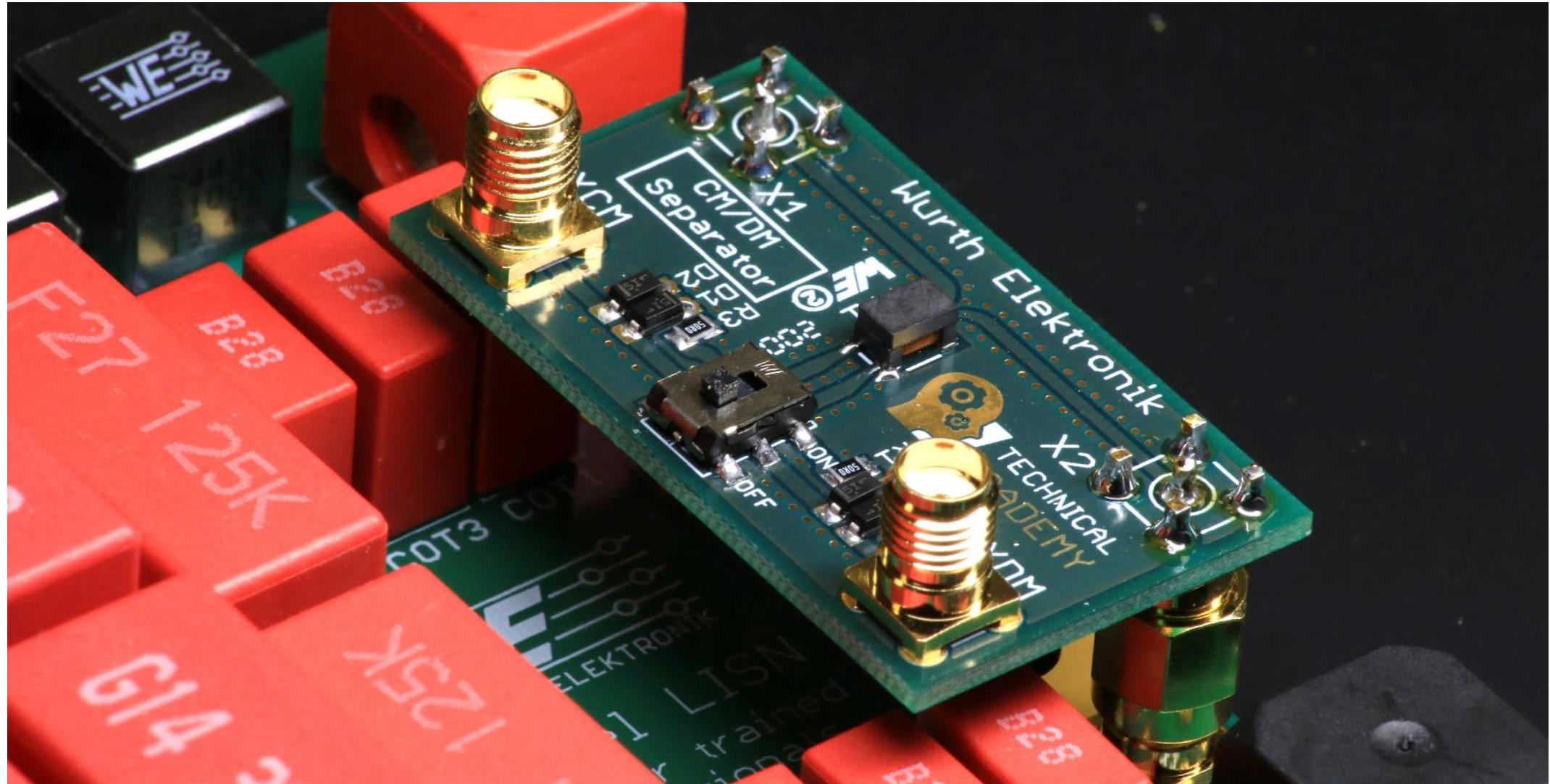
# Going further ?

Common mode / Differential Mode separator in real life



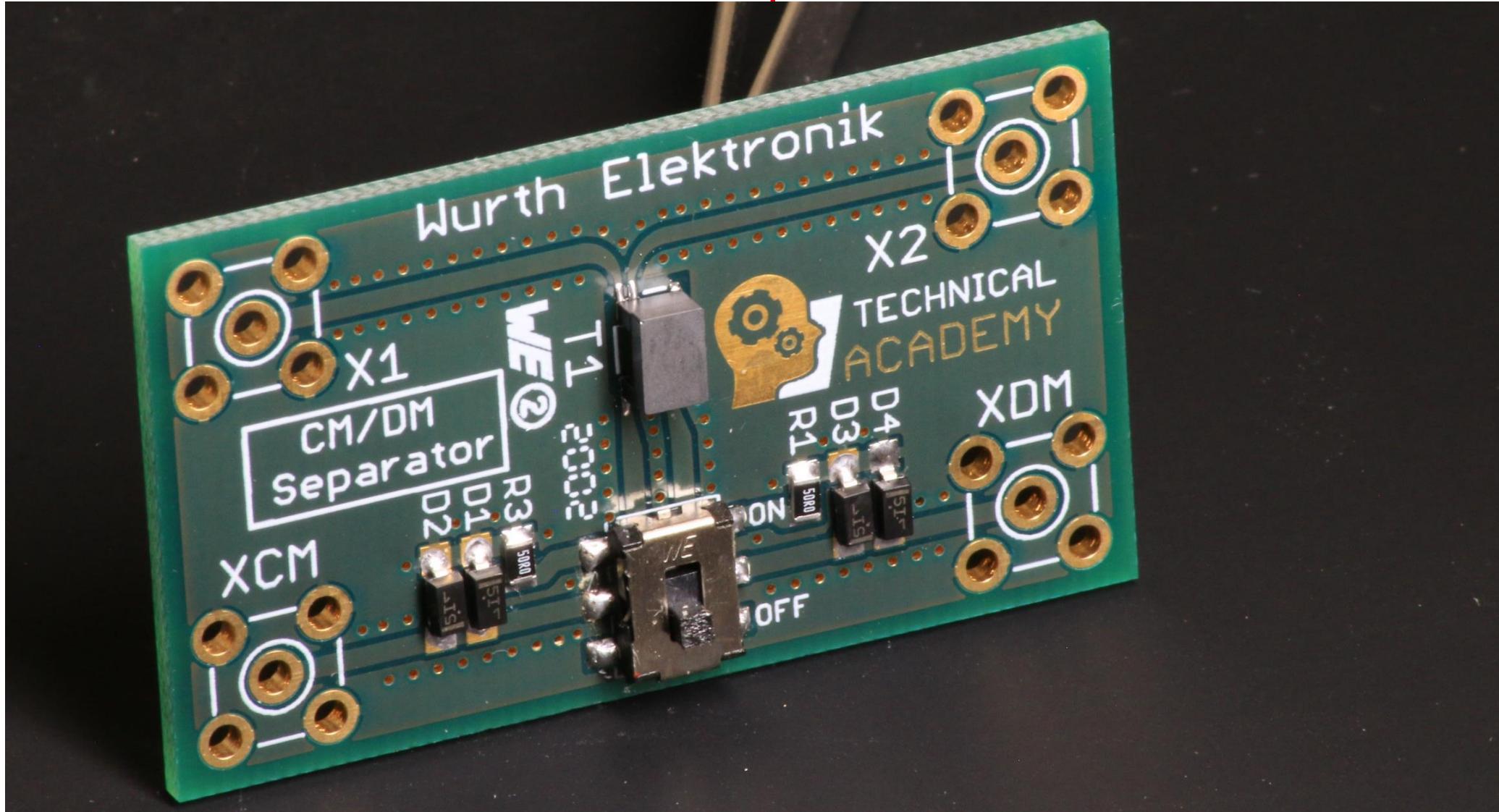
# Going further ?

Common mode / Differential Mode separator in real life


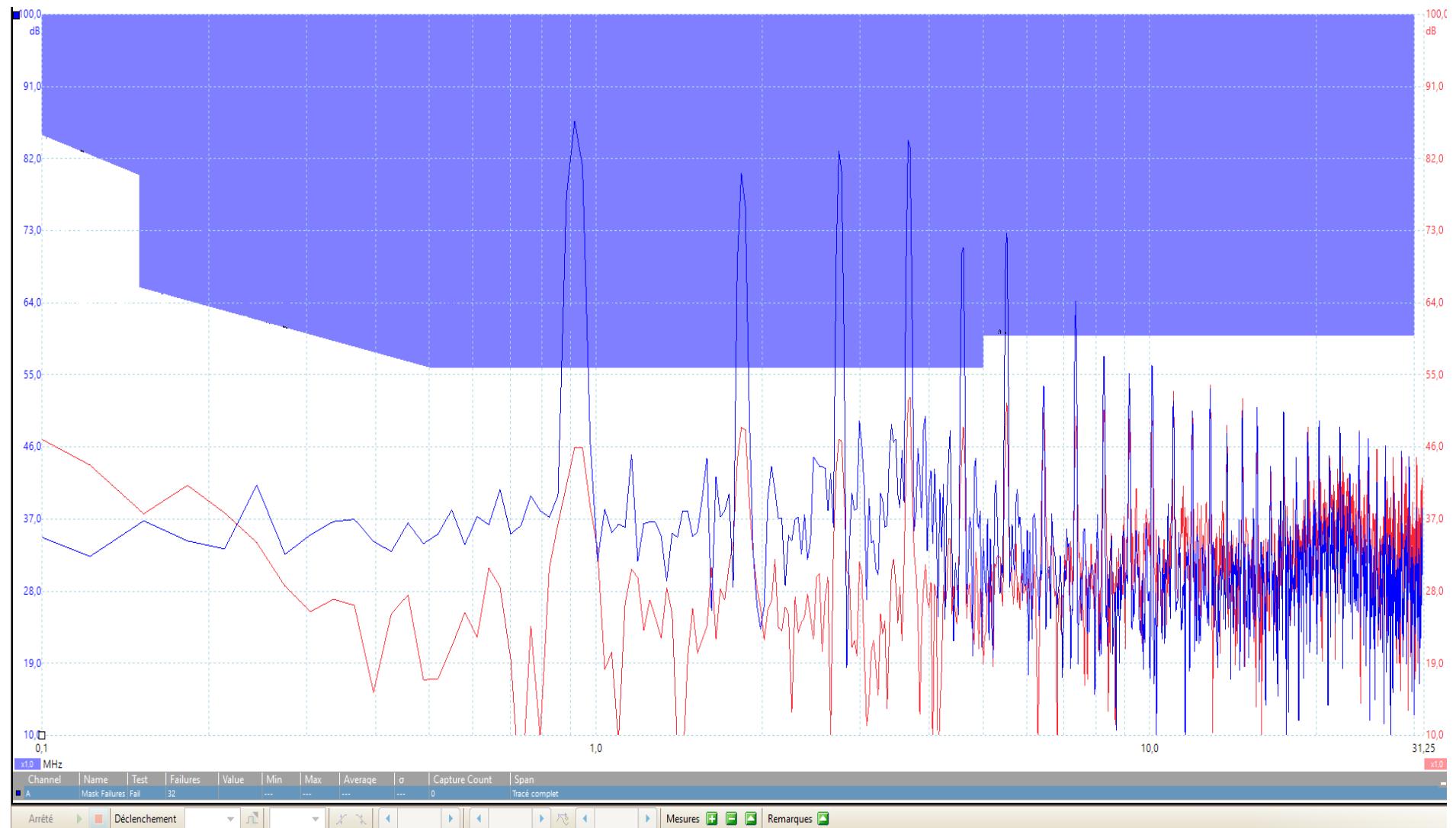
# Going further ?

Common mode / Differential Mode separator in real life



# Modeling Real life examples

## Flyback converter for lighting applications




# Modeling Real life examples
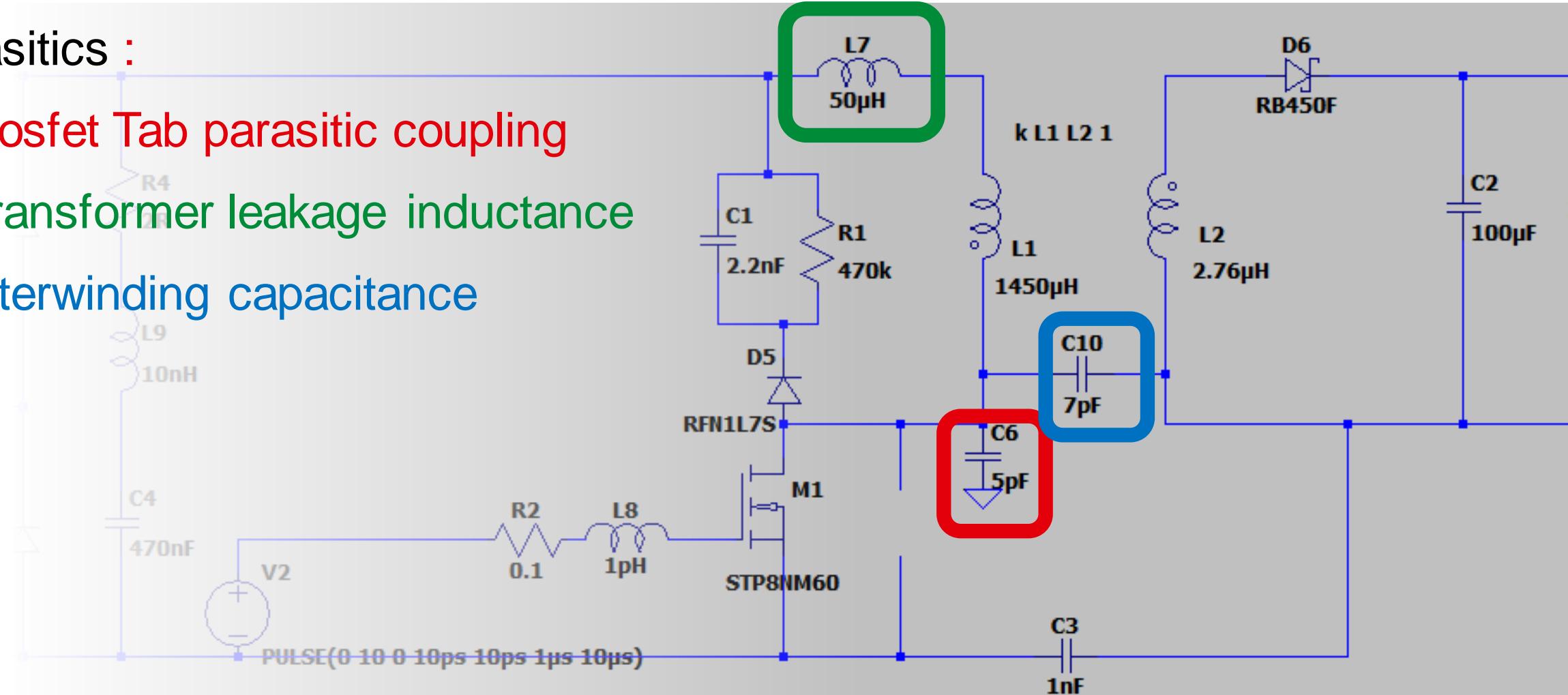
## Flyback converter for lighting applications



- Parasitics :


- Mosfet Tab parasitic coupling
- Transformer leakage inductance
- Interwinding capacitance



# Real life examples

## Flyback converter for lighting applications



Mosfet Tab parasitic coupling

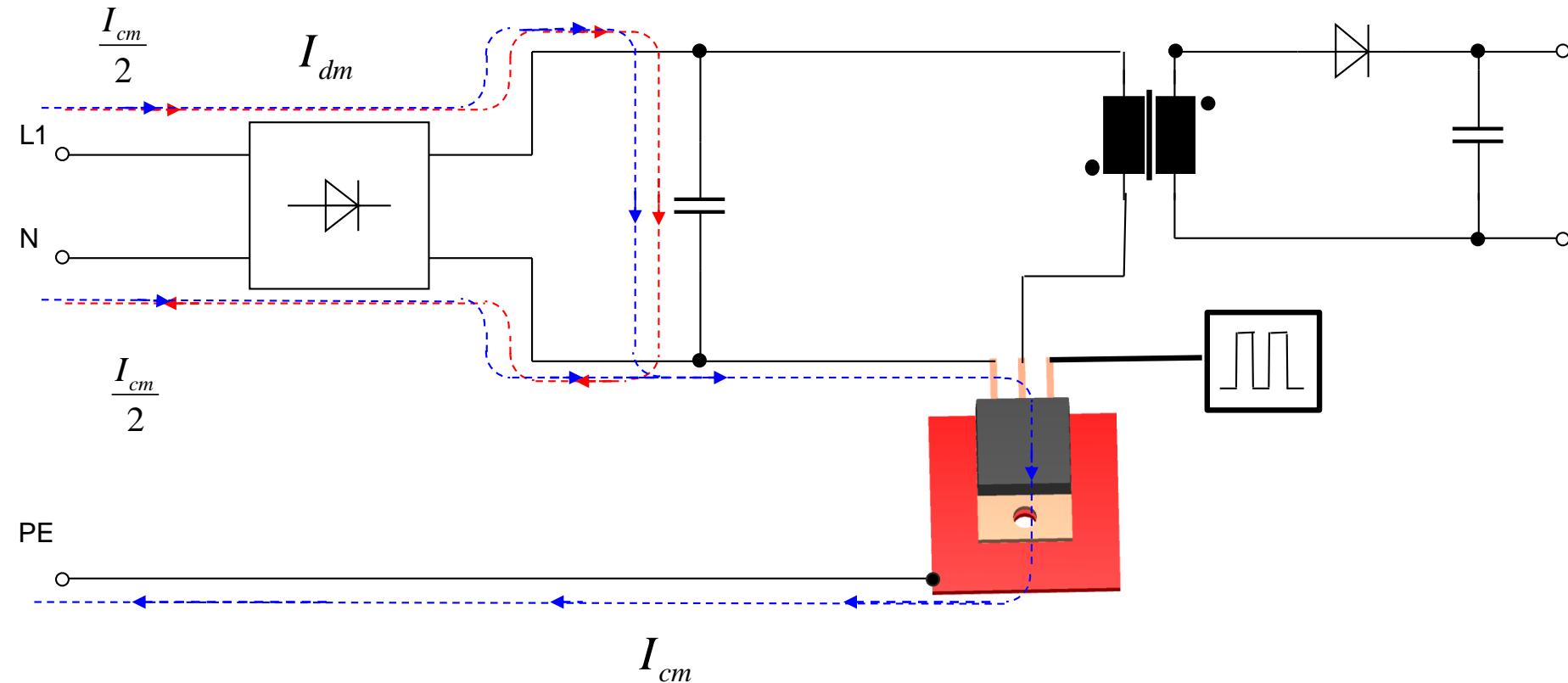

# Real life examples

## Flyback converter for lighting applications


Mosfet Tab parasitic coupling

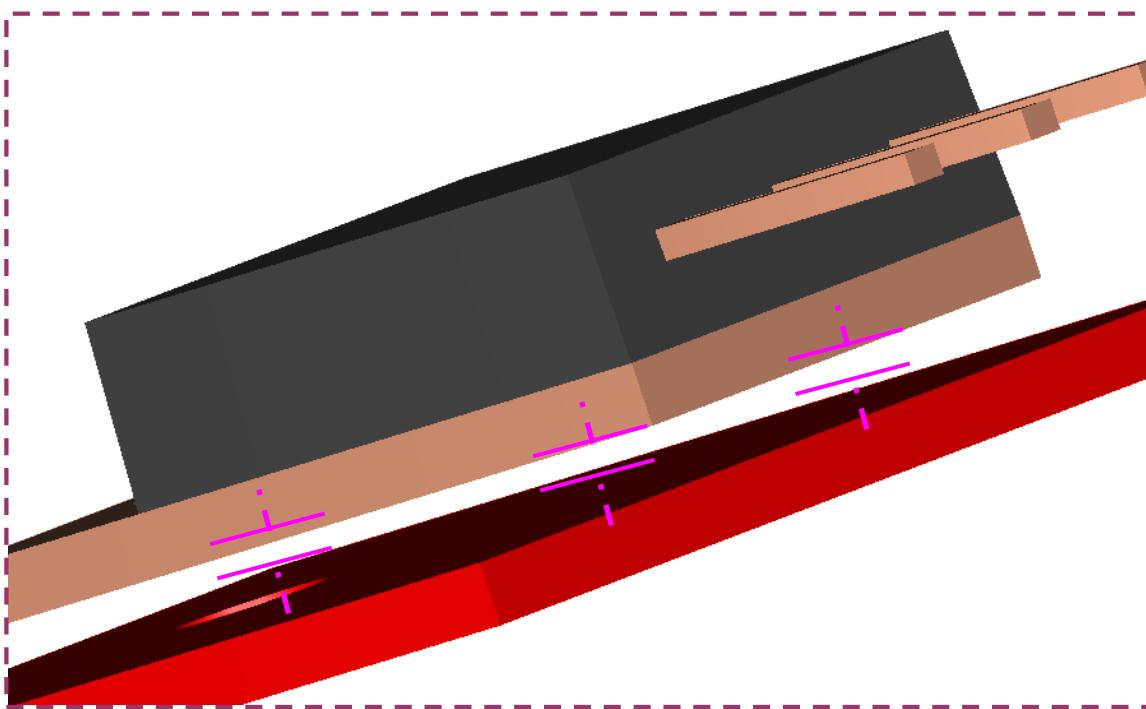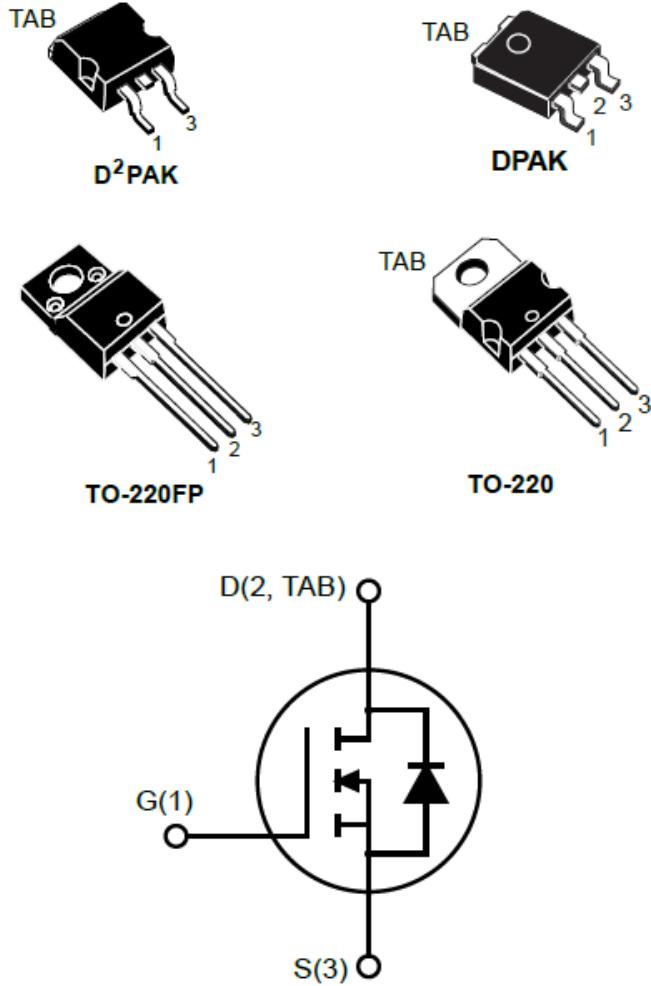

# Real life examples

## Flyback converter for lighting applications

Mosfet Tab parasitic coupling

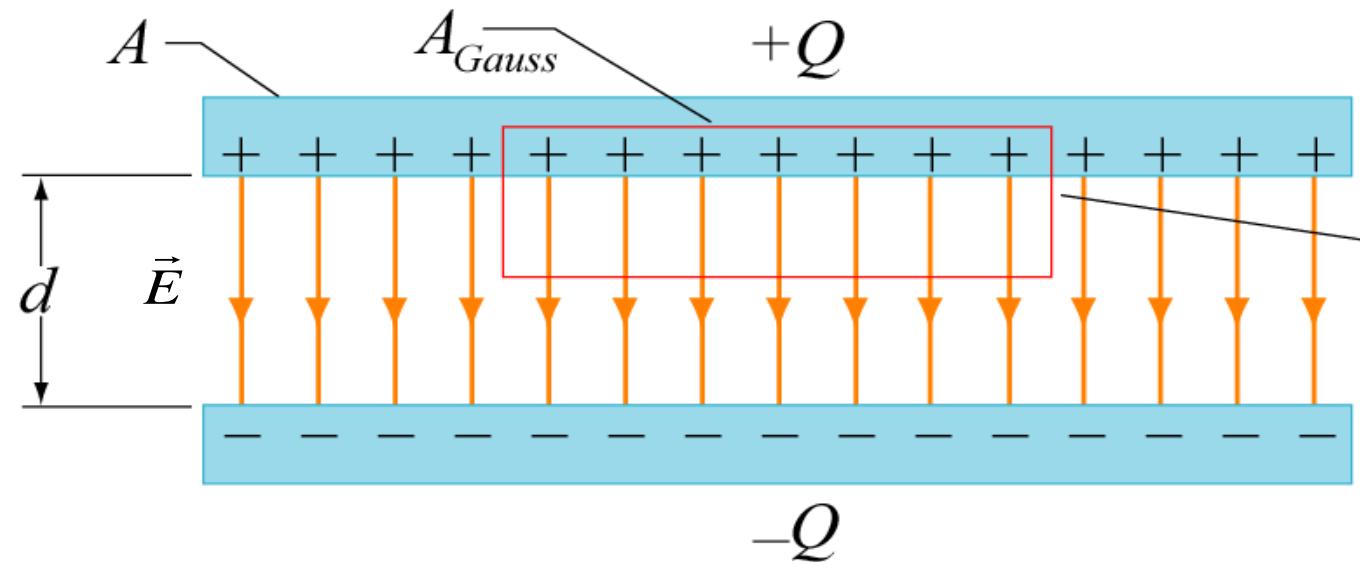

$$C = \frac{\epsilon_0 A}{d}$$


# Real life examples

## Flyback converter for lighting applications

Primary leakage inductance

### D Electrical Properties:

Properties	Test conditions		Value	Unit	Tol.
<b>Inductance</b>	100 kHz/ 100 mV	L	1310	µH	±10%
<b>Turns ratio</b>		n	140 : 6 : 6 : 16		±3%
<b>Saturation current</b>	$  \Delta L / L   < 20\%$	$I_{sat}$	0.8	A	typ.
<b>DC Resistance 1</b>	@ 20°C	$R_{DC1}$	3000.0	mΩ	max.
<b>DC Resistance 2</b>	@ 20°C	$R_{DC2}$	25.0	mΩ	max.
<b>DC Resistance 3</b>	@ 20°C	$R_{DC3}$	25.0	mΩ	max.
<b>DC Resistance 4</b>	@ 20°C	$R_{DC4}$	450.0	mΩ	max.
<b>Leakage inductance</b>	100 kHz/ 100 mV	$L_S$	40.0	µH	max.
<b>Insulation test voltage</b>	$W1,4 \Rightarrow W2,3$	$U_T$	4000	V (AC)	

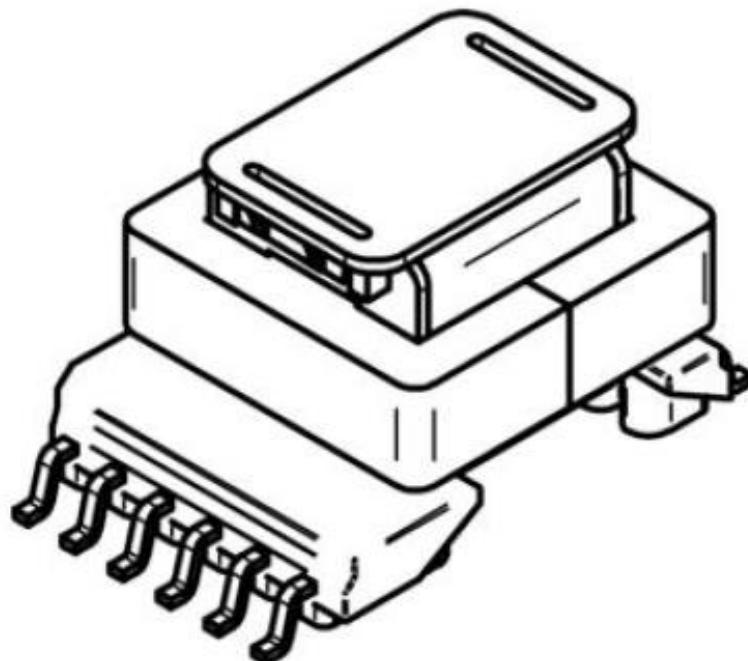

**WE-UOST**

# Real life examples

## Turn ratio to inductance ?



Transformers : from datasheet to LTSpice model

Primary inductance

1310  $\mu\text{H}$

L<sub>p</sub>

Leakage inductance

50  $\mu\text{H}$

L<sub>1</sub>

Primary	Secondary	Aux
---------	-----------	-----

130	6	16
-----	---	----

Secondary inductance


2.79  $\mu\text{H}$

L<sub>s</sub>

Auxiliary inductance

19.84  $\mu\text{H}$



L<sub>a</sub>

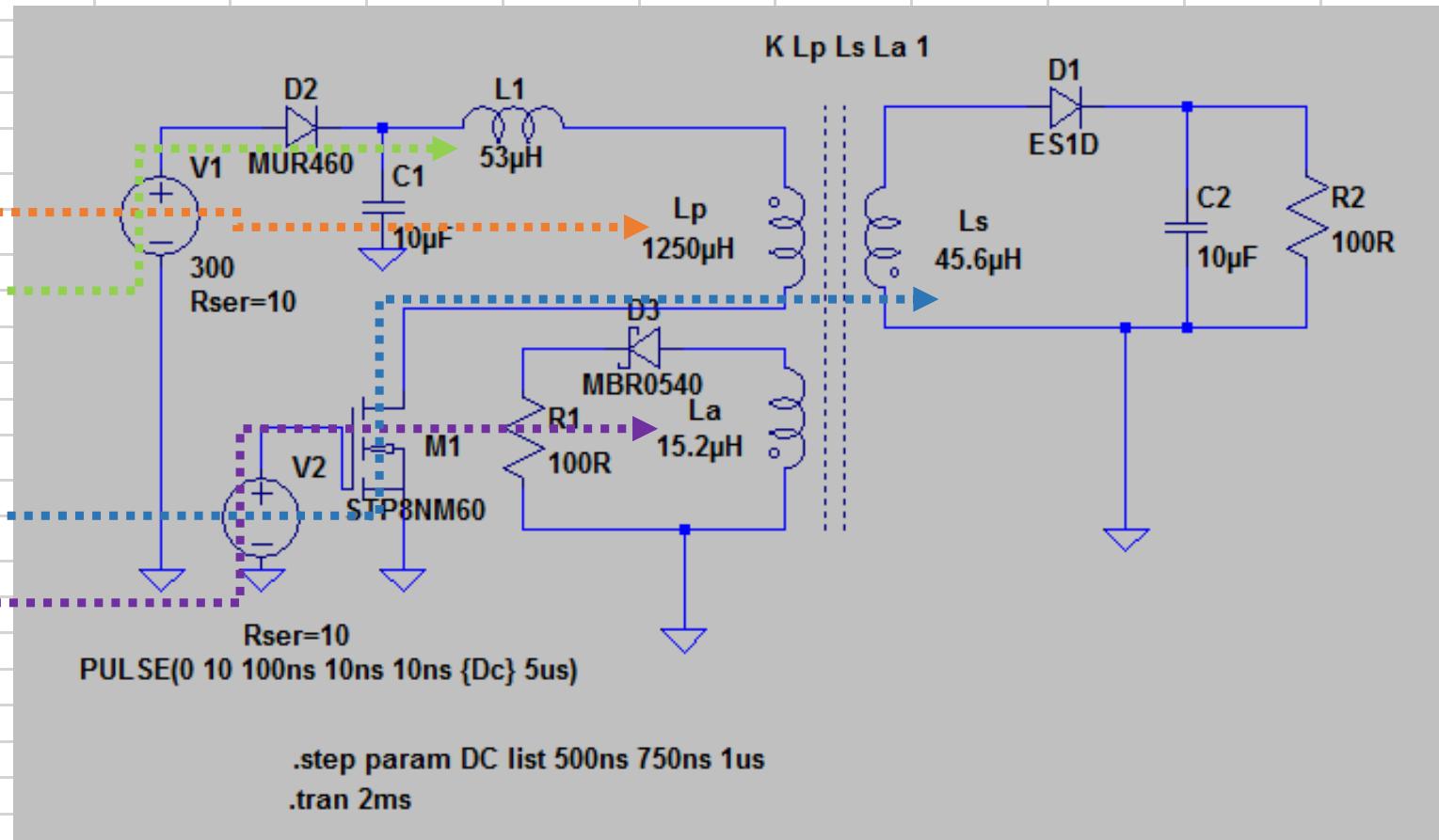

# Real life examples


## Flyback converter for lighting applications

### ■ Interwinding capacitance ?

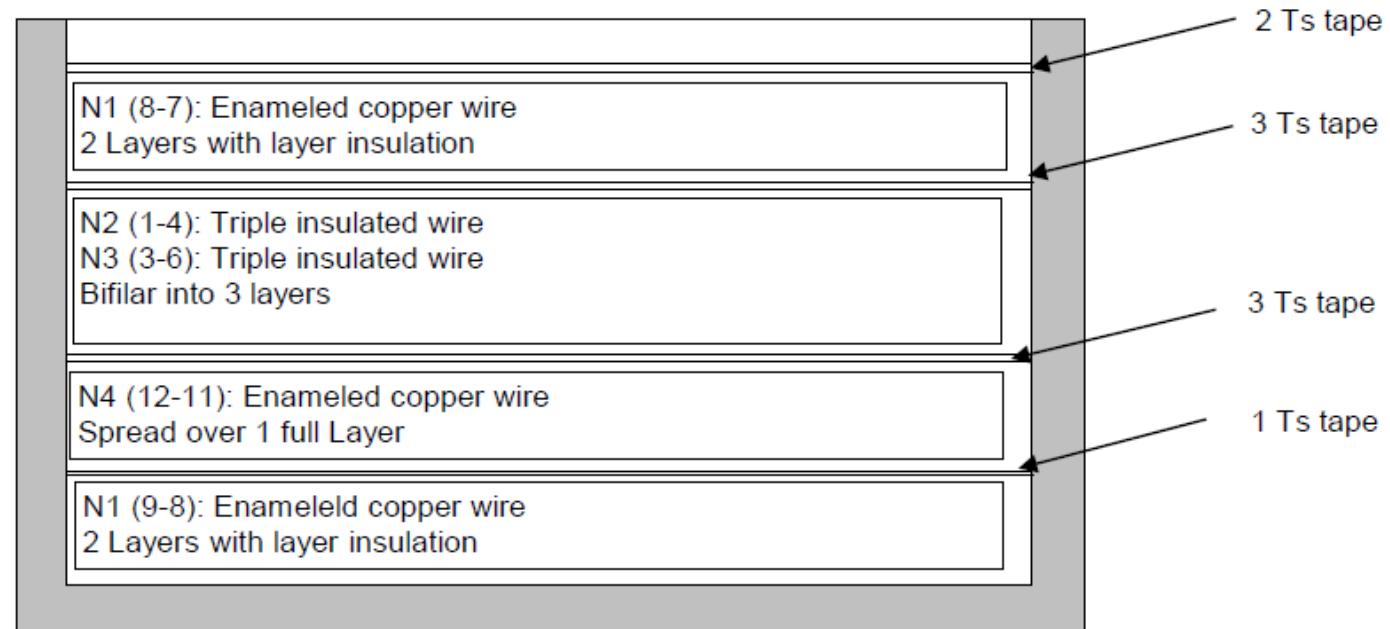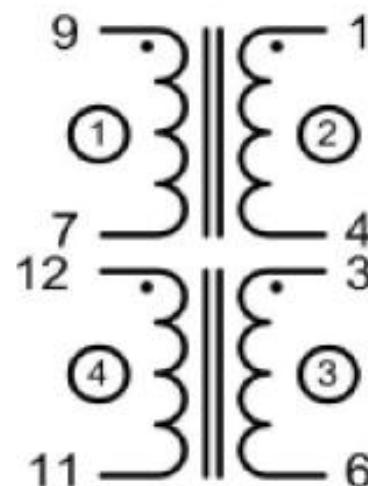

# Real life examples

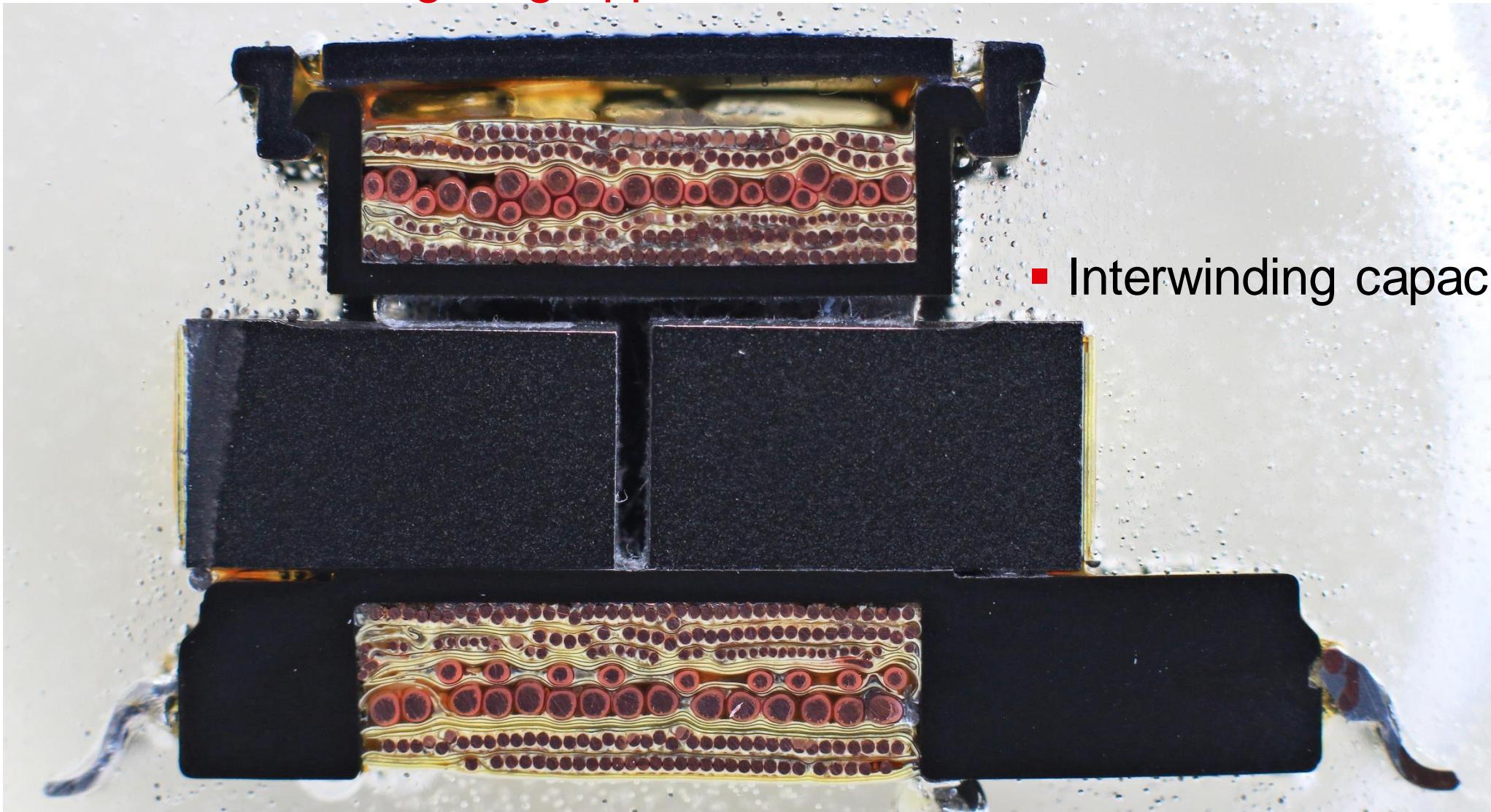
## Flyback converter for lighting applications



- Interwinding capacitance ?


# Real life examples
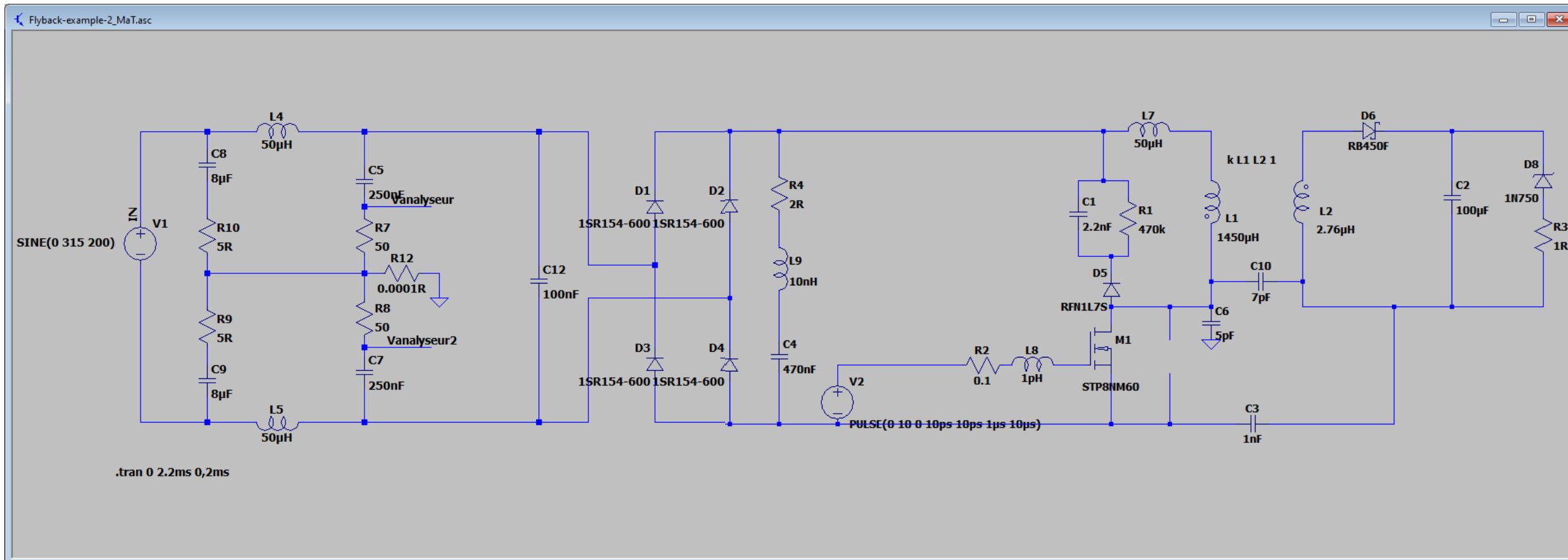
## Flyback converter for lighting applications



# Real life examples

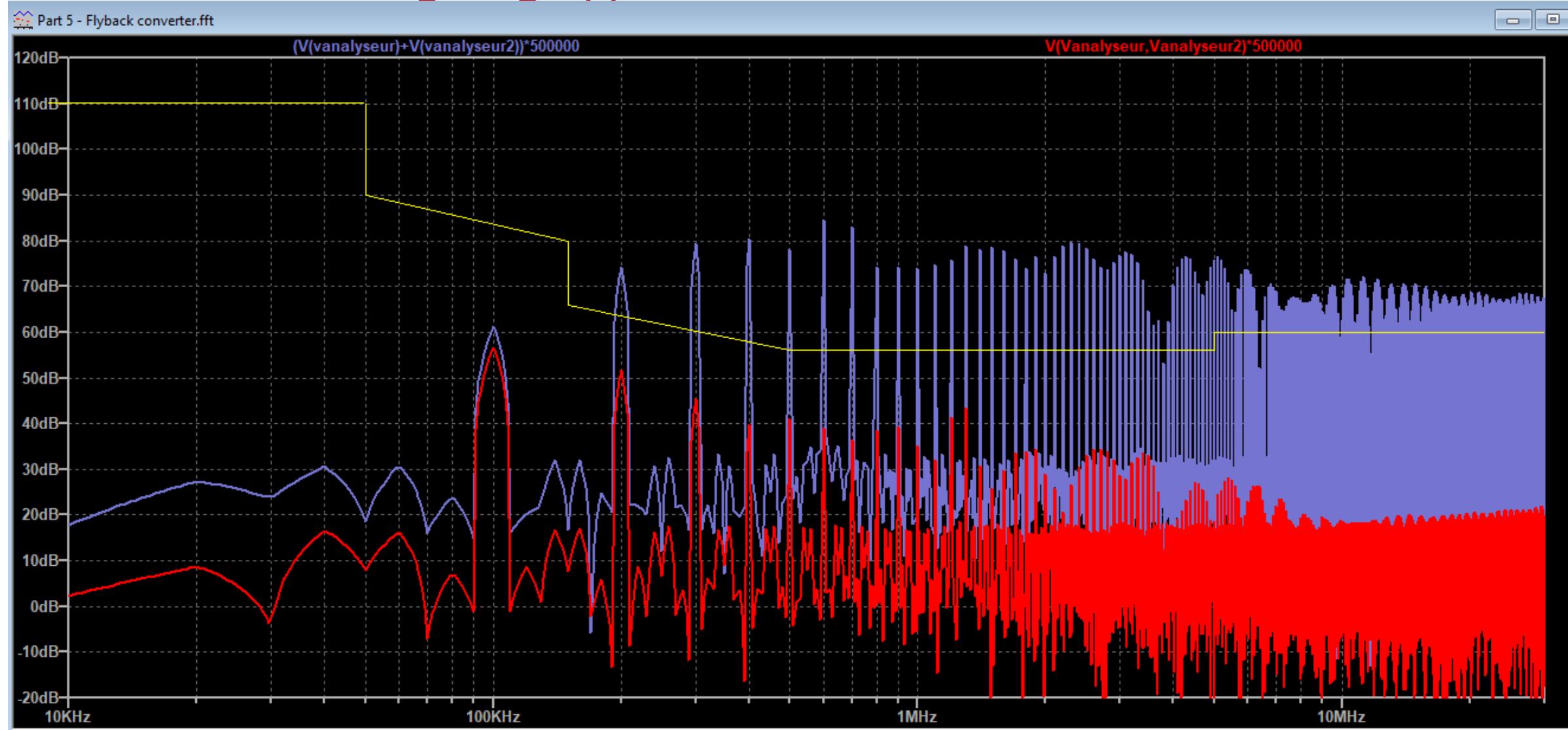
## Flyback converter for lighting applications




# Real life examples

## Flyback converter for lighting applications

Simulation

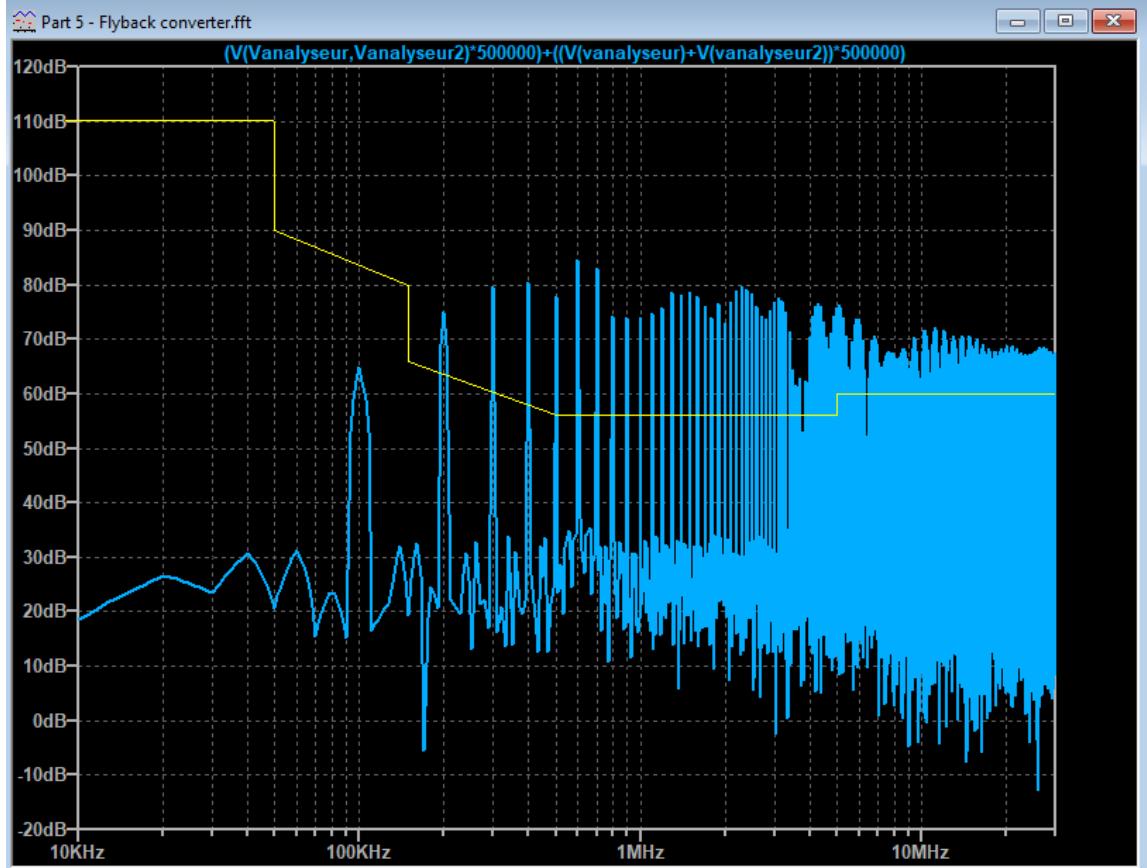

Example of actual measurement

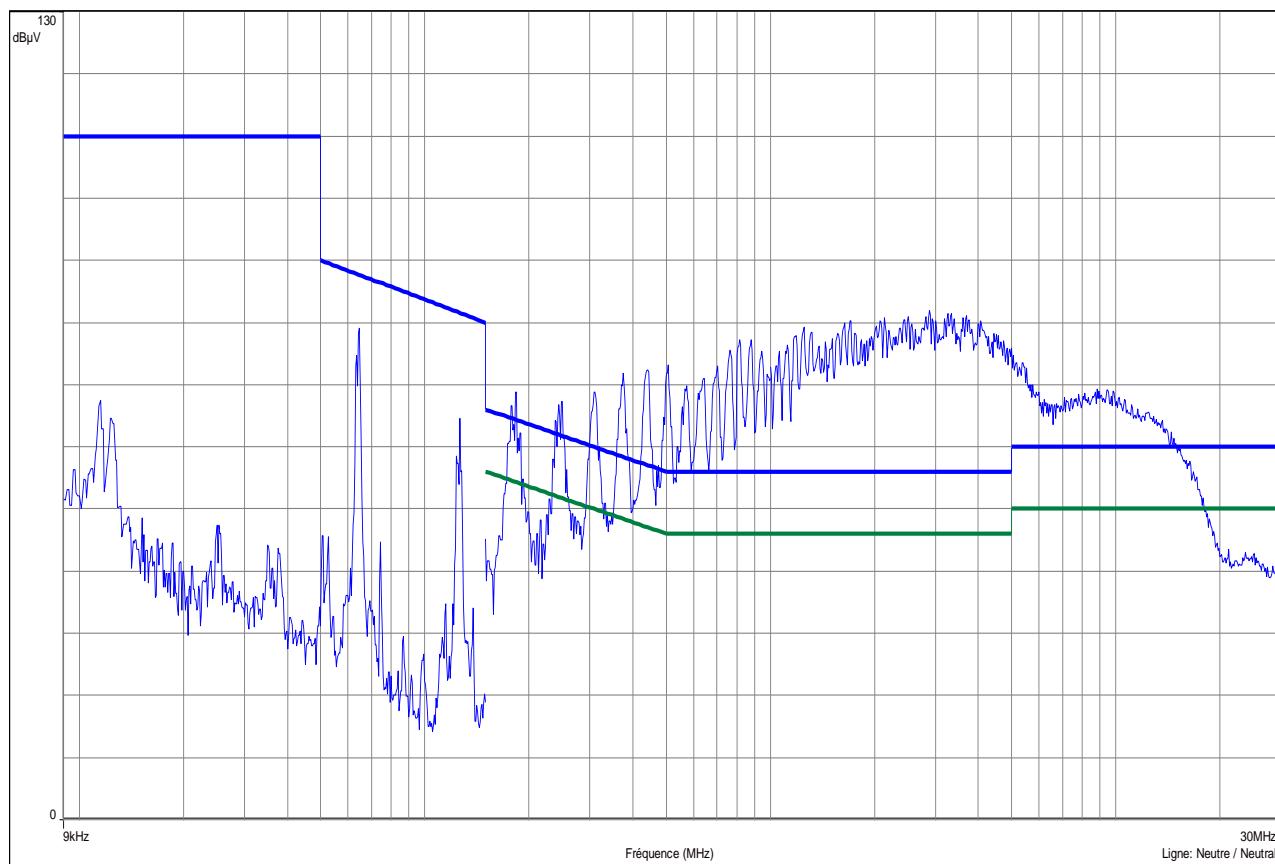

# Real life examples


## Mains voltage BLDC driver + motor



# Real life examples

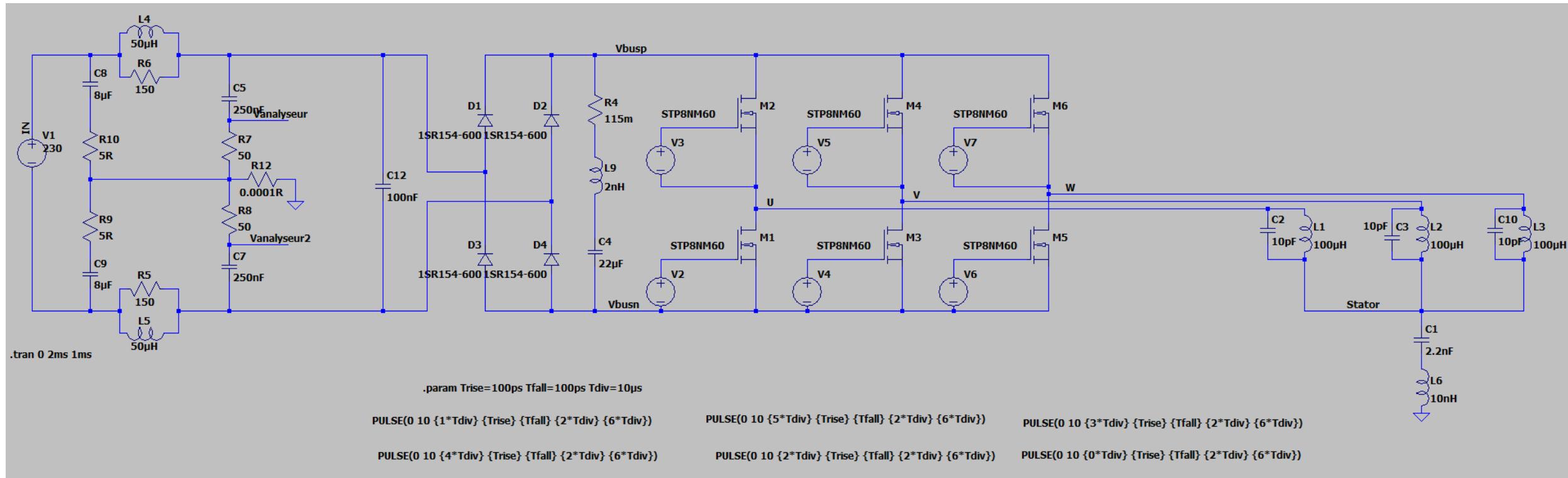
## Mains voltage BLDC driver + motor

- Parasitic coupling to and through stator
- Influence of grounding
- Slew rate of driver
- Dead time impact



# Real life examples


## Mains voltage BLDC driver + motor

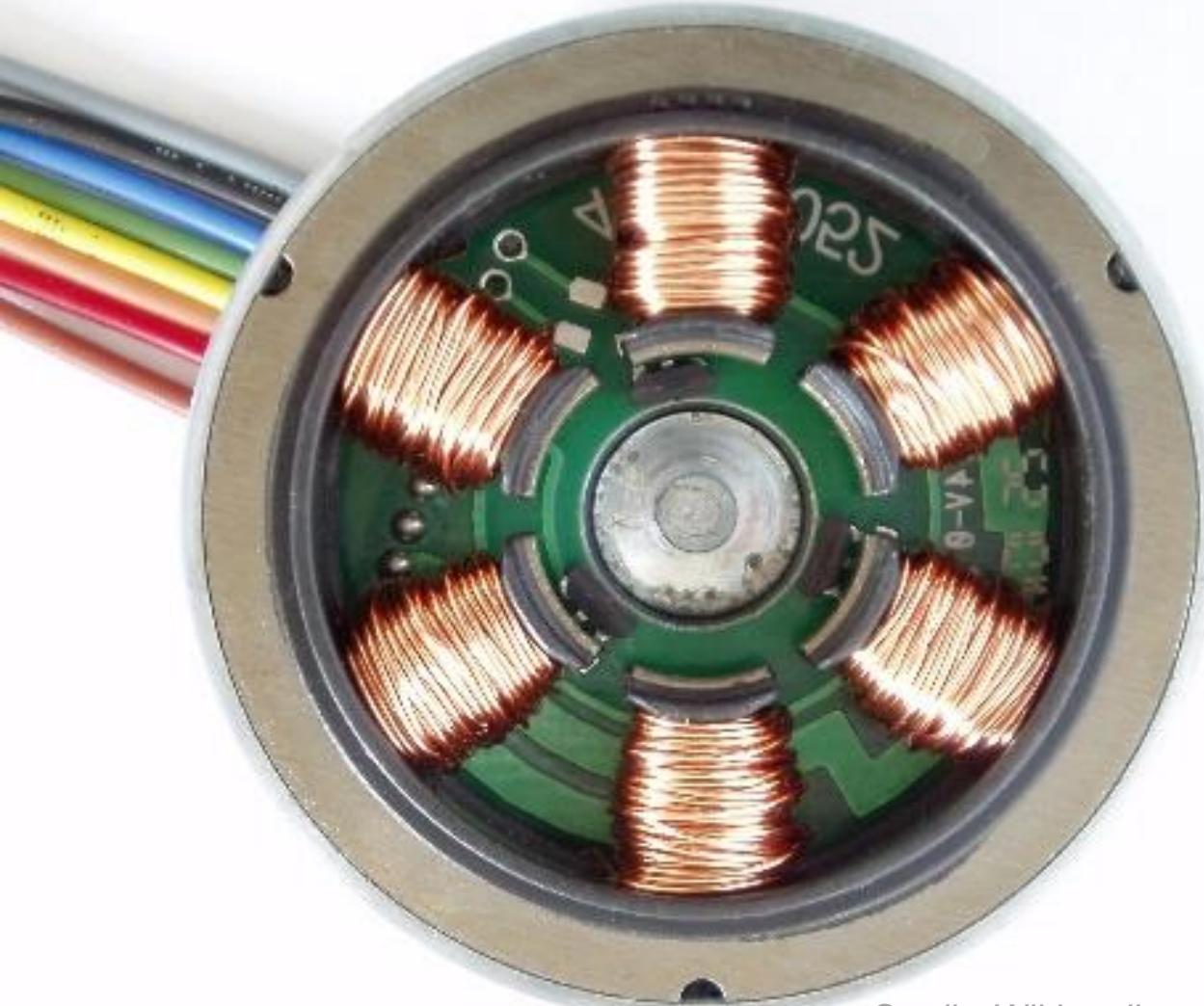

Credits Wikimedia commons



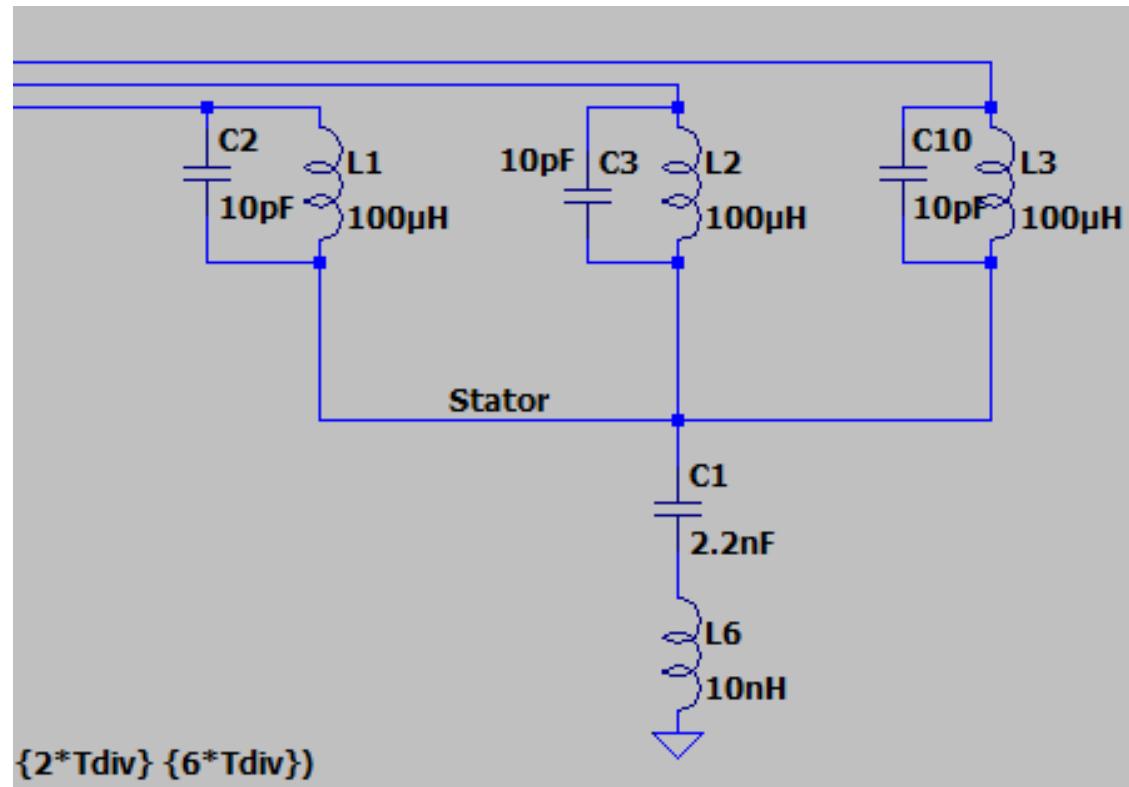
- Parasitic coupling to and through stator
- Influence of grounding (of stator)



$\{2^*T_{div}\} \{6^*T_{div}\}$

# Real life examples

## Mains voltage BLDC driver + motor

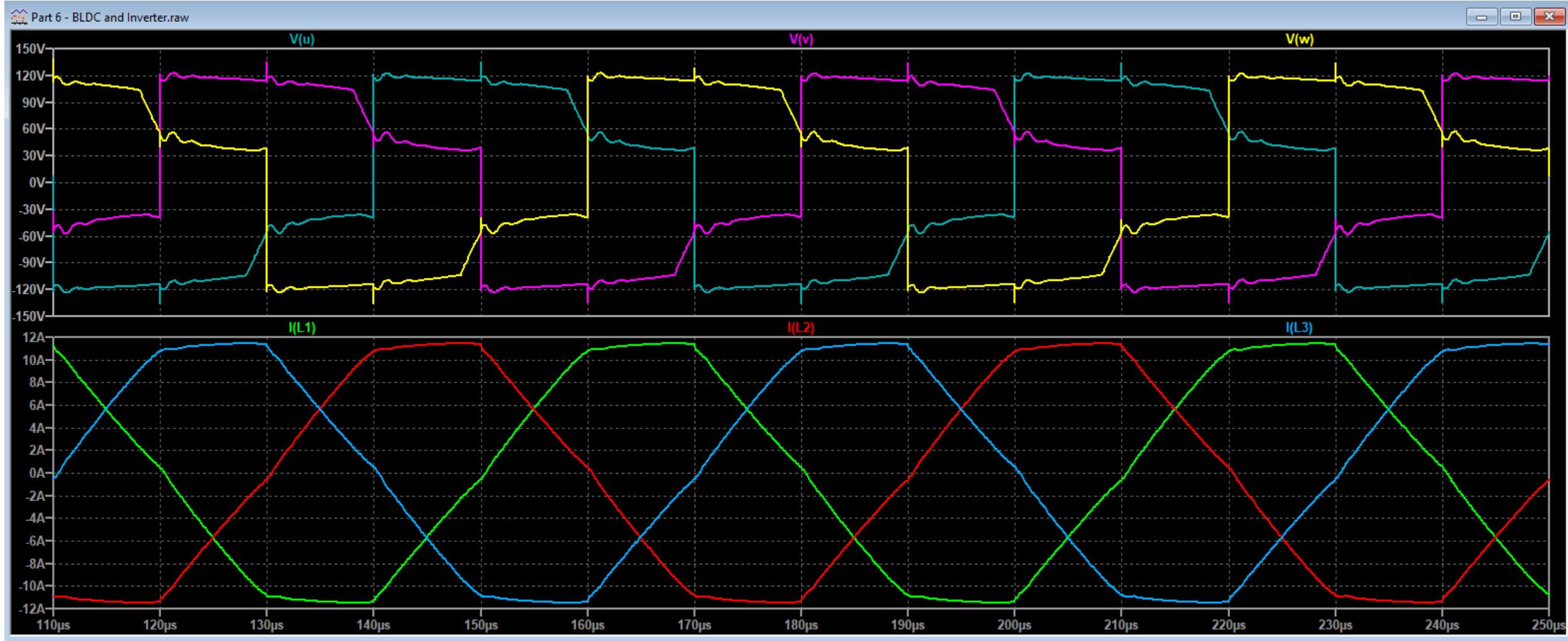


# Real life examples

## Mains voltage BLDC driver + motor

- Parametric simulation


```
.param Trise=100ps Tfall=100ps Tdiv=10μs
```

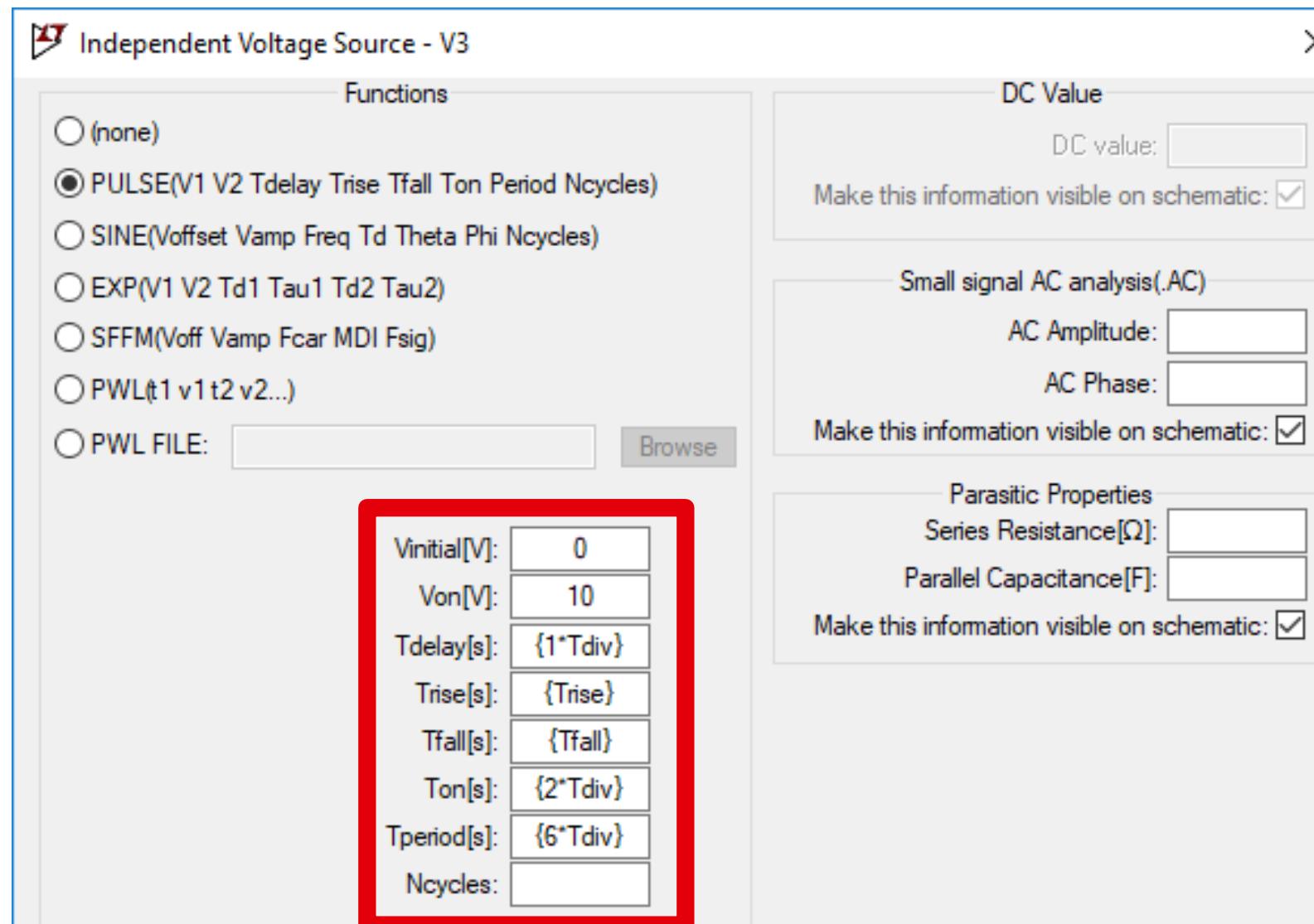- .STEP is possible to see impact of slew rate and dead time on EMC signature




# Real life examples

## Mains voltage BLDC driver + motor

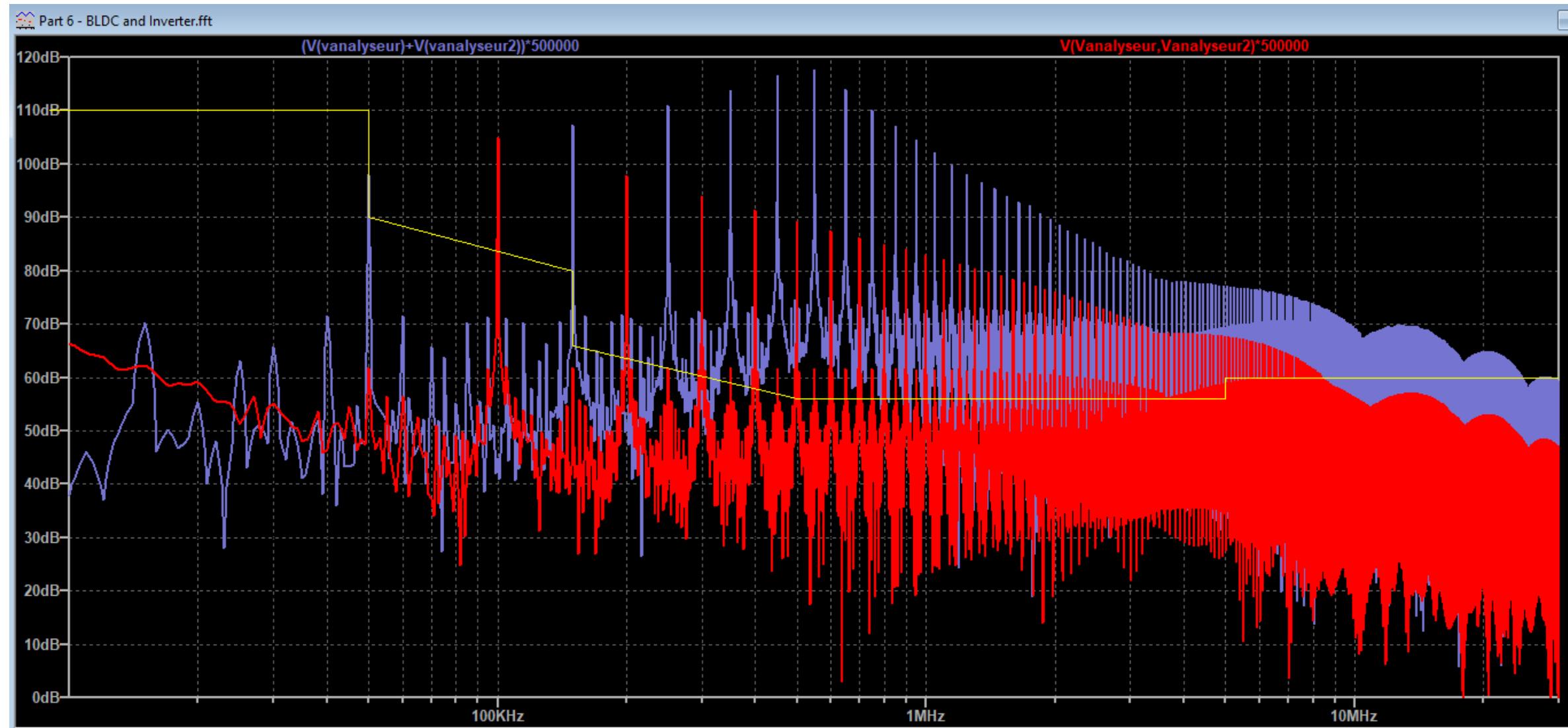

# Evaluation of Filter Insertion losses

Design your EMC filter in LTspice

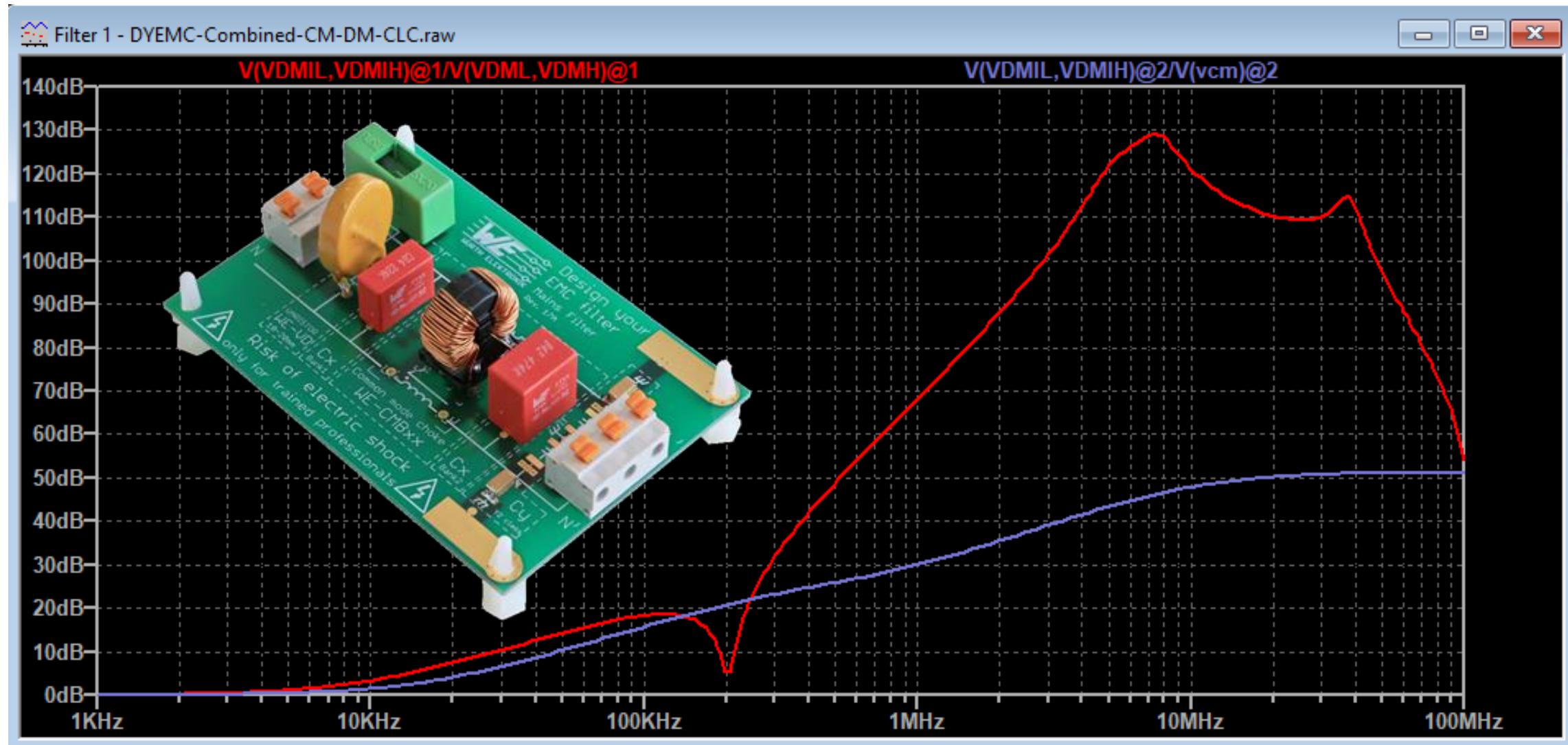


# Evaluation of Filter Insertion losses

Design your EMC filter in LTspice




**V(VDMIL,VDMIH)@1/V(VDML,VDMH)@1**

**V(VDMIL,VDMIH)@2/V(vcm)@2**

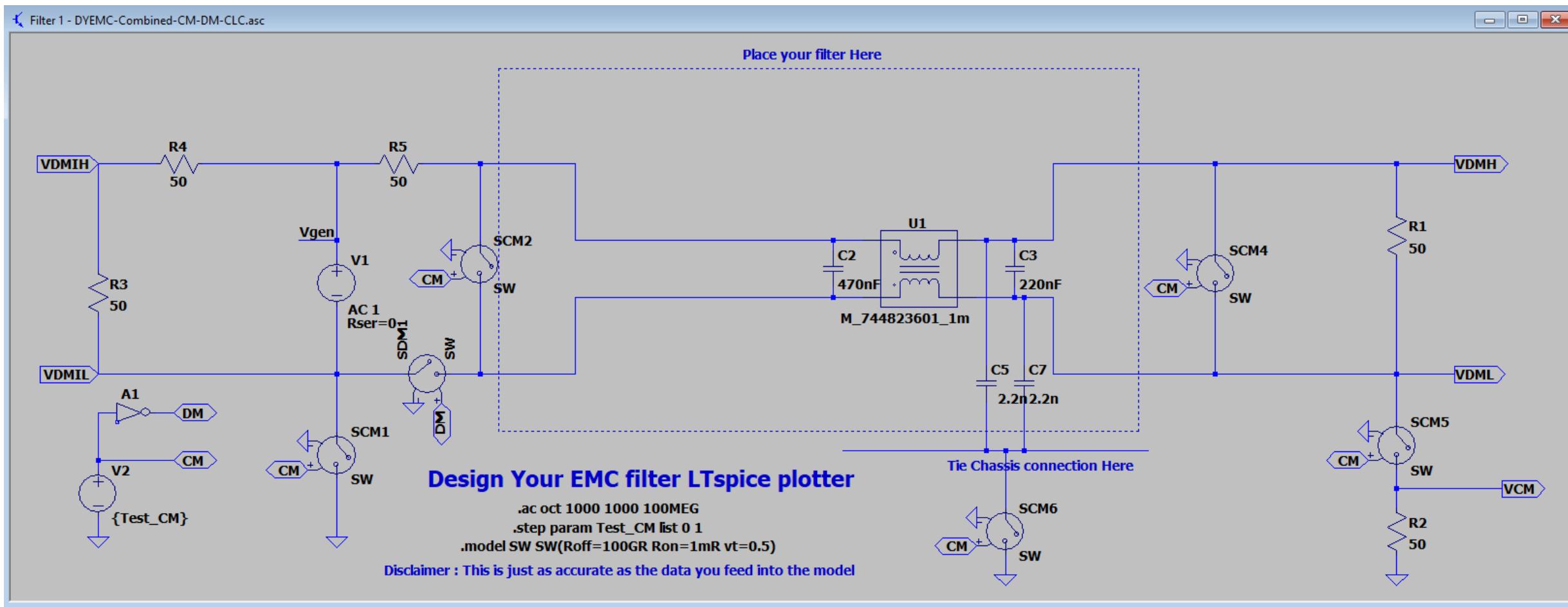


# Power Factor and Harmonic current

Anticipate IEC 61000-3-2

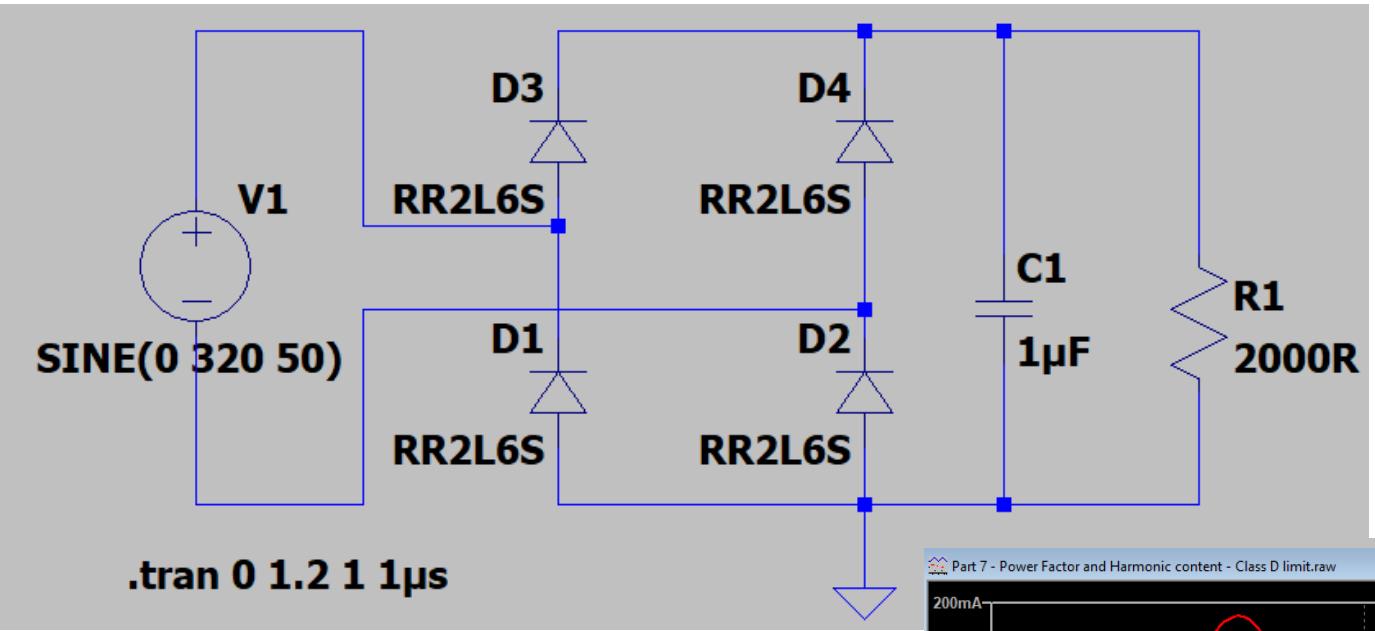


Harmonic order (n)	Maximum permissible harmonic current per watt (mA/W)
3	3.4
5	1.9
7	1.0
9	0.5
11	0.35
13	0.3
$15 \leq n \leq 39$ (odd harmonics only)	$3.85/n$

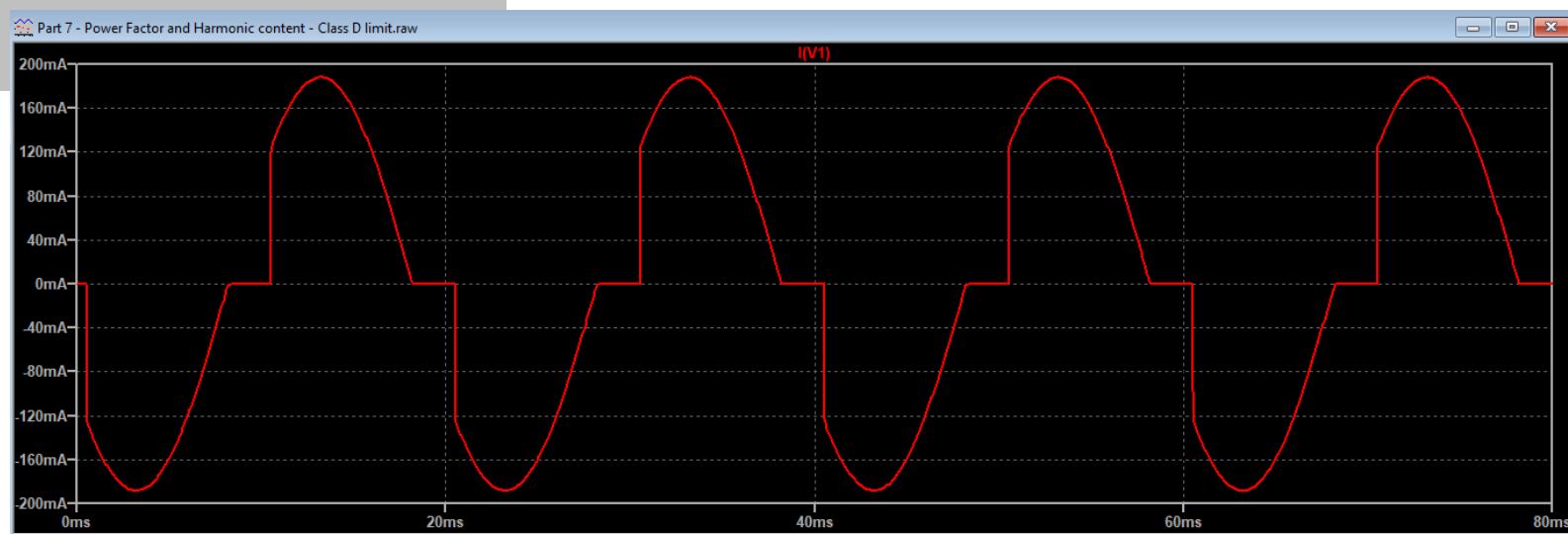

# Power Factor and Harmonic current

## Anticipate IEC 61000-3-2

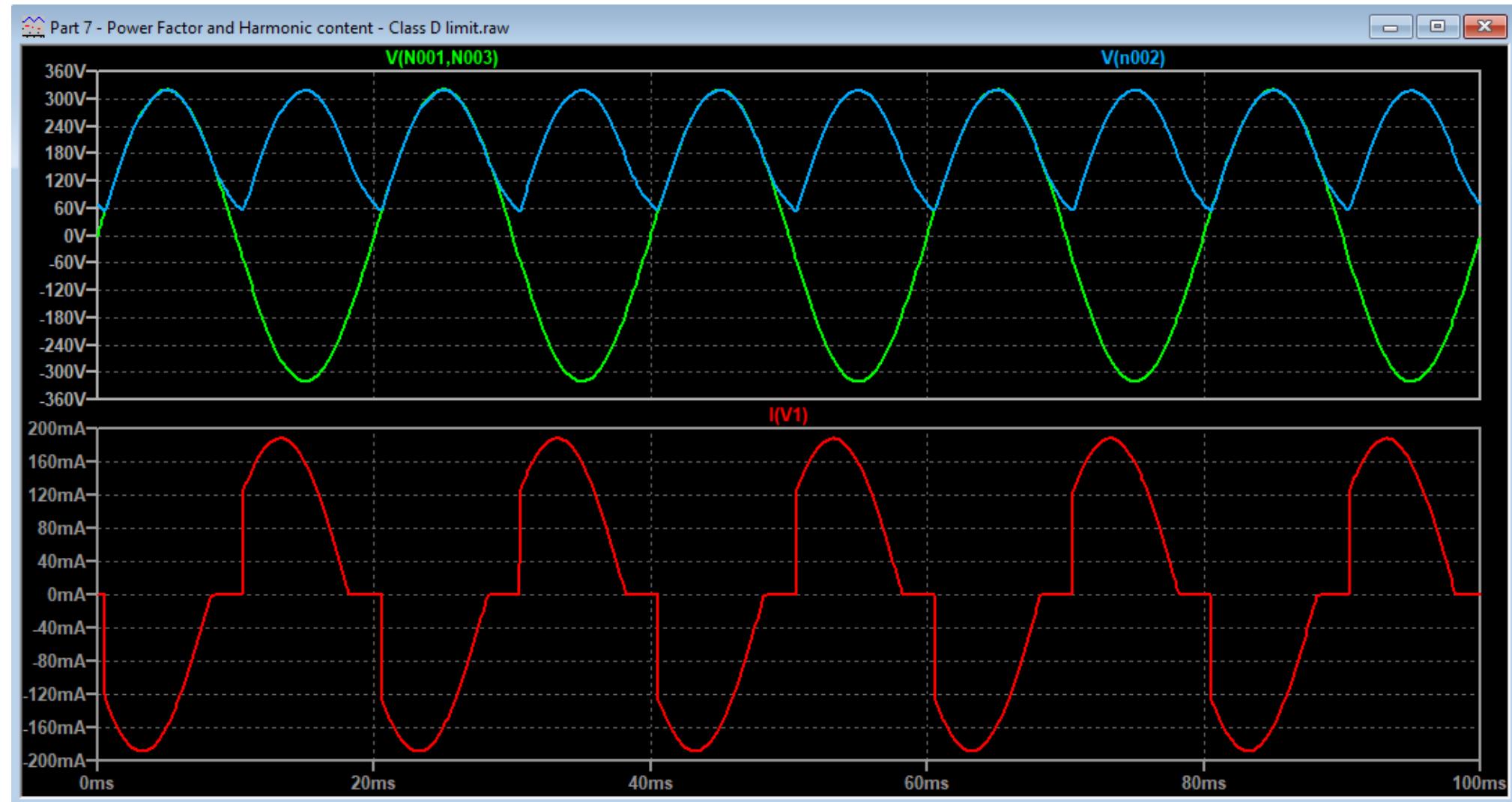


# Power Factor and Harmonic current

## Anticipate IEC 61000-3-2




Harmonic order (n)	Maximum permissible harmonic current per watt (mA/W)
3	3.4
5	1.9
7	1.0
9	0.5
11	0.35
13	0.3
$15 \leq n \leq 39$ (odd harmonics only)	$3.85/n$

?

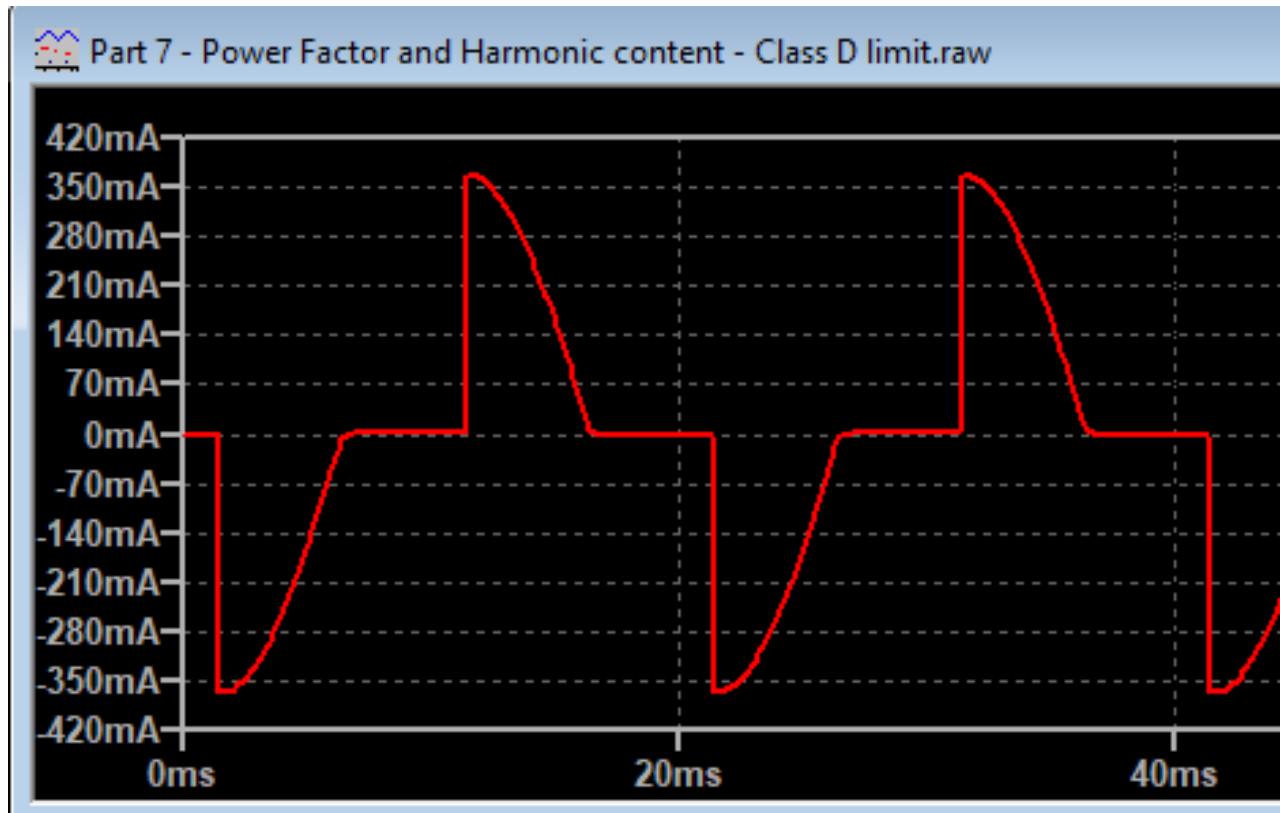
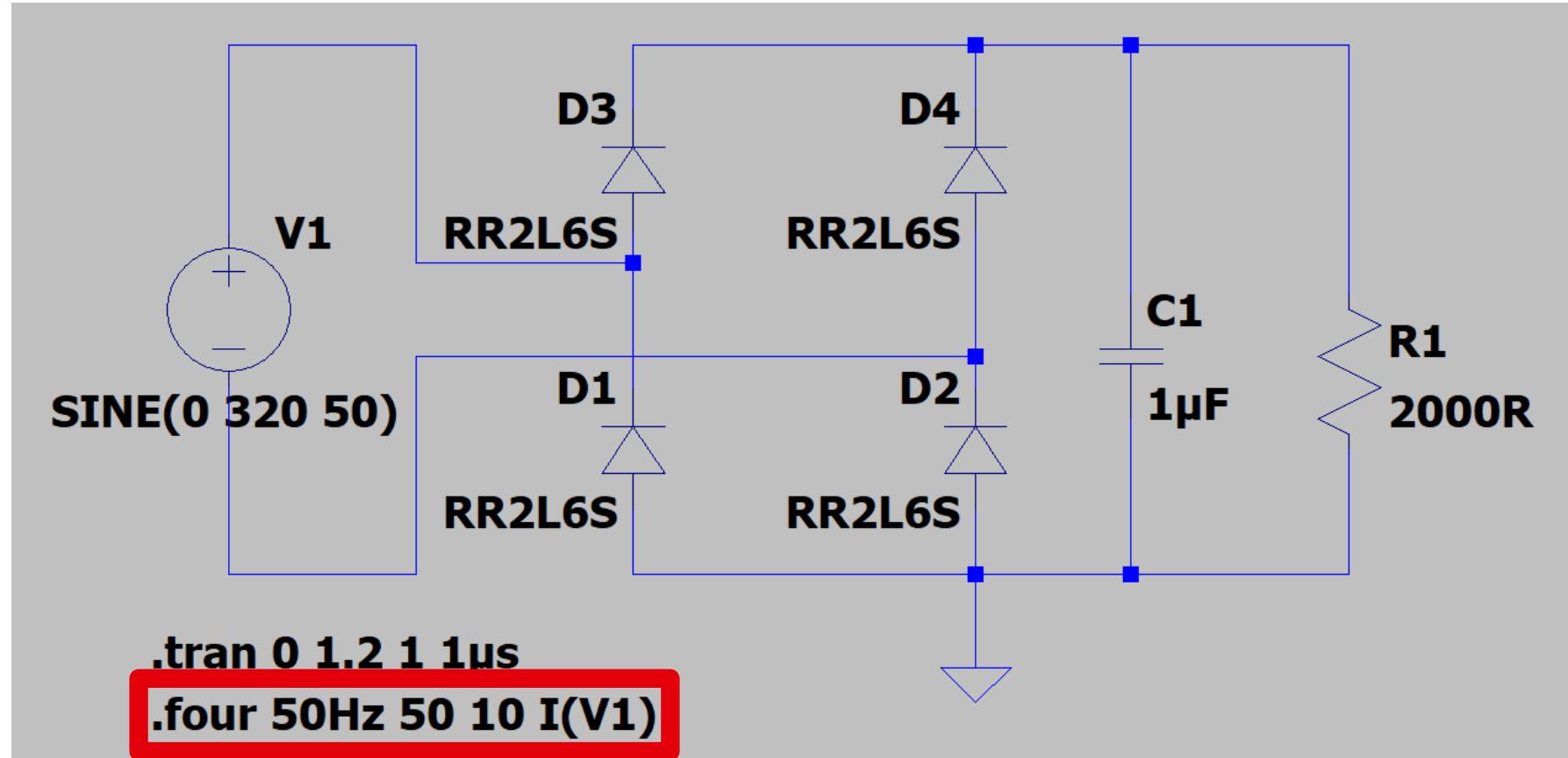
# Power Factor and Harmonic current

.FOUR directive to Anticipate IEC 61000-3-2




# Power Factor and Harmonic current

.FOUR directive to Anticipate IEC 61000-3-2



Fraction of  
Ampera  
fundamental

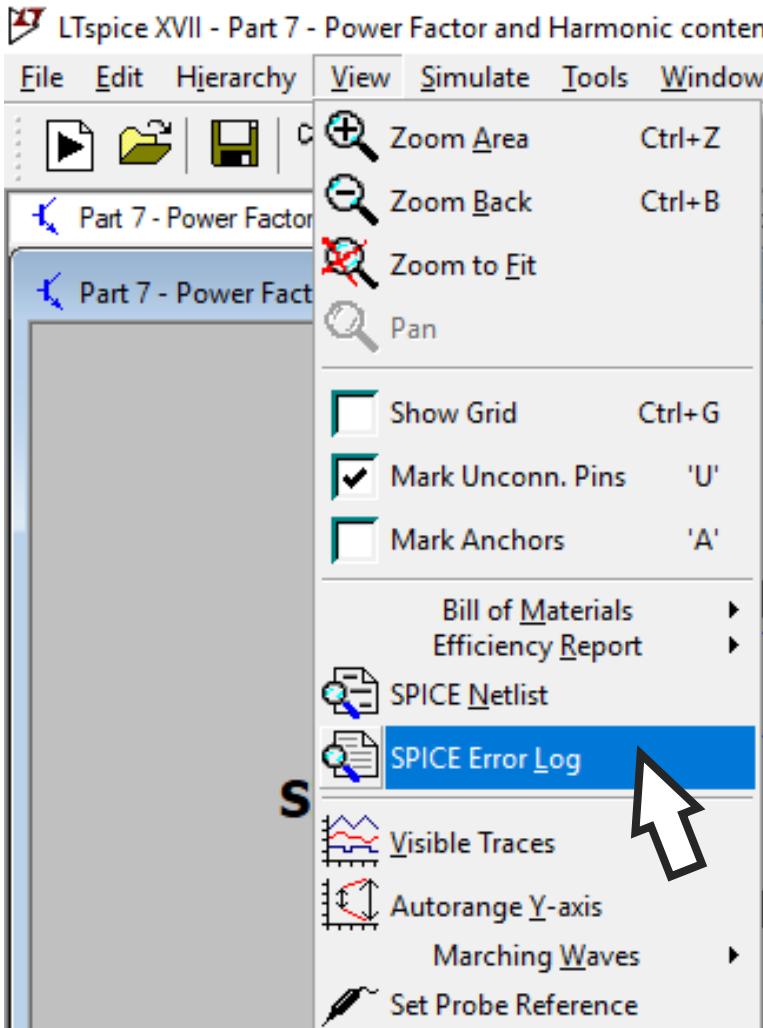

Fourier components of I(v1)			
Harmonic Number	Frequency [Hz]	Fourier Component	Normalized Component
1	5.000e+01	1.760e-01	1.000e+00
2	1.000e+02	3.265e-07	1.855e-06
3	1.500e+02	2.687e-02	1.526e-01
4	2.000e+02	1.123e-06	6.379e-06
5	2.500e+02	2.074e-02	1.178e-01
6	3.000e+02	2.040e-07	1.159e-06
7	3.500e+02	1.391e-02	7.904e-02
8	4.000e+02	9.960e-07	5.658e-06
9	4.500e+02	8.532e-03	4.847e-02
10	5.000e+02	9.480e-07	5.386e-06
11	5.500e+02	6.452e-03	3.665e-02
12	6.000e+02	7.110e-07	4.039e-06
13	6.500e+02	6.362e-03	3.614e-02
14	7.000e+02	1.526e-06	8.671e-06
15	7.500e+02	5.865e-03	3.332e-02
16	8.000e+02	4.225e-07	2.401e-06
17	8.500e+02	4.761e-03	2.705e-02
18	9.000e+02	1.168e-06	6.634e-06
19	9.500e+02	3.923e-03	2.229e-02
20	1.000e+03	8.830e-07	5.016e-06
21	1.050e+03	3.752e-03	2.131e-02
...	...	...	...
45	2.250e+03	1.732e-03	9.838e-03
46	2.300e+03	7.944e-07	4.513e-06
47	2.350e+03	1.685e-03	9.573e-03
48	2.400e+03	1.657e-07	9.416e-07
49	2.450e+03	1.657e-03	9.412e-03
50	2.500e+03	1.697e-07	4.373e-06
Total Harmonic Distortion: 23.211629% (23.614123%) PF=0.893698 (0.8929)			

Phase [degree]	Normalized Phase [deg]
-156.56°	0.00°
57.75°	214.31°
102.46°	259.01°
2.94°	159.50°
108.42°	264.98°
-164.89°	-8.33°
108.04°	264.59°
-63.52°	93.04°
93.80°	250.36°
125.74°	282.30°
64.05°	220.61°
-101.44°	55.12°
41.96°	198.52°
51.93°	208.48°
29.38°	185.94°
-89.14°	67.42°
14.64°	171.20°
-50.15°	106.41°
-8.40°	148.16°
-105.51°	51.05°
-31.96°	124.60°
-100.51°	55.00°
98.91°	255.46°
-44.86°	111.70°
77.95°	234.51°
-81.86°	74.69°
59.24°	215.79°
-107.70°	48.86°

# Power Factor and Harmonic current


Graphical method to anticipate IEC 61000-3-2



IEC 61000-3-2 Class D - LTSpice limit line calculator					
in 50Hz base	Start Freq	End Freq	mA/W start	Line def for LTSPICE plot settings file	
Line 3	130	170	3.4	Line: "A" 40	(130,0.0034) (170,0.0034)
Line 5	230	270	1.9	Line: "A" 40	(230,0.0019) (270,0.0019)
Line 7	330	370	1	Line: "A" 40	(330,0.001) (370,0.001)
Line 9	430	470	0.5	Line: "A" 40	(430,0.0005) (470,0.0005)
Line 11	530	570	0.35	Line: "A" 40	(530,0.00035) (570,0.00035)
Line 13	630	670	0.296153846	Line: "A" 40	(630,0.000296153846153846) (670,0.000296153846153846)
Line 15	730	770	0.2566666667	Line: "A" 40	(730,0.00025666666666666667) (770,0.00025666666666666667)
Line 17	830	870	0.226470588	Line: "A" 40	(830,0.000226470588235294) (870,0.000226470588235294)
Line 19	930	970	0.202631579	Line: "A" 40	(930,0.000202631578947368) (970,0.000202631578947368)
Line 21	1030	1070	0.1833333333	Line: "A" 40	(1030,0.0001833333333333) (1070,0.0001833333333333)
Line 23	1130	1170	0.167391304	Line: "A" 40	(1130,0.000167391304347826) (1170,0.000167391304347826)
Line 25	1230	1270	0.154	Line: "A" 40	(1230,0.000154) (1270,0.000154)
Line 27	1330	1370	0.142592593	Line: "A" 40	(1330,0.000142592592592593) (1370,0.000142592592592593)
Line 29	1430	1470	0.132758621	Line: "A" 40	(1430,0.000132758620689655) (1470,0.000132758620689655)
Line 31	1530	1570	0.124193548	Line: "A" 40	(1530,0.000124193548387097) (1570,0.000124193548387097)
Line 33	1630	1670	0.1166666667	Line: "A" 40	(1630,0.000116666666666667) (1670,0.000116666666666667)
Line 35	1730	1770	0.11	Line: "A" 40	(1730,0.00011) (1770,0.00011)
Line 37	1830	1870	0.104054054	Line: "A" 40	(1830,0.000104054054054054) (1870,0.000104054054054054)
Line 39	1930	1970	0.098717949	Line: "A" 40	(1930,9.87179487179487E-05) (1970,9.87179487179487E-05)


# Power Factor and Harmonic current
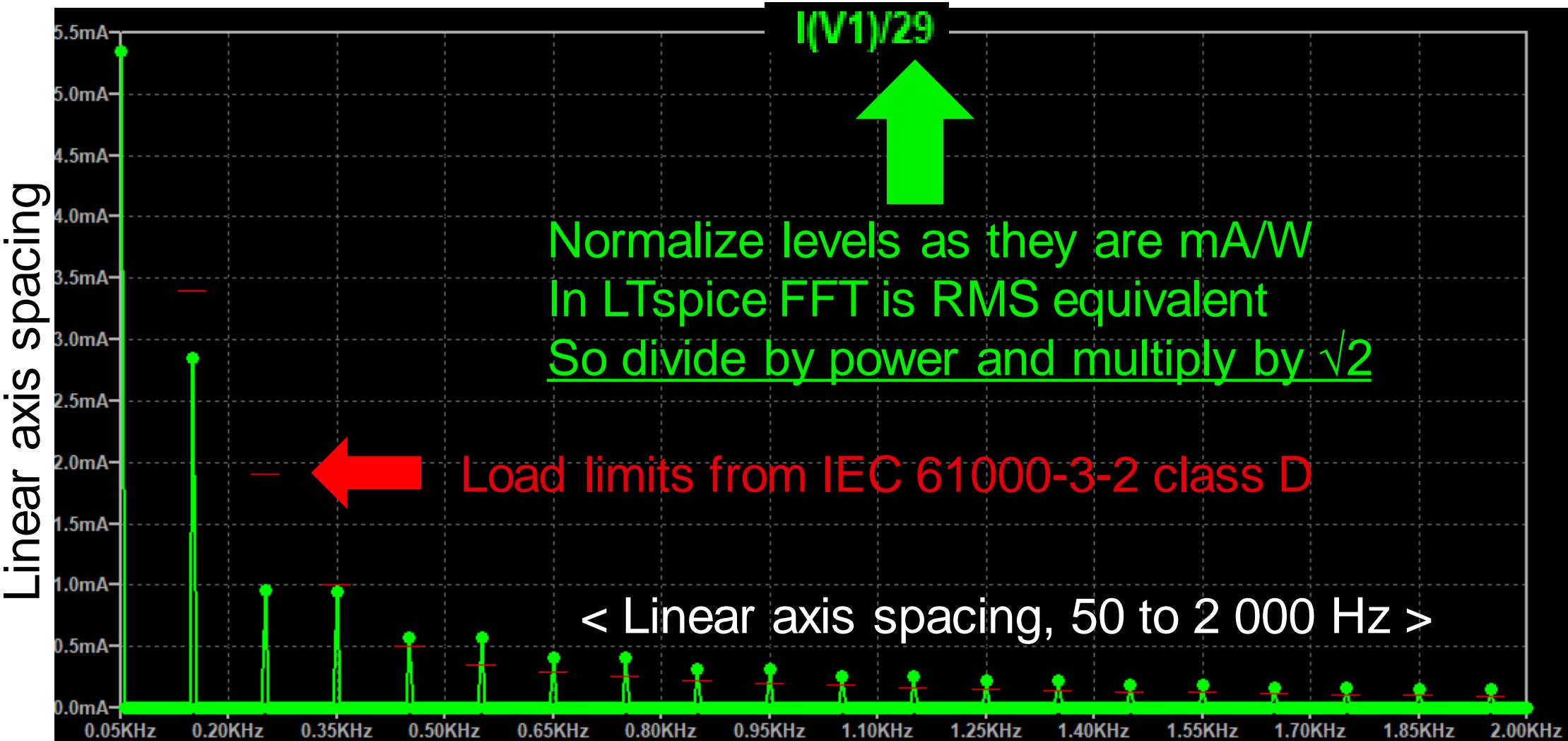
## Graphical method to anticipate IEC 61000-3-2



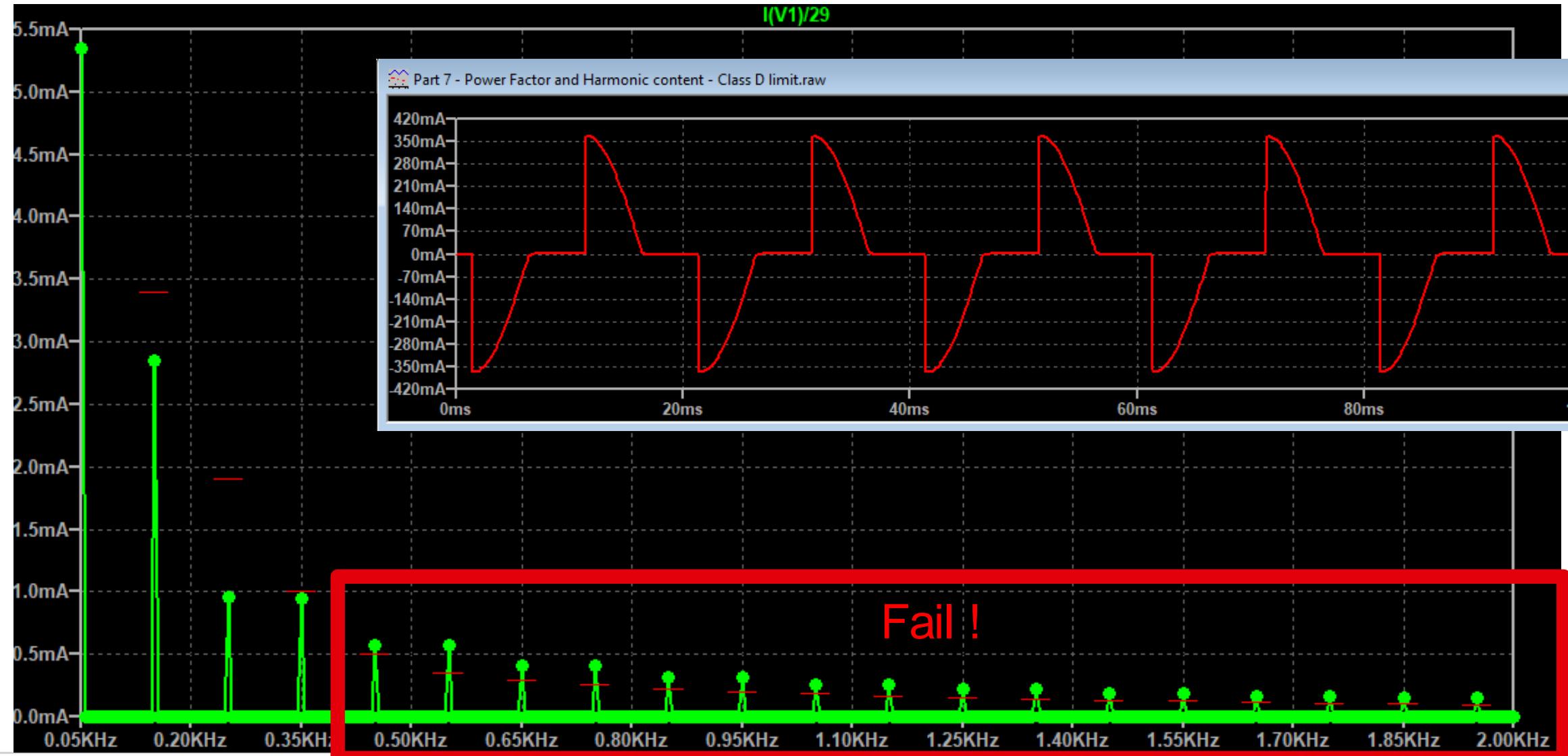
# Power Factor and Harmonic current

Graphical method to anticipate IEC 61000-3-2



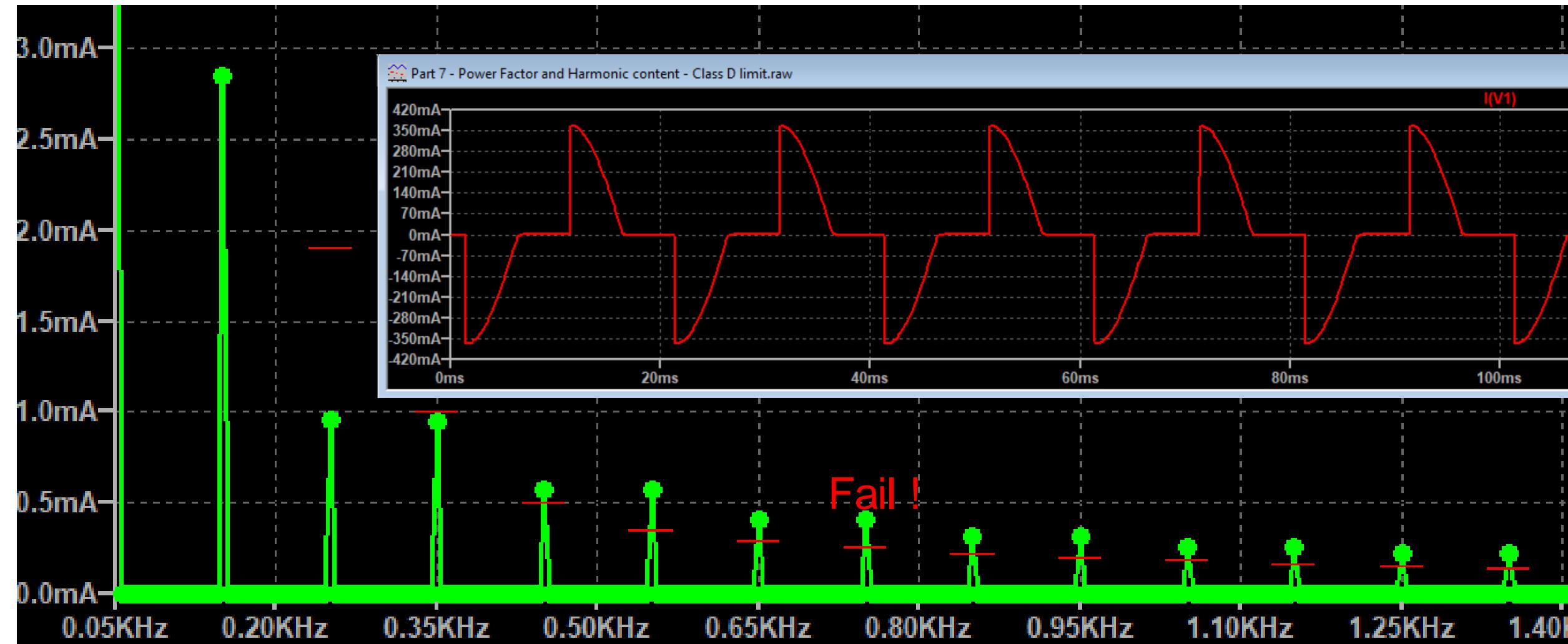
# Power Factor and Harmonic current

Graphical method to anticipate IEC 61000-3-2





# Power Factor and Harmonic current
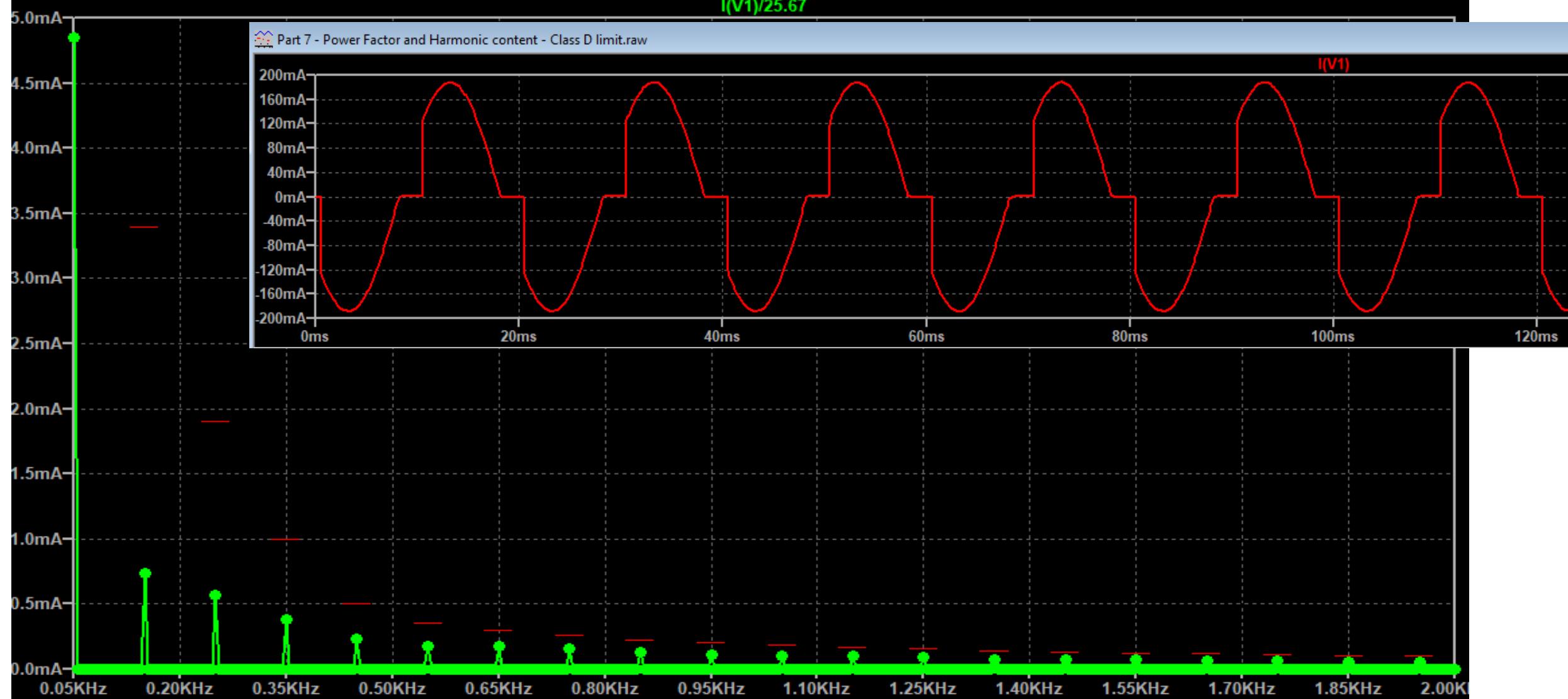
## Graphical method to anticipate IEC 61000-3-2



# Good to know

## Speed up simulations

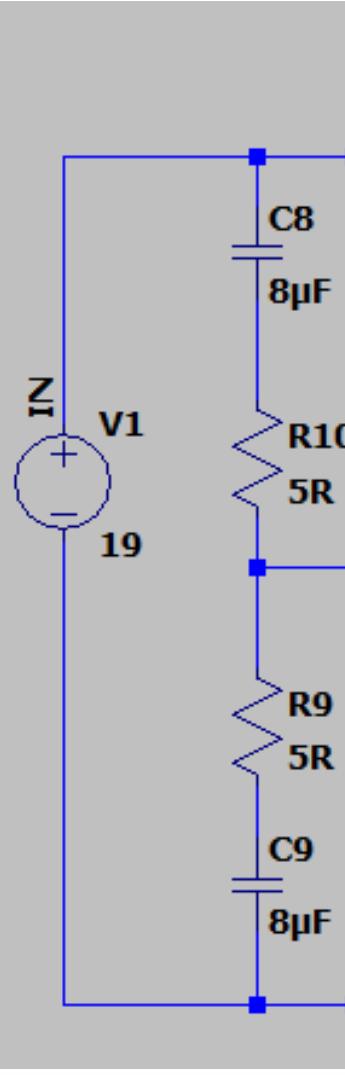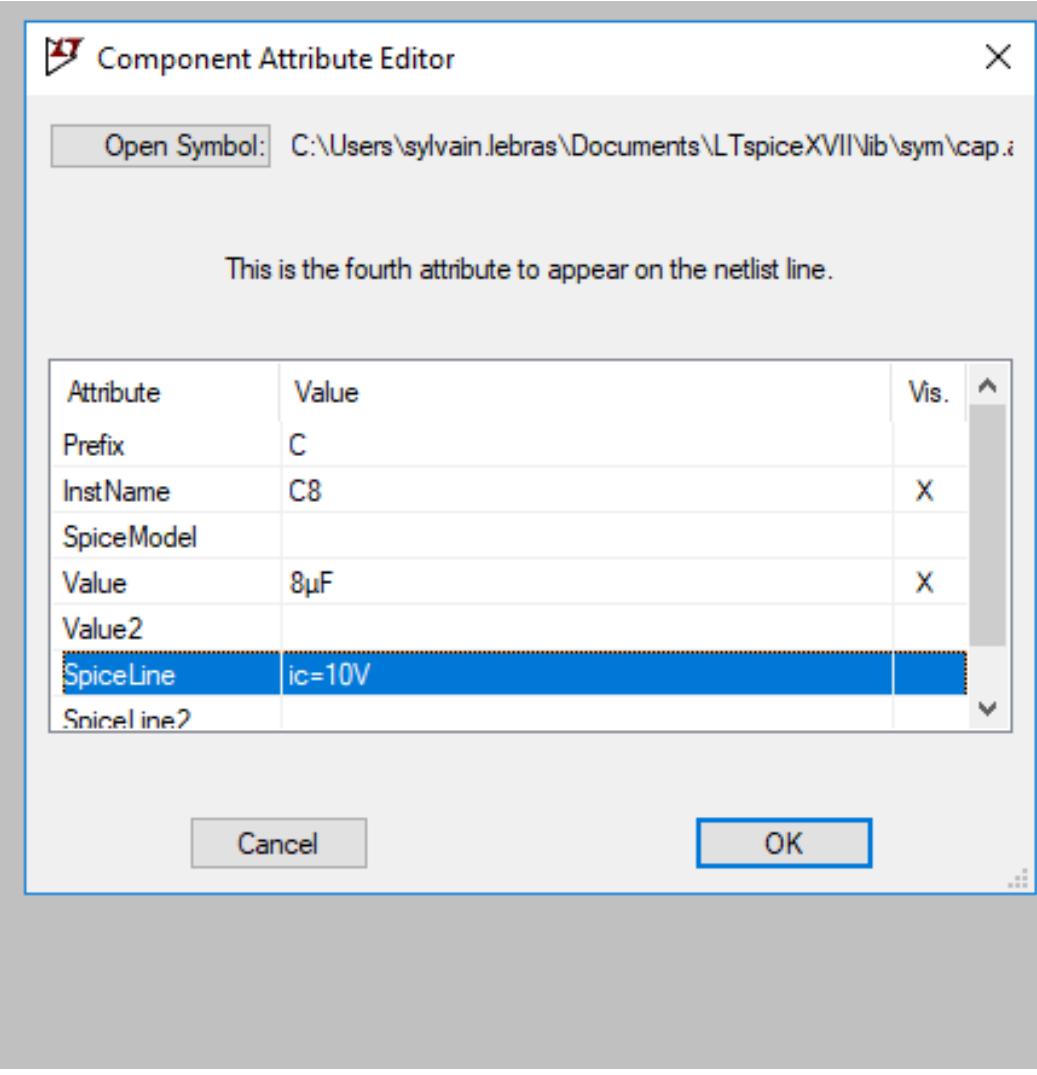

## Setting initial condition

- Ctrl + Right Click
- SpiceLine
  - $ic=10V$